 


Basics of Operational Amplifiers

UNIT – I





CONTENTS

- ▶ Operational Amplifiers
 - Basic Informations (IC741)
 - Characteristics of Ideal Op–Amp
 - Operational Amplifier Stages
 - Internal circuits of IC741
 - DC and AC Characteristics (Slew rate)
 - Open and Closed loop configurations
- ▶ BJT Differential Amplifier
- ▶ Current Mirror, Current sources(Widlor and Wilson)
- ▶ Voltage sources

Operational Amplifier (Op-Amp)

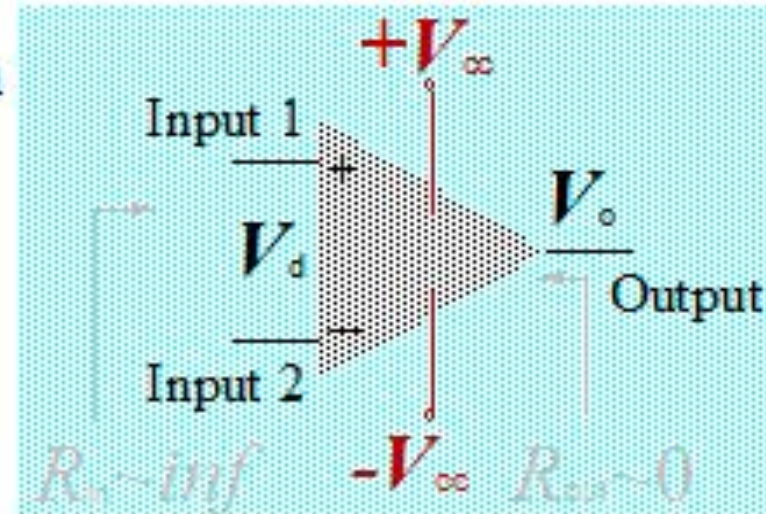
- Very high differential gain
- High input impedance
- Low output impedance
- Used in oscillator, filter and instrumentation
- Accumulate a very high gain by multiple stages



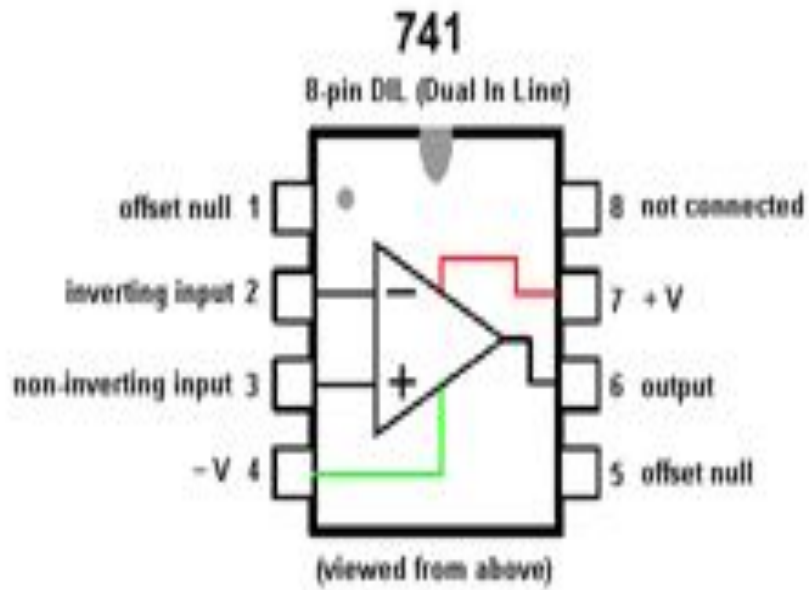

Common-Mode Operation

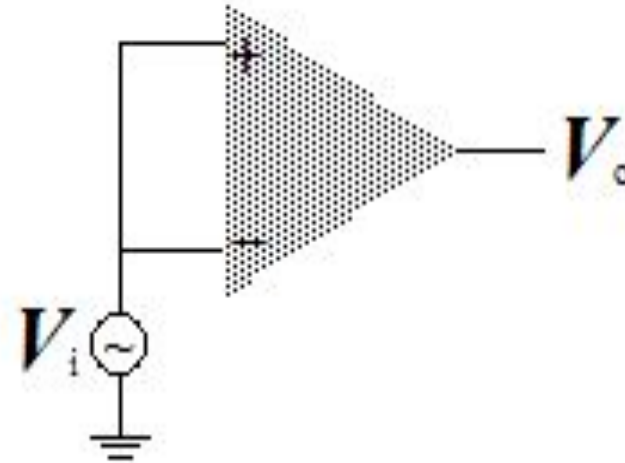- Same voltage source is applied at both terminals
- Ideally, two input are equally amplified
- Output voltage is ideally zero due to differential voltage is zero
- Practically, a small output signal can still be measured



Common-Mode Rejection Ratio (CMRR)

Differential voltage input :

$$V_d = V_+ - V_-$$

Common voltage input :


$$V_c = \frac{1}{2}(V_+ + V_-)$$

Output voltage :

$$V_o = G_d V_d + G_c V_c$$

G_d : Differential gain

G_c : Common mode gain

 


Common-mode rejection ratio:

$$\text{CMRR} = \frac{G_d}{G_c} = 20 \log_{10} \frac{G_d}{G_c} \text{ (dB)}$$

Noninverting Amplifier

(1) Kirchhoff node equation at V_+ yields, $V_+ = V_i$

 (2) Kirchhoff node equation at V_- yields, $\frac{V_- - 0}{R_a} + \frac{V_- - V_o}{R_f} = 0$




$V_+ = V_-$ yields

$$\frac{V_i}{R_a} + \frac{V_i - V_o}{R_f} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = 1 + \frac{R_f}{R_a}$$

Inverting Amplifier

(1) Kirchhoff node equation at V_+
yields, $V_+ = 0$

 (2) Kirchhoff node equation at V_-
yields, $\frac{V_{in} - V_-}{R_a} + \frac{V_o - V_-}{R_f} = 0$



$V_+ = V_-$ yields

$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_a}$$


Characteristics of Ideal Op-Amp

- For an ideal Op-Amp, $V_1 = V_2 = 0$ and hence
 $i_1 = i_2 = 0$
- Open loop voltage gain $A_{OL} = \infty$
- Input Impedance $R_i = \infty$
- Output Impedance $R_o = 0$
- Bandwidth $BW = \infty$

Stages and Internal circuit of general Op–Amp (IC 741)

▶ General Stages

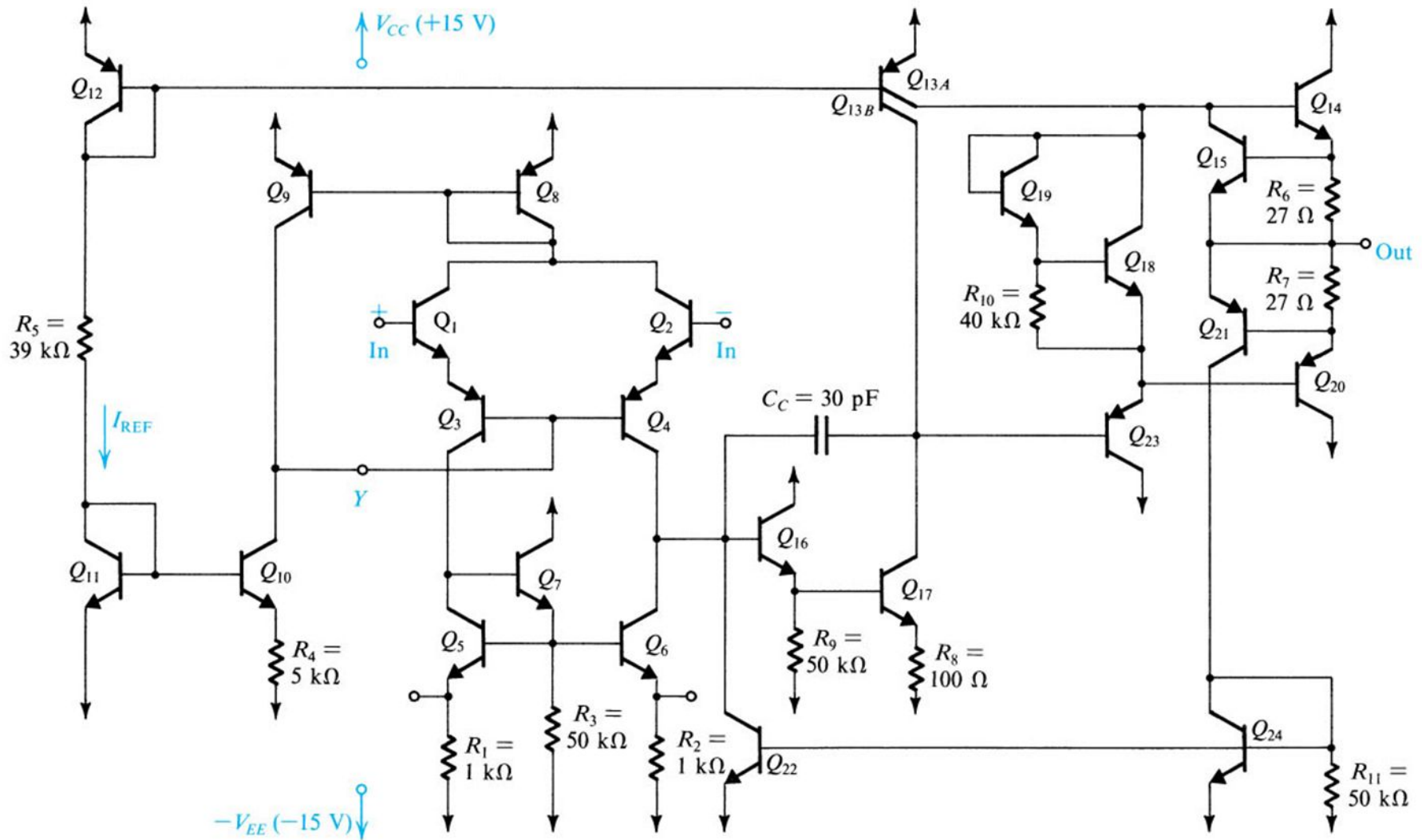- Input Stage
- Intermediate Stage
- Buffer and Level Shifting Stage
- Output Stage



The Input Stage

- The input stage consists of transistors $Q1$ through $Q7$.
- $Q1$ - $Q4$ is the differential version of CC and CB configuration.
- High input resistance.
- Current source ($Q5$ - $Q7$) is the active load of input stage. It not only provides a high-resistance load but also converts the signal from differential to single-ended form with no loss in gain or common-mode rejection.



The Intermediate Stage

- The intermediate stage is composed of Q_{16} , Q_{17} and Q_{13B} .
- Common-collector configuration for Q_{16} gives this stage a high input resistance as well as reduces the load effect on the input stage.
- Common-emitter configuration for Q_{17} provides high voltage gain because of the active load Q_{13B} .
- Capacitor C_c introduces the miller compensation to insure that the op amp has a very high unit-gain frequency.

Level Shifting Stage

- ▶ All stages coupled to each other, hence voltage level of previous stage applied to next stages.
- ▶ So stage by stage d.c level increases , such high voltage drives the transistors into saturation
- ▶ Hence before output stage, it is necessary to bring such high voltage to zero volt.
- ▶ Level shifter brings the d.c level down to ground potential when no signal is applied
- ▶ The buffer is an emitter follower whose input impedance is very high.


The Output Stage

- The output stage is the efficient circuit called class AB output stage.
- Voltage source composed of Q_{18} and Q_{19} supplies the DC voltage for Q_{14} and Q_{20} in order to reduce the cross-over distortion.
- Q_{23} is the CC configuration to reduce the load effect on intermediate stage.
- Short-circuit protection circuitry
 - Forward protection is implemented by R_6 and Q_{15} .
 - Reverse protection is implemented by R_7 , Q_{21} , current source (Q_{24} , Q_{22}) and intermediate stage.

DC Characteristics


- ▶ Input Bias Current (I_b)
- ▶ Input Offset Current (I_{os})
- ▶ Input Offset Voltage (V_{ios})
- ▶ Thermal Drift

Input Bias Current

 


$$\text{Bias Current } I_B = \frac{I_b^+ + I_b^-}{2}$$

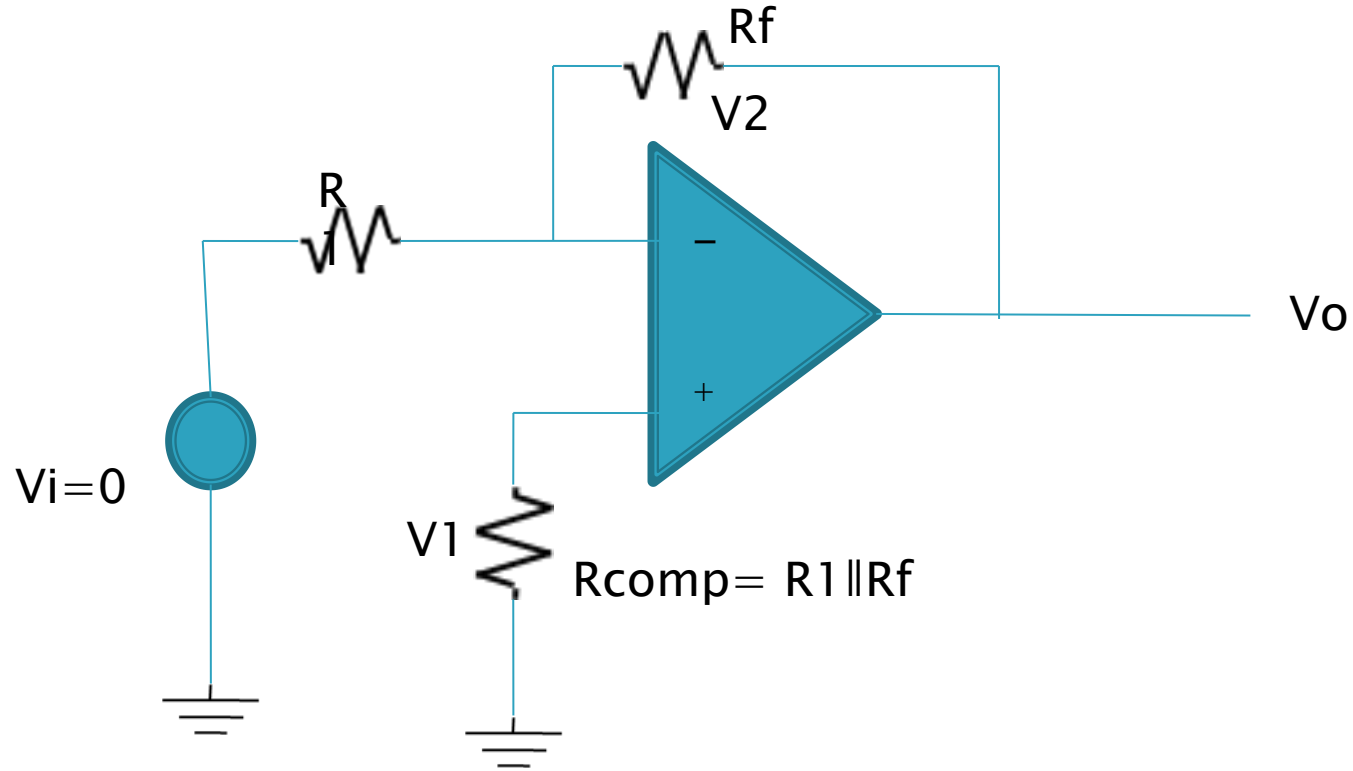Bias Current Compensation in Inverting mode



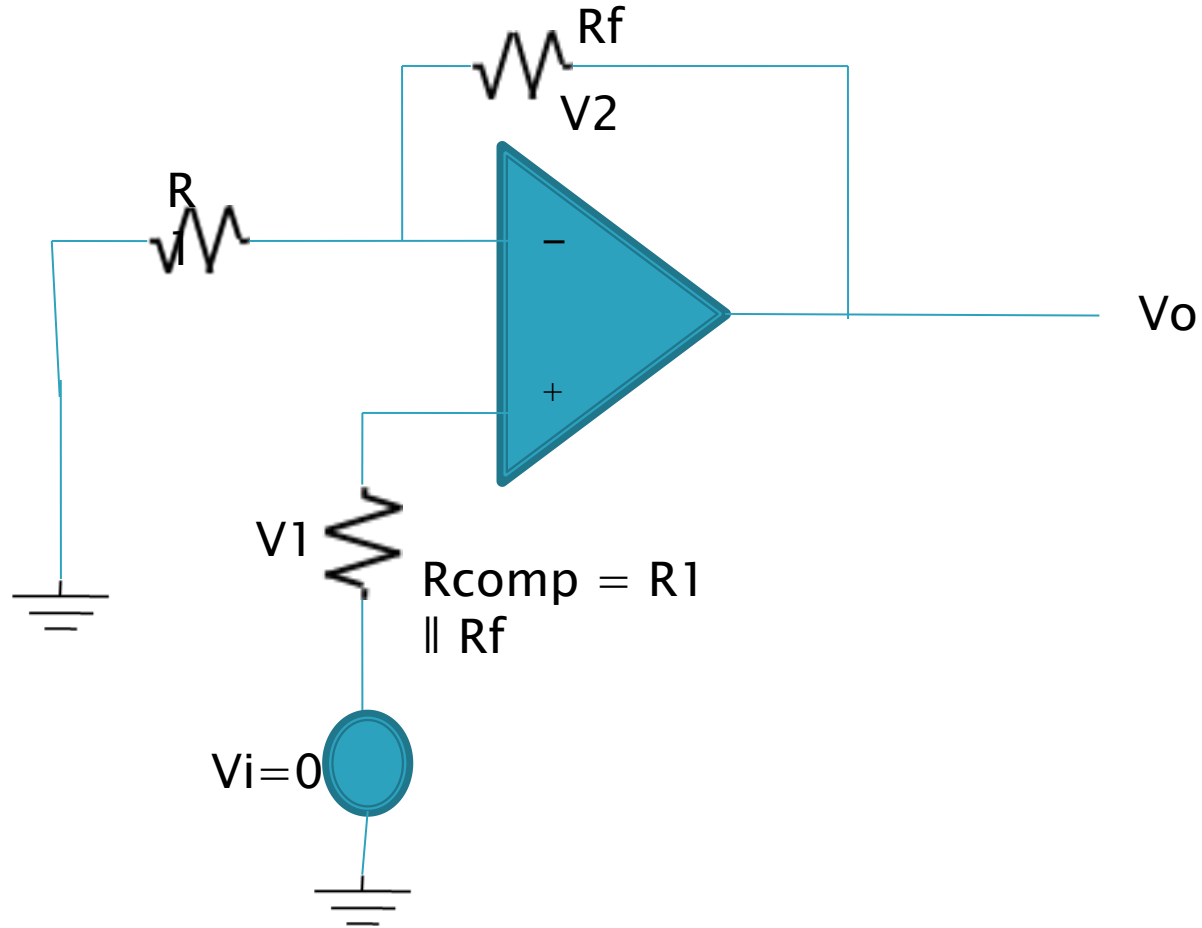Bias Current Compensation in Non Inverting mode



Input Offset Current

- ▶ Input Offset current will work if both bias currents are equal.
- ▶ If they are not equal, the difference between them is known as Input Offset current

$$I_{os} = I_b^+ - I_b^-$$

Input Offset Voltage

- Due to unavoidable imbalances inside the op-amp, the output voltage will not be zero with zero input voltage. This voltage is called as input offset voltage.

Considering this voltage V_{ios} ,

$$\text{Output Voltage } V_o = \left(1 + \frac{R_f}{R_1}\right) V_{ios}$$

Thermal Drift

- ▶ Bias current, Offset current and Offset voltages change with temperature. This change is called as drift.
- ▶ Offset current drift is expressed in $\text{nA}/^{\circ}\text{C}$
- ▶ Offset voltage drift is expressed in $\text{mV}/^{\circ}\text{C}$
- ▶ To avoid this drift careful printed circuit board layout must be used and forced air cooling may be used to stabilize the ambient temperature.

AC Characteristics (Slew Rate – SR)

▶ The maximum rate of change of output voltage caused by step input voltage, specified in $V/\mu s$

▶ **Cause of SR:**

There is a **capacitor** within an op-amp which prevent the output voltage from responding immediately to a fast change in input. This capacitor caused the SR

- For example, if $V_o = V_m \sin \omega t$

Then the rate of change of output is,

$$\frac{dv_o}{dt} = V_m \omega \cos \omega t$$


The maximum rate of change occurs when $\cos \omega t = 1$

Therefore $SR = (dv_o/dt)_{\max} = \omega V_m$

Or $SR = 2\pi f V_m \text{ V/s}$

Or $SR = \frac{2\pi f V_m}{10^6} \text{ V}/\mu\text{s}$


Open Loop Operation

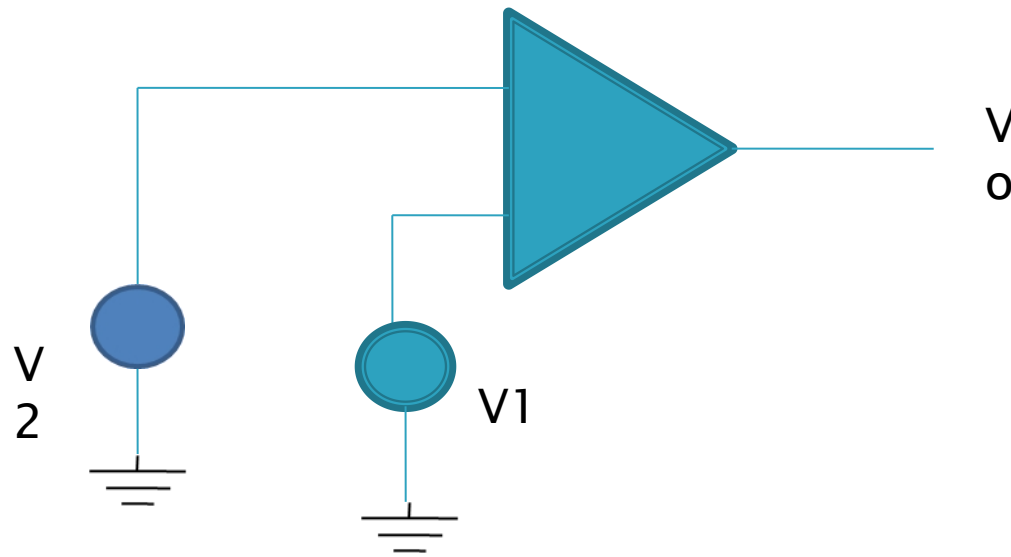

Open loop operation

- ▶ Simplest way of operation in op-amp
- ▶ V_1 and V_2 applied to non-inverting and inverting terminals respectively
- ▶ V_o will be either at positive saturation or negative saturation as $V_1 > V_2$ or $V_2 > V_1$ respectively
- ▶ Hence amplifier acts as switch only
- ▶ Applications as voltage comparator, zero crossing detector.

Closed Loop Operation

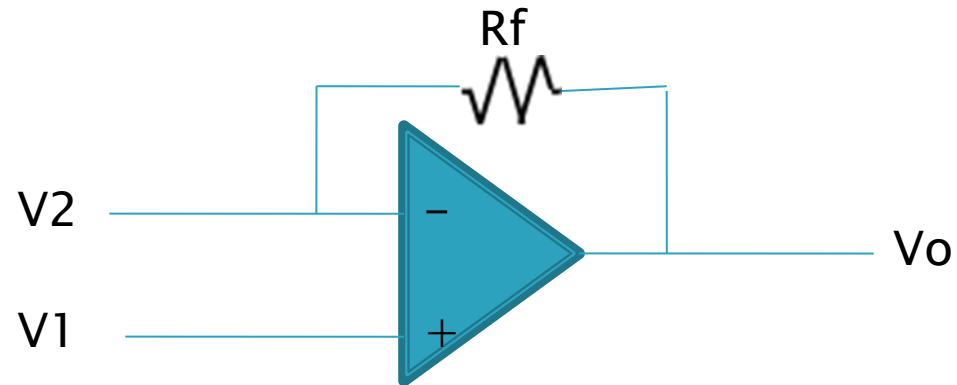


Closed loop Operation

- ▶ Mostly used configuration
- ▶ The feedback allows to feed the some part of output back to input
- ▶ The feedback is said to be negative as the resistor connects the output to inverting terminal
- ▶ Closed loop gain is much less than Open loop gain
- ▶ It reduces the possibility of distortion, increases the BW.

Differential Amplifier

 - ▶ Amplifies the difference between two input voltages. ($V_d = V_1 - V_2$)




- ▶ $V_o \propto (V_1 - V_2)$
- ▶ $V_o = A_d(V_1 - V_2)$ where $A_d =$ Differential Gain
 $V_o = A_d V_d$, hence $A_d = V_o / V_d$
 $A_d = 20 \log A_d$ (dB)

Common Mode Gain

- ▶ If two input voltages are equal, it is common mode
- ▶ Then common mode voltage $V_c = (V_1 + V_2) / 2$
- ▶ Now output voltage $V_o = A_c V_c$
- ▶ Total voltage for any differential amplifier is
$$V_o = A_d V_d + A_c V_c$$
- ▶ CMMR = A_d / A_c (or) $20 \log (A_d / A_c)$ dB

BJT Differential Amplifier

 


The basic BJT differential-pair configuration.



Difference Mode Operation

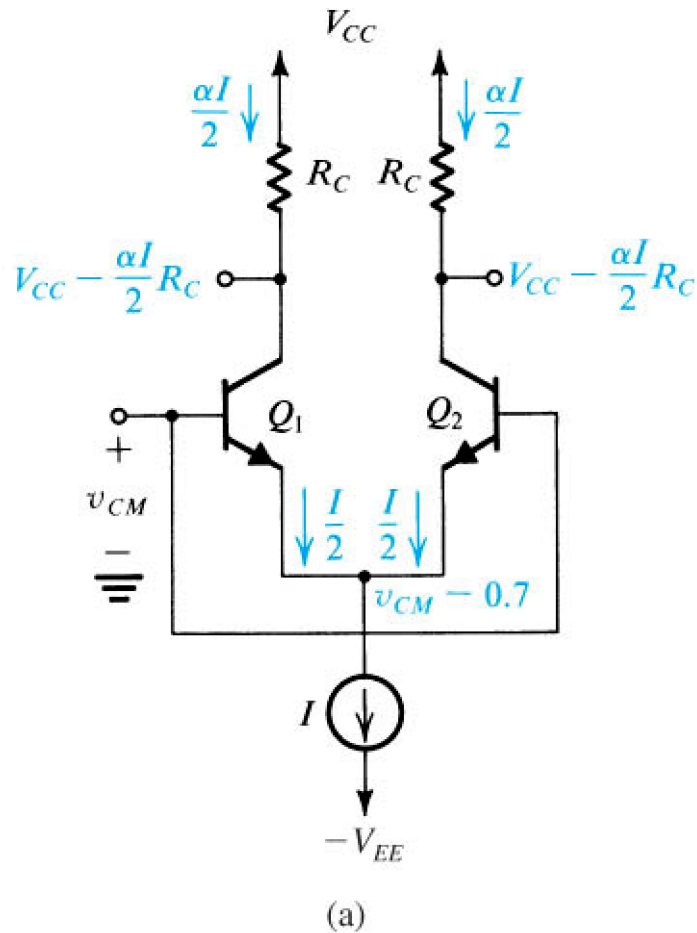- ▶ Q1 positive going, Q2 negative going signal
- ▶ Hence there will be negative going output at the collector of Q1 and positive going output at the collector of Q2
- ▶ So the difference between two voltages V_o is the twice as large as the signal voltage.



➤ Common Mode Operation

➤ The differential pair with a common-mode input signal v_{CM} .

➤ Two transistors are matched.

➤ Current is divided equally between two transistors.

➤ The difference in voltage between the two collector is zero.

Configurations of Differential Amplifier

- ▶ Dual input , balanced output
- ▶ Dual input, unbalanced output
- ▶ Single input, balanced output
- ▶ Single input, unbalanced output

Note:

- ▶ If output is taken between two collectors – balanced output
- ▶ If output is taken between one collector with respect to ground then it is unbalanced output

D.C Analysis of Differential Amplifier

Applying KVL to base-emitter loop,

$$-I_B R_S - V_{BE} - 2I_E R_E + V_{EE} = 0 \quad \text{-----(1)}$$

But, $I_C = \beta I_B$ and $I_C \approx I_E$

Therefore, $I_B = I_E / \beta$ -----(2)

(2) In (1) we get,

$$\begin{aligned} [-I_E R_S / \beta] - V_{BE} - 2I_E R_E + V_{EE} &= 0 \\ I_E [(-R_S / \beta) - 2R_E] + V_{EE} - V_{BE} &= 0 \end{aligned} \quad \text{-----(3)}$$

Therefore

$$I_E = \frac{V_{EE} - V_{BE}}{\left(\frac{R_S}{\beta}\right) - 2R_E} \quad \text{-----(4)}$$

In practical,

$R_S / 2R_E$, hence $I_E = [V_{EE} - V_{BE}] / 2R_E$ -----(5)

► The collector voltage of Q1

$$V_c = V_{CC} - I_c R_c \quad \text{-----(5)}$$

And $V_{CE} = V_c - V_E = (V_{CC} - I_c R_c) - (-V_{BE})$

$$V_{CE} = V_{CC} + V_{BE} - I_c R_c \quad \text{-----(6)}$$

For the differential amplifier,


The operating point values

$$V_{CEQ} \approx V_{CE}$$

And


$$I_{CQ} \approx I_E$$

Differential Amplifier with active load

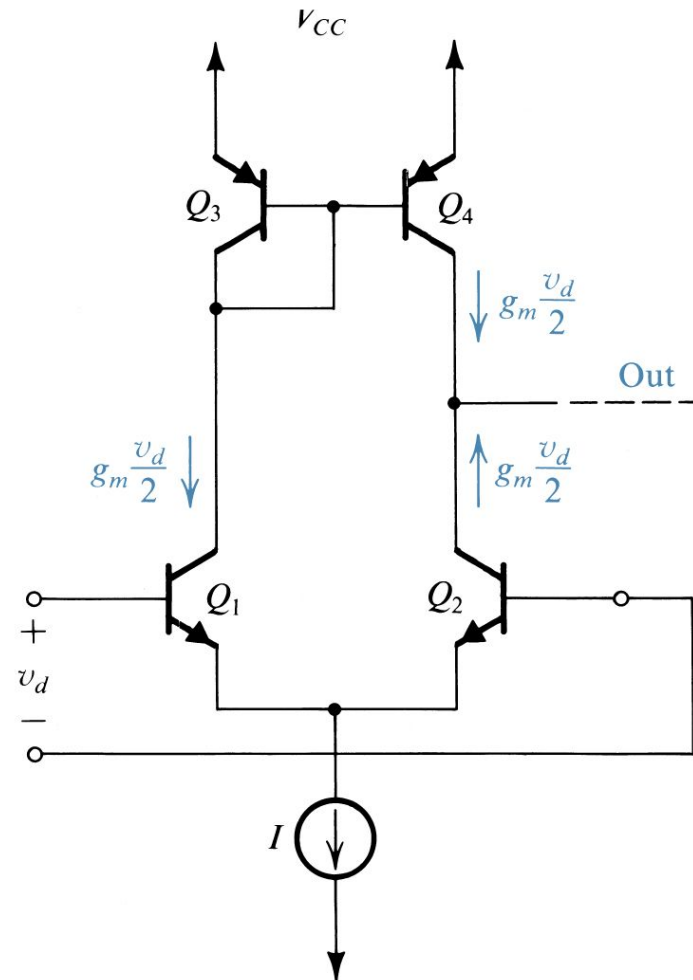


Current Mirror Circuit

 - ▶ A current mirror is a circuit designed to copy a current through one active device by controlling the current in another active device of a circuit, keeping the output current constant regardless of loading



Multiple current mirror

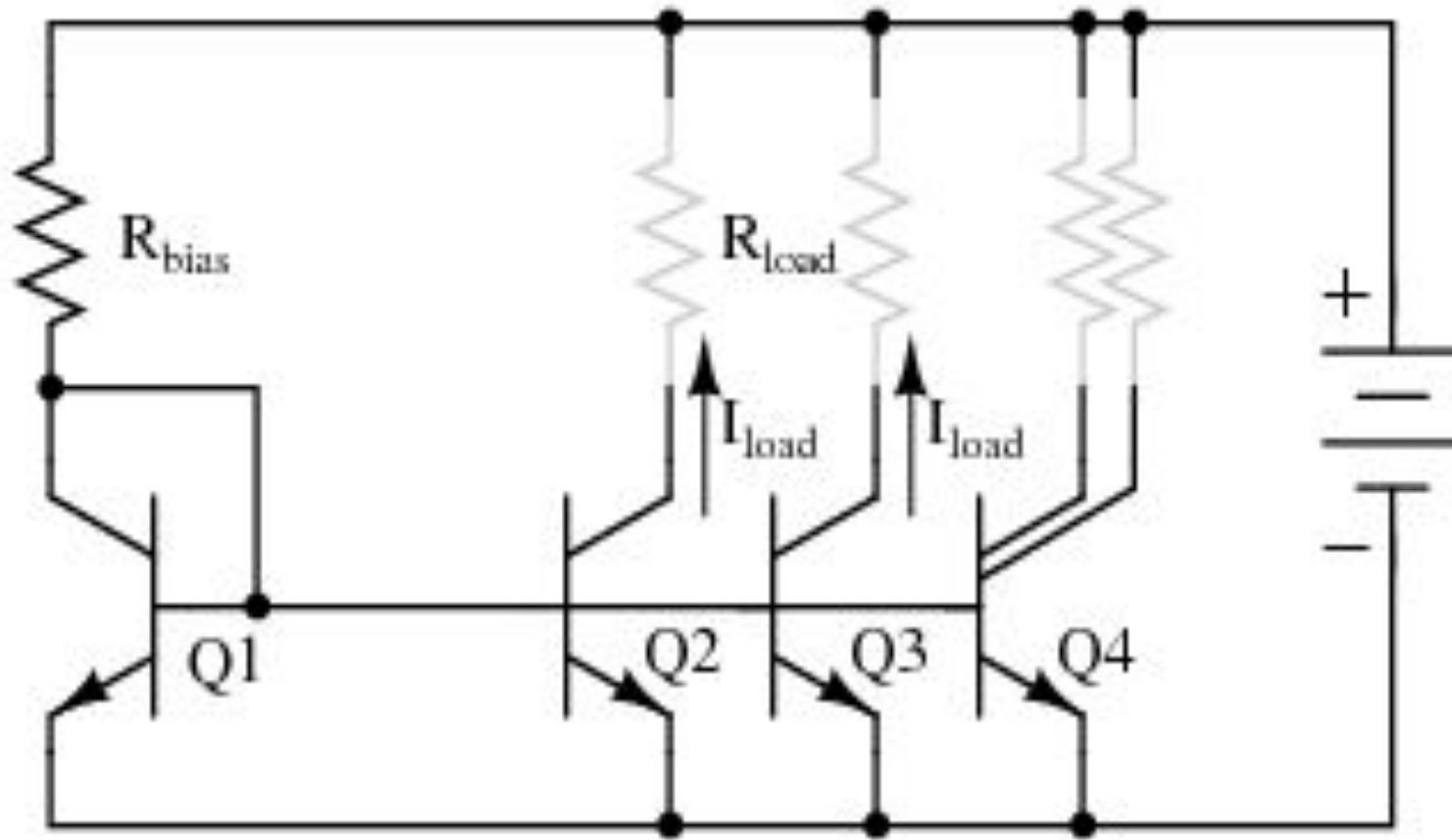


The Wilson current source

An improved circuit, called Wilson current source, with higher output impedance than the previous current mirror.

For the Wilson current source, the following
 
$$I_{ref} = \frac{V_{CC} - V_{BE2} - V_{BE3}}{R}$$
$$I_{C2} \approx \frac{A_3}{A_1} I_{ref}$$




The Widlar current source

When the desired current is small, the Widlar current source may be a better alternative, as shown in the Figure.

For Widlar current source,

 
$$R_2 \approx \frac{V_T}{I_{C2}} \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$
$$I_{C1} \approx I_{ref} = \frac{V_{CC} - V_{BE1}}{R_1}$$



The combined current sources

In an Integrated Circuit amplifier, several current sources use the same reference current, as shown below.

 The current through R_1 is the reference current for all four current sources. Q_1, Q_2 forms a current mirror, and Q_1, Q_3 forms a Widlar source. Notice the pnp current source by Q_4, Q_5 and Q_6 .



Voltage Reference Circuits

- ▶ Used to provide a constant d.c voltage, which acts as a reference for other circuits
- It is independent of changes in the parameters like temperature, input line voltage and load current
- Accuracy and stability with temperature are the basic characteristics of any voltage reference circuit
- Temperature coefficient TC = $\Delta V_o / \Delta T$ in mV/°C
- % of temperature coefficient

$$\%TC = 100 \left[\frac{\Delta V_o / V_o}{\Delta T} \right] \text{ in } \%/^{\circ}\text{C}$$

Performance parameters of Voltage reference circuits

- **Line regulation** (Input/Supply regulation)

$$\text{Line Regulation} = \frac{\Delta v_o}{\Delta v_i}$$

- **Load regulation**

$$\text{Load Regulation} = \frac{\Delta v_o}{\Delta I_L}$$

- **Long term stability**

The ability of circuit to maintain the output voltage constant with respect to time

- **Ripple Rejection Ratio (RRR)**

$$\text{RRR} = 20 \log \frac{v_{ri}}{v_{ro}}$$

Problems

- ▶ Design an amplifier with a gain of -10 and input resistance equal to $10\text{K}\Omega$
- ▶ For an op-amp with $R_1=10\text{K}\Omega$ and $R_2=100\text{K}\Omega$ is given $v_i=1\text{V}$. A load $25\text{K}\Omega$ is connected to the terminal. Calculate i_1, V_o, i_L and total current i_o into the output pin.
- ▶ Design an amplifier with a gain of $+5$ using op-amp.
- ▶ For an op-amp circuit, $R_1=5\text{k}\Omega$ and $R_f=20\text{k}\Omega$ with $v_i=1\text{V}$. A load resistor of $5\text{k}\Omega$ is connected at the output. Calculate V_o, A_{CL}, i_L and i_o .