

UNIT-1

Linear waveshaping

High pass & Low pass RC circuits and their responses for sinusoidal, step, pulse, square, ramp and exponential inputs. High pass RC circuit as differentiator. Low pass RC circuit as integrator, Attenuators. RL and RLC circuits and their response for step input. Ringing circuit.

Linear network:-

The passive elements such as resistor, inductor and capacitor are linear, since the current through them is proportional to the voltage.

ie, there is a linear relationship between the applied voltage and the resulting current.

A network consisting of these linear elements is called as linear network.

Wave shaping:-

"It is the process of changing the shape of input signal with linear/non-linear circuits".

Uses

- 1) Converting one waveform to another.
- 2) To clip the positive (or) negative amplitude of the waveform.
- 3) To hold the waveform to a certain d.c level.


Types

- 1) Linear wave shaping.
- 2) Non-linear wave shaping.

Linear waveshaping :-

When a sinusoidal signal is applied to a transmission network consisting of linear elements, the output signal will be a true replica of the input signal except a change in amplitude & phase angle.

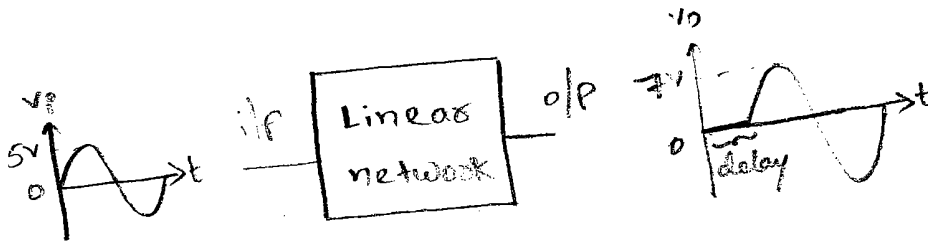So, the feature of preserving waveshape in all linear network, the sinusoidal signal is unique.




∴ "The process whereby the form of a non-sinusoidal signal is altered by transmission through a linear network is called Linear wave shaping."

The most important non-sinusoidal waveforms are step, pulse, square wave, ramp and exponential waveforms.

Step:

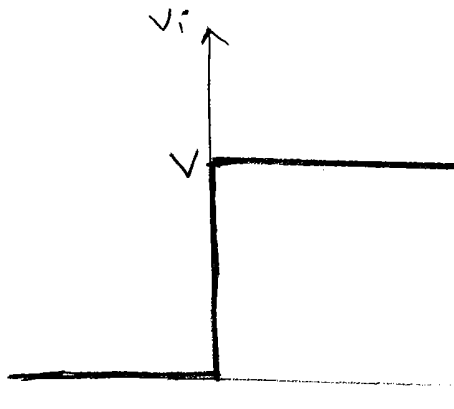A step voltage is one which maintains the value zero for all times $t < 0$ and maintains the value V for all times $t > 0$.




$$V_i = 0, t < 0$$

$$V_i = V, t > 0$$

voltage increases from 0 to max, $t = 0$

Pulse:

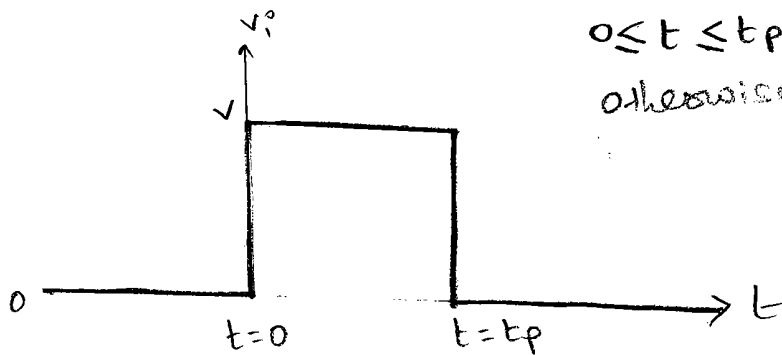An ideal pulse waveform is shown below. The pulse amplitude is ' V ' and the pulse duration is t_p .




$$0 \leq t \leq t_p, V_i = V$$

$$\text{otherwise, } V_i = 0$$


Square wave:

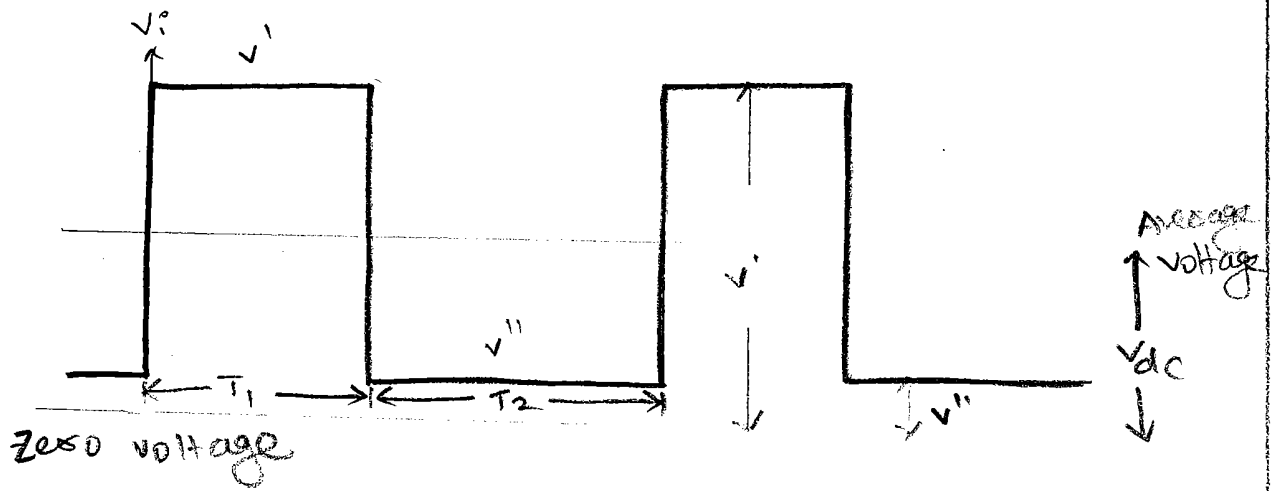A waveform which maintains itself at one constant level V' for a time T_1 and at other constant level V'' for a time T_2 and which is repetitive with a period of $T = T_1 + T_2$ is called a square wave.



Ramp:

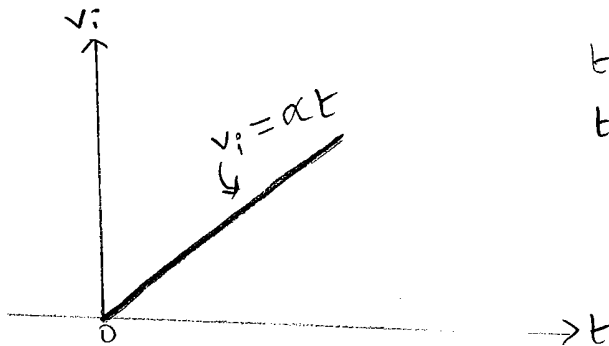A waveform which is zero for $t < 0$ and which increases linearly with time for $t > 0$ is called ramp.



$$t < 0, V_i = 0$$

$t > 0$, V_i increases linearly with time

$$V_i = \alpha t$$


$$\alpha = \frac{V_i}{t}$$

Exponential signal:

The exponential input waveform is given by


$$V_o = V(1 - e^{-t/\tau})$$

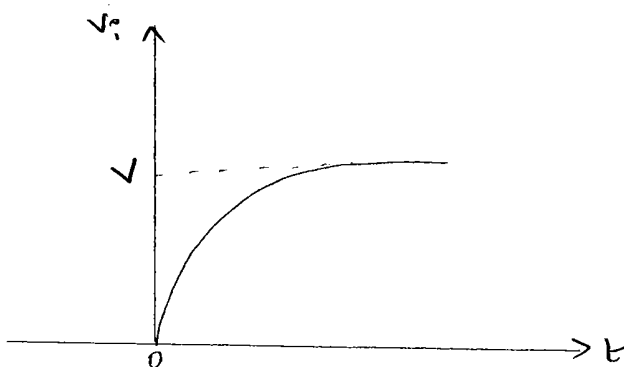where τ = time constant of the exponential input



High-pass RC circuit

The High-pass RC circuit is shown below.

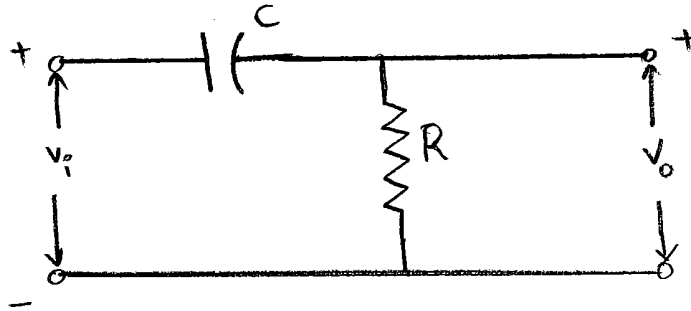

We know $X_C = \frac{1}{2\pi fC}$

"Voltage across a capacitor cannot reduce to zero instantaneously."

The reactance of the capacitor decreases with increasing frequency.

→ At higher frequencies, the capacitive reactance decreases and capacitor acts almost as a short circuit.

∴ "The higher frequency components in the input signal appear at the output with less attenuation. Due to this behaviour, the circuit is called as High pass filter."


→ At zero frequencies, the capacitor has infinite reactance and hence behaves as an open circuit.
i.e; if any D.C is present in the input voltage that is blocked by the capacitor.

∴ capacitor C is called as blocking capacitor.

- High pass RC circuit is also called as Differentiator or DC isolation circuit.

① Sinusoidal input:

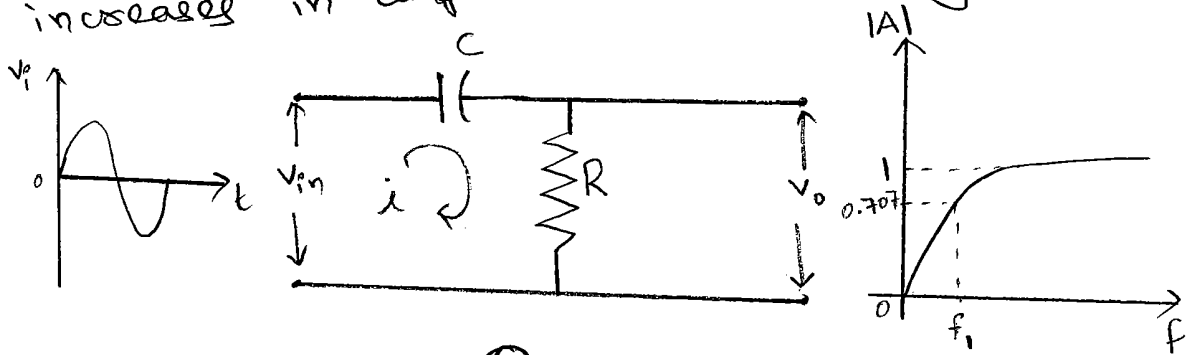For a sinusoidal input V_{in} , the output signal V_o increases in amplitude with increasing frequency.



$$V_o = iR \quad \text{--- ①}$$

$$\text{but } i = \frac{V_{in}}{R + \frac{1}{j\omega C}} = \frac{V_{in}}{R + \frac{j}{2\pi f C}}$$

$$\text{but } i = \frac{V_{in}}{R + jX_C} = \frac{V_{in}}{R + \frac{j}{2\pi f C}} = \frac{V_{in}}{R \left[1 + \frac{j}{2\pi f R C} \right]} \quad \text{--- ②}$$

Sub eqn ② in eqn ①

$$V_o = \frac{V_{in}}{R \left[1 + \frac{j}{2\pi f R C} \right]} \times R = \frac{V_{in}}{1 + \frac{j}{2\pi f R C}}$$

$$\text{Let } f_1 = \frac{1}{2\pi R C}$$

$$V_o = \frac{V_{in}}{1 + j \frac{f_1}{f}}$$

$$A = \frac{V_o}{V_{in}} = \frac{1}{1 + j \left(\frac{f_1}{f} \right)}$$

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}}$$

$$\theta = +\tan^{-1}\left(\frac{f_1}{f}\right)$$

at $f = f_1$, the magnitude of capacitive reactance is equal to the resistance

$$\text{i.e.; } X_C = R$$

$$|A| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\therefore |A| = 0.707$$

$$\theta = \tan^{-1} 1 = 45^\circ$$

$$\therefore \theta = 45^\circ$$



→ the gain $|A| = 0.707$ indicates signal reduction of 3 decibels (3dB).

$\therefore f_1$ is called Lower 3-dB frequency.

→ The maximum possible value of the gain is unity at high frequencies.

② Step input:

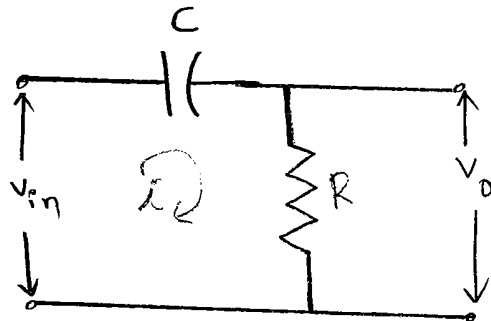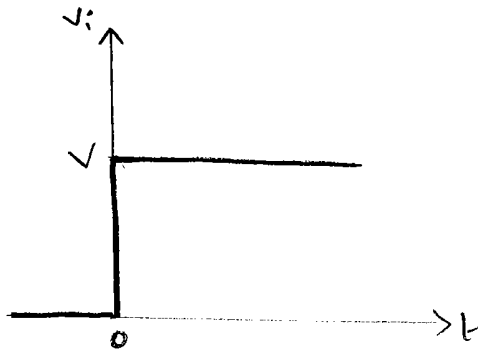A step voltage is one which maintains the value zero for all times $t < 0$ and maintains the value V for all times $t > 0$.



The transition between the two voltages takes place at $t = 0$.

$V_o = 0$ immediately before $t = 0$
[to be referred as $t = 0^-$]

$V_o = V$ immediately after $t = 0$
[to be referred as $t = 0^+$]

Apply KVL to the input side

$$V_i = \frac{1}{C} \int i dt + R i$$

but $V_o = i R \Rightarrow i = \frac{V_o}{R}$

$$V_i = \frac{1}{C} \int \frac{V_o}{R} dt + V_o \quad \text{--- (1)}$$

Differentiate eqn (1) with respect to time

$$\frac{dV_i}{dt} = \frac{V_o}{RC} + \frac{dV_o}{dt}$$

$$\boxed{\frac{dV_i}{dt} = \left(\frac{1}{RC}\right)V_0 + \frac{dV_0}{dt}} \quad \text{--- (2)}$$

$\downarrow$ $\downarrow$
 steady state transient
 response response

Since $V_i = V$ (constant) at $t = 0^+$

$$\frac{dV_i}{dt} = \frac{dV}{dt} = 0$$

$$\therefore \frac{1}{RC}V_0 + \frac{dV_0}{dt} = 0$$

The general solution is

$V_0 = \text{complementary function} + \text{particular integral.}$

i) complementary function

$$\frac{dV_i}{dt} = \frac{V_0}{RC} + \frac{dV_0}{dt}$$

$$\text{let } \frac{d}{dt} = D$$

$$DV_0 + \frac{V_0}{RC} = DV_i$$

$$V_0 \left[D + \frac{1}{RC} \right] = DV_i \quad \text{--- (3)}$$

L.H.S R.H.S

to find Complementary function take L.H.S

$$V_0 \left[D + \frac{1}{RC} \right]$$

$$D = -\frac{1}{RC} = \phi,$$

$$C.F = K e^{+\phi t} = \underline{K e^{-t/RC}}$$

ii) Particular integral

to find P.I take R.H.S of eqn ③

$$DV_i$$

$$\Rightarrow \frac{d}{dt} V_i$$

input is a step which is constant

$$\therefore \frac{d}{dt} V = 0$$

$$\underline{\underline{P.I = 0}}$$

$$V_o = C.F + P.I$$

$$V_o = K e^{-t/RC} + 0$$

$$V_o = K e^{-t/RC} \quad \text{--- (4)}$$

To find the value of K, we have to apply initial conditions.


At $t=0$, capacitor acts as short circuit.

$$V_o = K e^{-0/RC}$$

$$V_o = K, \text{ but } V_o(0^+) = V \therefore K = V$$

Substitute K value in eqn (4)

$$\boxed{V_o = V e^{-t/RC}}$$

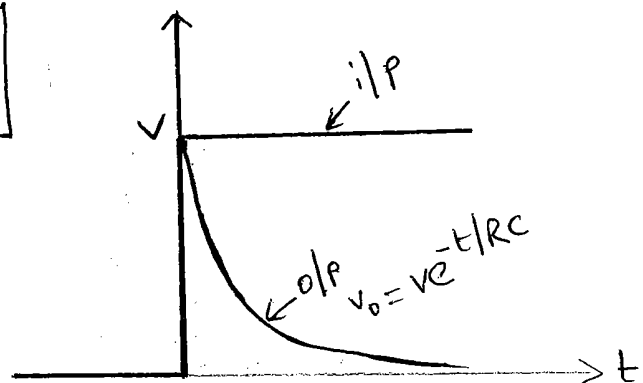

$$V_0 = V e^{-t/RC}$$

i) At $t = RC$

$$V_0 = V e^{-RC/RC} = 0.3678V$$

ii) At $t = 2RC$


$$V_0 = V e^{-2RC/RC} = 0.135V$$

iii) At $t = 3RC$

$$V_0 = V e^{-3RC/RC} = 0.049V$$

iv) At $t = 5RC$



$$V_0 = V e^{-5RC/RC} = 0.007V$$

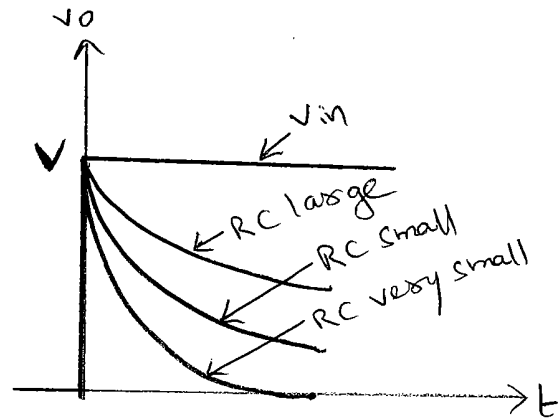

∴ The output voltage V_0 becomes practically Zero after 5 time-constants.

③ pulse input :

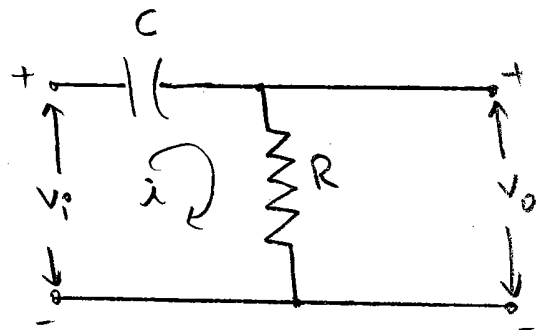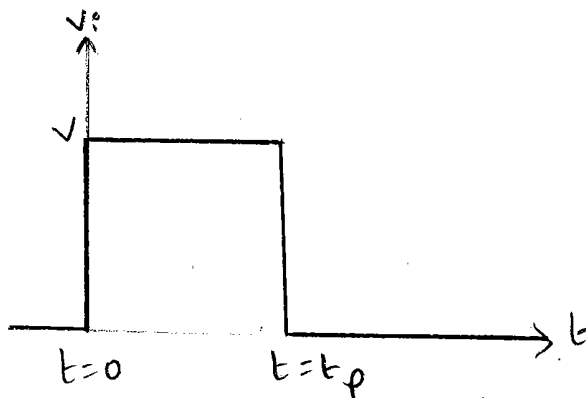An ideal pulse waveform is shown below. The pulse amplitude is V and pulse duration is t_p .







→ pulse may be considered to be the sum of a step voltage $+V$ volts starting at $t=0$ and a step voltage $-V$ volts starting at $t=t_p$.

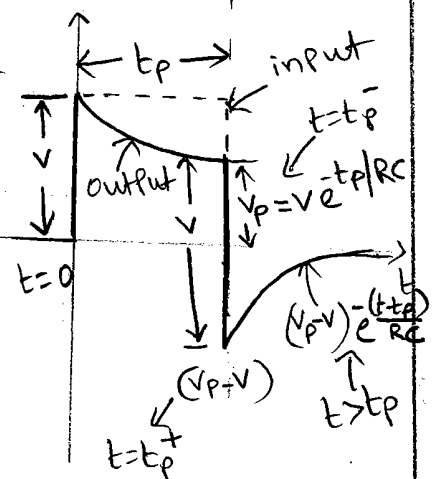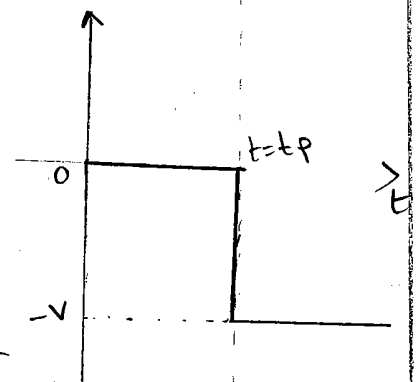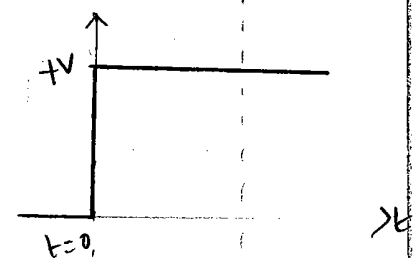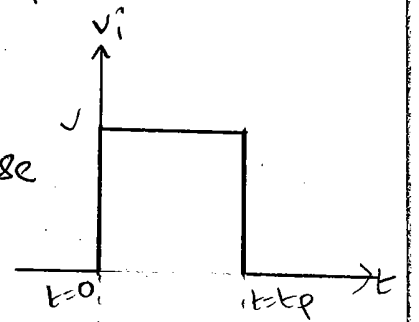i) If the pulse is applied to the High pass RC circuit, the response for time $t < t_p$ is same as the step voltage input.

Hence the output at $t=t_p^-$ is given by

$$V_p = V_0 = V e^{-t_p/RC} \quad \text{--- (1)}$$



ii) At the end of the pulse, the input falls abruptly by the amount V . For this sudden change the capacitor acts as short circuit and this change will appear at the output (the voltage across the capacitor cannot change instantaneously) so, the output also decreases by the same amount of V volts

At $t=t_p^+$

$$V_0 = V_p - V = V e^{-t_p/RC} - V$$

$$V_0 = V [e^{-t_p/RC} - 1] \quad \text{--- (2)}$$

iii) $t > t_p$

$$V_0 = (V_p - V) e^{-(t-t_p)/RC}$$

$$V_0 = V(e^{-t_p/RC} - 1) e^{-(t-t_p)/RC} \quad \text{--- (3)}$$

$\therefore$ for $t > t_p$, the output rises exponentially towards zero with a time constant RC .

The response of High-pass RC circuit to a pulse
if $RC \gg t_p$ and $RC \ll t_p$

→ Passing a pulse through an RC coupling network which results distortion in the output.

There is a tilt to the top of the pulse and an undershoot at the end of the pulse. These distortions are to be minimized, if the time constant RC must be very large as compared to the pulse width t_p .

→ If RC is greater means the time taken by the capacitor to charge is more and also the time taken by the capacitor to discharge is more.

→ However for all the values of ratio $\frac{RC}{t_p}$ the area below the axis will always equal to the area above.


→ For High pass RC circuit the input and output are separated by the blocking capacitor C . So the d.c (or) average level of the output signal is zero for this linear circuit.

i) $RC \ll t_p$ i.e., $\frac{RC}{t_p} \ll 1$

If the time constant is very small, the output consists of a positive spike of amplitude V volts at the beginning of the pulse and a negative spike of the same size at the end of the pulse.

"The process of converting pulses into spikes by means of a circuit of short time constant is called peaking."

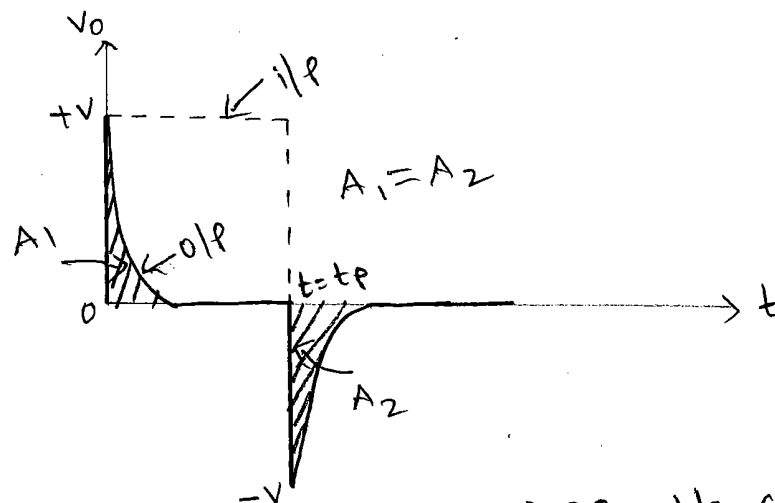"So, the High pass circuit with a very small time constant is called peaking circuit."




The output waveform bears no resemblance to the input waveform. Smaller the time constant, larger the distortion.

and vice versa.

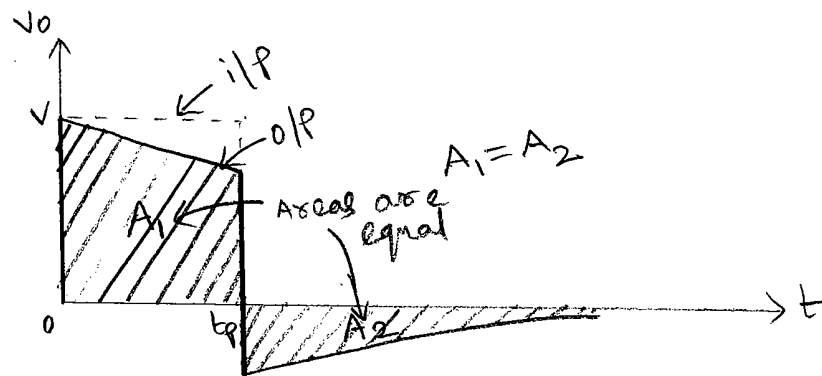ii) $R_C \gg t_p$ (or) $\frac{R_C}{t_p} \gg 1$


If the time constant is very large, there is only a slight tilt to the output pulse and the undershoot is very small, but for $t > t_p$, the output rises towards zero very slowly. Since its area must equal that of the positive portion,



∴ In order to minimize distortion, it is clear that the time-constant of the circuit must be very large as compared to the pulse width.

④ Square wave input:

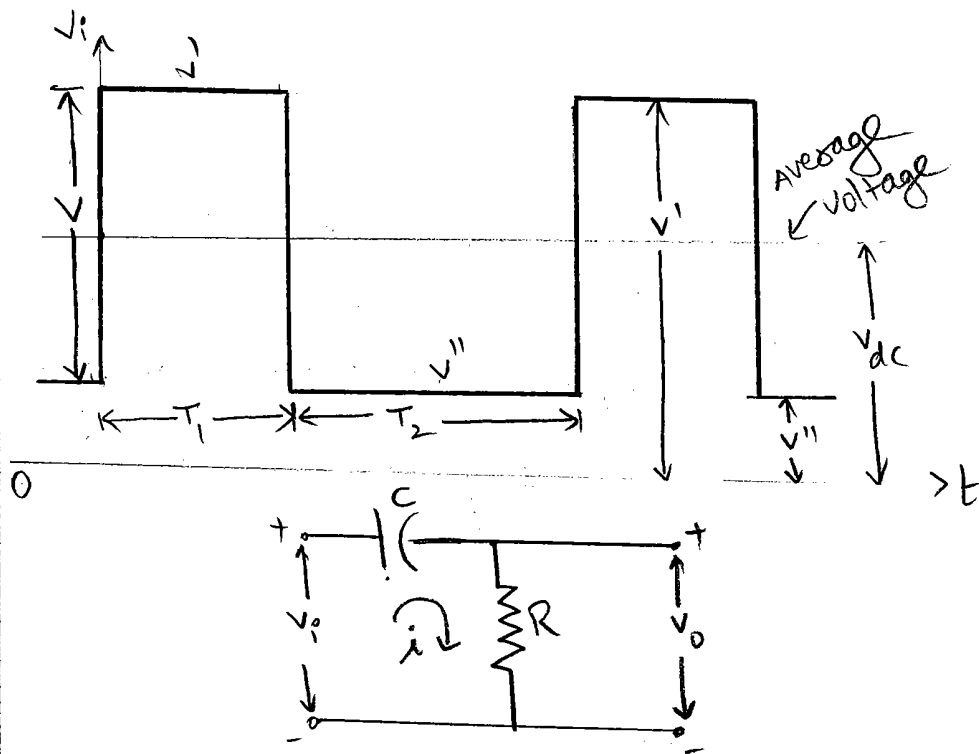A square wave is a periodic waveform which maintains itself at one constant level V' for a time T_1 and at another constant level V'' for a time T_2 and which is repetitive with a period $T = T_1 + T_2$.



Proof:-

By writing KVL at the input side

$$V_i = \frac{1}{C} \int i dt + iR$$

$$\text{but } V_o = iR, \quad i = \frac{V_o}{R}$$

$$V_i = \frac{1}{C} \int i dt + V_o$$

$$V_i = \frac{1}{C} \int \frac{V_o}{R} dt + V_o$$

Differentiating the above equation with respect to 't' we get

$$\frac{dV_i}{dt} = \frac{1}{C} \times \frac{V_o}{R} + \frac{dV_o}{dt}$$

$$\frac{dV_i}{dt} = \frac{V_o}{RC} + \frac{dV_o}{dt}$$

Multiplying by dt and integrating this equation over one period T we get

$$\int_0^T \frac{dv_i}{dt} \times dt = \int_0^T \frac{v_o}{RC} dt + \int_0^T \frac{dv_o}{dt} \times dt$$

$$\int_0^T dv_i = \frac{1}{RC} \int_0^T v_o dt + \int_0^T dv_o$$

$$v_i(T) - v_i(0) = \frac{1}{RC} \int_0^T v_o dt + v_o(T) - v_o(0)$$

Under steady state conditions, the output waveform (as well as input waveform) is repetitive with a period T .

So

$$v_o(T) = v_o(0) \text{ and}$$

$$v_i(T) = v_i(0)$$

$$\therefore v_i(T) - v_i(0) = \frac{1}{RC} \int_0^T v_o dt + v_o(T) - v_o(0)$$


$$0 = \frac{1}{RC} \int_0^T v_o dt$$

$$\boxed{\int_0^T v_o dt = 0}$$

$\therefore$ This integral represents the area under the output waveform over one cycle is zero.


The average level (d.c component) of the output is always zero.

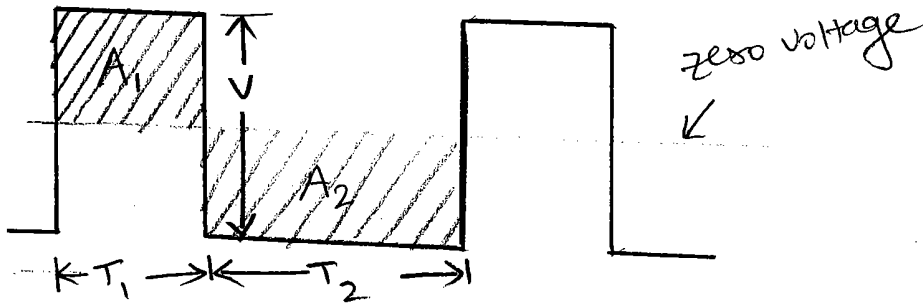i) $RC \gg T \Rightarrow \frac{RC}{T} \gg 1$




when the time constant is arbitrarily large (ie; $\frac{RC}{T_1}$ and $\frac{RC}{T_2}$ are very very large in comparison to unity) the output is same as the input but with zero d.c level.

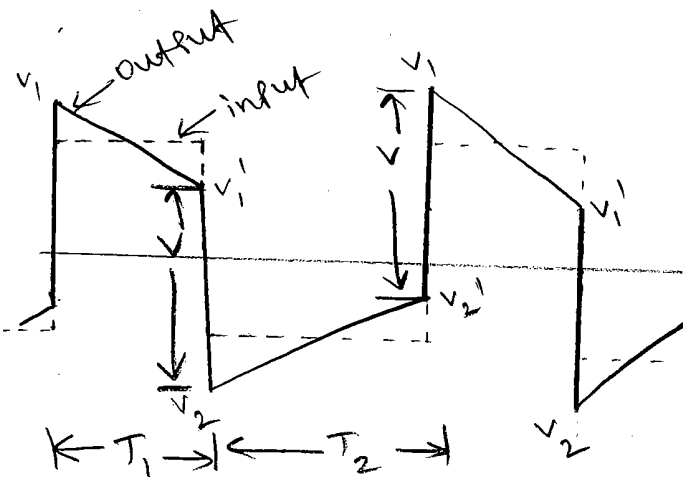ii) $RC > T \Rightarrow \frac{RC}{T} > 1$



In this condition the output is in the form of a tilt.

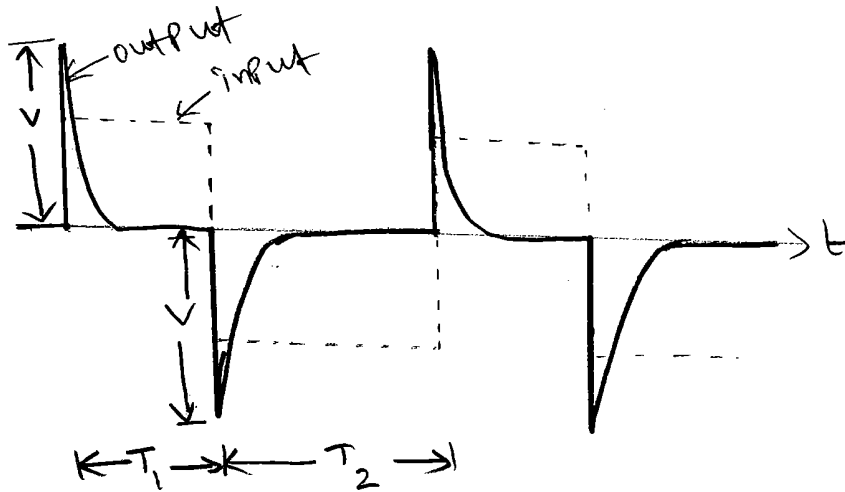
ii) $RC \ll T \Rightarrow \frac{RC}{T} \ll 1$



if $RC \ll T$ (ie; $\frac{RC}{T_1}$ and $\frac{RC}{T_2}$ are very very small in comparison to unity), the output consists of alternate positive and negative spikes.

In this case, the peak-to-peak amplitude of the output waveform is twice the peak-to-peak value of the input waveform.

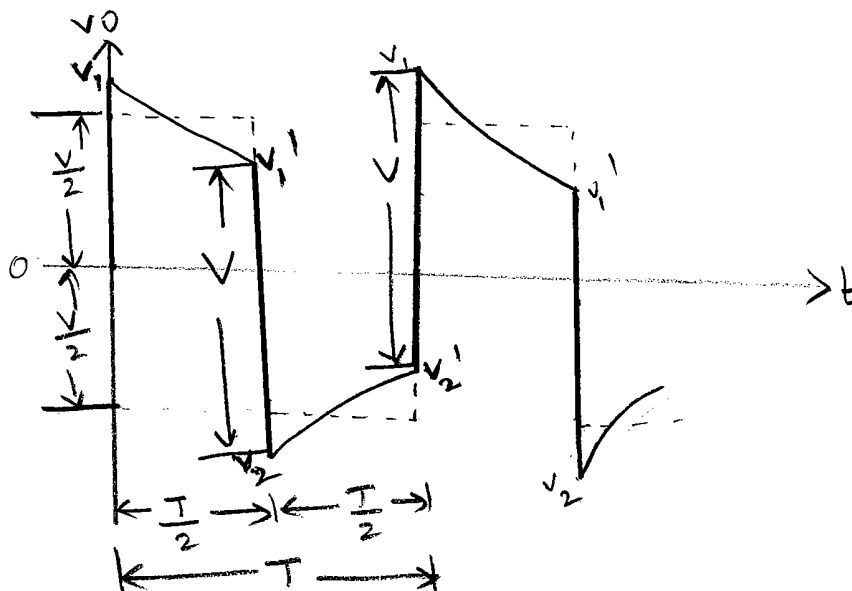Expression for percentage tilt % ($RC > T$)



Consider the steady state response of a High pass RC circuit to a symmetrical square wave input.

"Tilt is defined as the decay in the amplitude of the output voltage wave, due to the input voltage maintaining a constant level."

$$\text{Percentage tilt (P)} = \frac{V_1 - V_1'}{V_1} \times 100$$

i) At $t=0$, $V_0 = V_1$

ii) At $t > 0$, $V_0 = V_1 e^{-t/RC}$

iii) At $t = T/2$, $V_0 = V_1'$

$$V_1' = V_1 e^{-T/2RC} \quad \text{--- (1)}$$

iv) again at $t = T/2$, $V_0 = V_2'$

$$V_2' = V_2 e^{-T/2RC} \quad \text{--- (2)}$$

$$V_1' - V_2 = V \quad \text{--- (3)}$$

$$V_1 - V_2' = V \quad \text{--- (4)}$$

Since input is symmetrical square wave, so

$$T_1 = T_2 = T/2$$

$$V_1 = -V_2$$

$$V_1' = -V_2'$$

Substitute these in eqn (3)

$$V = V_1' - V_2$$

$$V = V_1 e^{-T/2RC} - V_2$$

$$V = V_1 e^{-T/2RC} + V_1$$

$$V = V_1 [1 + e^{-T/2RC}]$$

$$V_1 = \frac{V}{1 + e^{-T/2RC}} \quad \text{--- (I)}$$

sub (I) in eqn (i)

$$V_1' = V_1 e^{-T/2RC}$$

$$V_1' = \frac{V}{1 + e^{-T/2RC}} \times e^{-T/2RC}$$

$$V_1' = \frac{V}{(1 + e^{-T/2RC}) e^{T/2RC}} = \frac{V}{e^{T/2RC} + 1}$$

$$V_1' = \frac{V}{1 + e^{T/2RC}} \quad \text{--- (II)}$$

sub (I) & (II) in percentage tilt

$$P = \frac{V_1 - V_1'}{V/2} \times 100$$

$$P = \frac{\frac{V}{1 + e^{-T/2RC}} - \frac{V}{1 + e^{T/2RC}}}{V/2} \times 100$$

$$P = \left[\frac{1}{1 + e^{-T/2RC}} - \frac{1}{1 + e^{T/2RC}} \right] \times 200$$

$$P = \left[\frac{1}{1 + e^{-T/2RC}} - \frac{e^{-T/2RC}}{1 + e^{-T/2RC}} \right] \times 200$$

$$P = \frac{1 - e^{-T/2RC}}{1 + e^{-T/2RC}} \times 200$$

$$P = \frac{1 - e^{-1/2RCf}}{1 + e^{-1/2RCf}} \times 200$$

$$\begin{aligned} & \frac{e^{-T/2RC}}{1 + e^{-T/2RC}} \\ &= \frac{1}{(1 + e^{-T/2RC})e^{T/2RC}} \\ &= \frac{1}{e^{T/2RC} + e} \\ &= \frac{1}{1 + e^{T/2RC}} \end{aligned}$$

we know $e^{-x} = 1 - \frac{x}{1!} + \frac{x^2}{2!} - \frac{x^3}{3!} + \dots$

$$P = \frac{1 - \left[1 - \frac{T}{2RC} + \frac{\left(\frac{T}{2RC}\right)^2}{2!} - \dots \right]}{1 + \left[1 - \frac{T}{2RC} + \frac{\left(\frac{T}{2RC}\right)^2}{2!} - \dots \right]} \times 200$$

$$P = \frac{\cancel{1} - \cancel{1} + \frac{T}{2RC}}{1 + 1 - \frac{T}{2RC}} \times 200$$

$$P = \frac{\frac{T}{2RC}}{2 - \frac{T}{2RC}} \times 200$$

since $RC > T \Rightarrow \frac{RC}{T} \gg 1 \Rightarrow \frac{T}{RC} < 1$ so $\frac{T}{2RC} < 1$

we can neglect

$$P = \frac{\frac{T}{2RC}}{2} \times \cancel{200}^{100}$$

$$\% \text{ tilt } P = \frac{T}{2RC} \times 100$$

we know $f_1 = \frac{1}{2\pi RC}$

$$2RC = \frac{1}{\pi f_1}$$

$$\% \text{ tilt } P = \frac{T}{1/\pi f_1} \times 100$$



$$= T\pi f_1 \times 100, \text{ since } T = \frac{1}{f}$$

$$\% \text{ tilt } = \frac{\pi f_1}{f} \times 100$$

⑤ Ramp input :

A waveform which is zero for $t < 0$ and which increases linearly with time for $t > 0$.

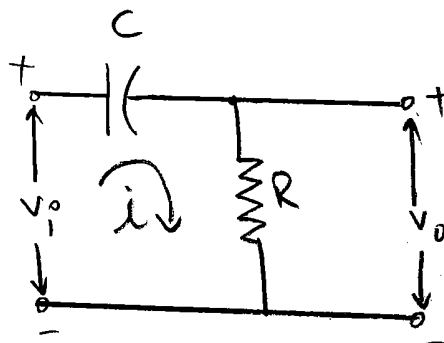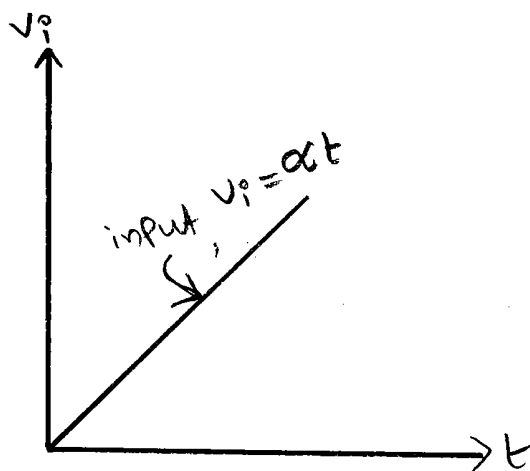$V_i = \alpha t$ is called a ramp or sweep voltage and is shown below:



By applying KVL to the input loop

$$V_i = \frac{1}{C} \int i dt + iR$$

$$V_o = iR$$

$$i = \frac{V_o}{R}$$

$$V_i = \frac{1}{C} \int \frac{V_o}{R} dt + V_o$$

differentiate with respect to time

$$\frac{dV_i}{dt} = \frac{V_o}{RC} + \frac{dV_o}{dt}$$

$$V_i = \alpha t$$

$$\frac{dV_i}{dt} = \alpha$$

$$\therefore \boxed{\alpha = \frac{V_o}{RC} + \frac{dV_o}{dt}}$$

$$\alpha = V_o \left[\frac{1}{RC} + \frac{d}{dt} \right], \quad \text{but } \frac{d}{dt} = D$$

$$\left(D + \frac{1}{RC} \right) V_o = \alpha$$

The solution of above Differential equation is

$$\text{formula: } V_o(I.f) = \int \frac{dV_o}{dt} \times I.f dt$$

$\text{where } \underset{\substack{\uparrow \\ \text{Integral function}}}{I.f} = e^{\int \frac{1}{RC} dt} = e^{\frac{t}{RC}}$

$$V_0 e^{t/RC} = \int \alpha e^{t/RC} dt + K$$

since $V_i = \alpha t$

$$\frac{dV_i}{dt} = \alpha$$

$$V_0 = \frac{\alpha e^{t/RC}}{1/RC} + K$$

$$= \frac{\alpha e^{t/RC}}{1/RC} \cdot e^{-t/RC} + K e^{-t/RC}$$

$$V_0 = \alpha RC + K e^{-t/RC}$$

To find K value apply initial conditions

at $t=0$, $V_0 = 0$

$$0 = \alpha RC + K e^{-0}$$

$$\therefore K = -\alpha RC$$

$$V_0 = \alpha RC - \alpha RC e^{-t/RC}$$

$$V_0 = \alpha RC [1 - e^{-t/RC}]$$

i) If $RC \gg t$

$$V_0 = \alpha RC [1 - e^{-t/RC}]$$

$$e^{-x} = 1 - \frac{x}{1!} + \frac{x^2}{2!} - \frac{x^3}{3!} + \dots$$


$$V_0 = \alpha RC \left[1 - \left(1 - \frac{t}{RC} + \frac{\left(\frac{t}{RC}\right)^2}{2!} - \dots \right) \right]$$

$$= \alpha RC \left[\cancel{1} - \cancel{1} + \frac{t}{RC} - \frac{t^2}{2RC^2} \right]$$

$$= \alpha \cancel{RC} \left[\frac{t}{\cancel{RC}} - \frac{t^2}{2\cancel{RC}^2} \right]$$

$$= \alpha \left[t - \frac{t^2}{2RC} \right]$$
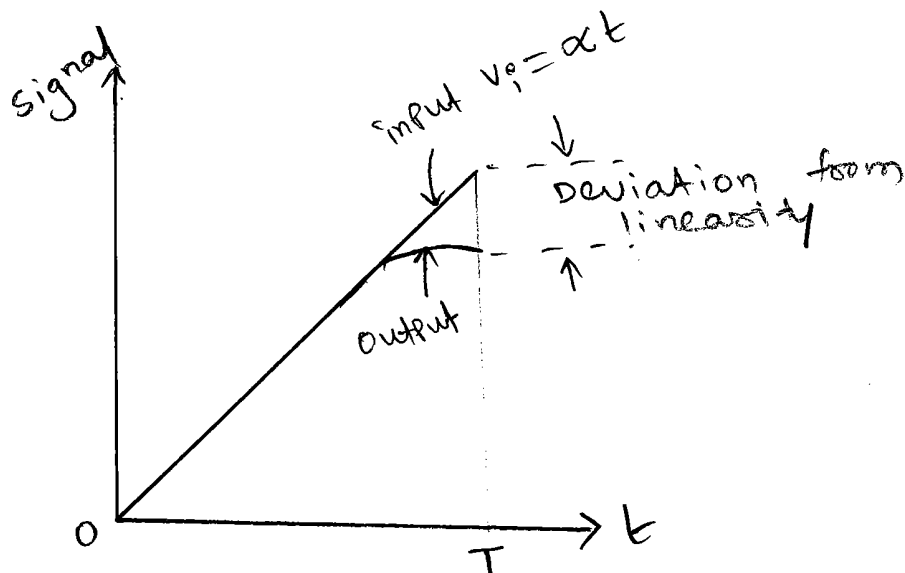
$$V_0 = \alpha t \left[1 - \frac{t}{2RC} \right]$$




i) If $RC \ll t$

$$V_o = \alpha RC (1 - e^{-t/RC})$$

$$V_o = \alpha RC (1 - 0)$$

$$\therefore \boxed{V_o = \alpha RC}$$

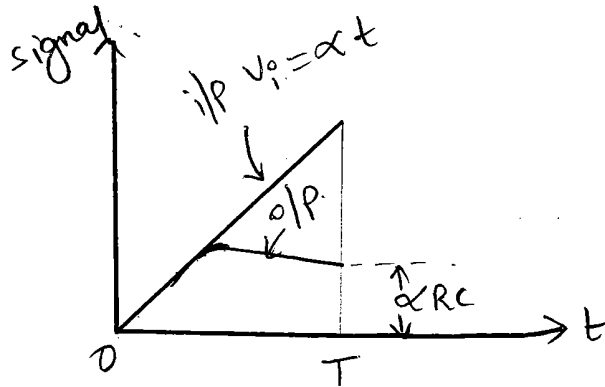

Transmission error (e_t):

for $RC \gg T$, the output signal falls away slightly from the input.

"A measure of the departure from linearity, expressed as the transmission error (e_t) is defined as the difference between input and output divided by the input."

The error at time $t = T$ is given by

$$e_t = \frac{V_i - V_o}{V_i} = \frac{\alpha T - \alpha T(1 - \frac{T}{2RC})}{\alpha T}$$

$$e_t = \frac{\alpha T \left[1 - 1 + \frac{T}{2RC} \right]}{\alpha T}$$

$$e_t = \frac{T}{2RC}$$



we know $f_1 = \frac{1}{2\pi RC}$

$$2RC = \frac{1}{\pi f_1}$$

$$e_t = \frac{T}{1/\pi f_1} = T\pi f_1$$

$$e_t = \frac{\pi f_1}{f}$$

⑥ Exponential signal:

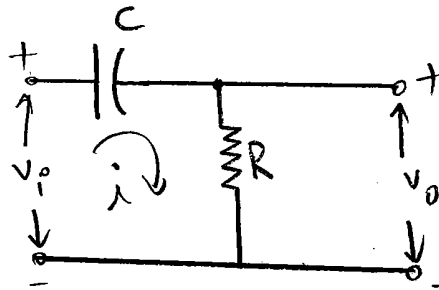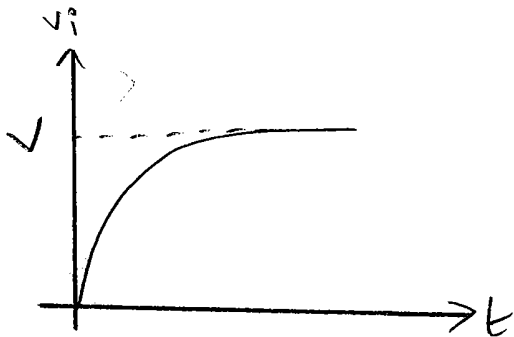

→ For all non-sinusoidal inputs like step, ramp, square, pulse, the output voltage is exponential in nature. In particular, for a ramp input, the output voltage is exponentially rising and its waveform practically coincides with the input waveform near $t=0$.

→ If the forcing function (particular integral) also an exponentially rising voltage, then the output and input waveforms are coincident at and near

$t=0$. The peak value of the output is decided by the time constant of the circuit.

→ Smaller the time constant, smaller is the output peak.

As $\tau(RC)$ increases in comparison with the time required for the input voltage to attain its steady state value, the output peak also increases. However the output voltage decays exponentially to zero after attaining peak value.

The exponential input waveform is given by

$$V_i = V [1 - e^{-t/\tau}] \quad \text{--- (1)}$$

where τ = Time constant of the exponential input.

Apply KVL at the input and output loops

$$V_i = \frac{1}{C} \int i dt + iR$$

$$V_o = iR$$

$$i = \frac{V_o}{R}$$

$$V_i = \frac{1}{C} \int \frac{V_o}{R} dt + V_o$$

Differentiating with respect to 't'

$$\frac{dV_i}{dt} = \frac{V_o}{RC} + \frac{dV_o}{dt} \quad \text{--- (2)}$$

$$v_i = v [1 - e^{-t/\tau}] = v - v e^{-t/\tau}$$

$$\frac{dv_i}{dt} = 0 - \frac{v e^{-t/\tau}}{\tau} \times \frac{-1}{\tau} =$$

$$\frac{dv_i}{dt} = \frac{v}{\tau} e^{-t/\tau}$$

$$\frac{v}{\tau} e^{-t/\tau} = \frac{v_0}{RC} + \frac{dv_0}{dt}$$

$$\frac{v}{\tau} e^{-t/\tau} = v_0 \left[\frac{1}{RC} + \frac{d}{dt} \right], \text{ but } \frac{d}{dt} = D$$

$$\left(D + \frac{1}{RC} \right) v_0 = \frac{v}{\tau} e^{-t/\tau} \Rightarrow \left(D + \frac{1}{RC} \right) v_0 = k$$

The solution of the differential equation with constant k is given by

$$\text{formula: } v_0 \times (I.f) = \int \frac{dv_i}{dt} \times I.f \, dt + C$$

R.H.S
 $\int \frac{1}{RC} dt \quad t/RC$
 $= e$

where $I.f = e$

$$v_0 \cdot e^{t/RC} = \int \frac{v}{\tau} e^{-t/\tau} \cdot e^{t/RC} dt + C$$

$$v_0 \cdot e^{t/RC} = \frac{v}{\tau} \int e^{t(\frac{1}{RC} - \frac{1}{\tau})} dt + C$$

$$v_0 = \frac{v}{\tau} \int e^{t(\frac{1}{RC} - \frac{1}{\tau})} dt + C$$

$$v_0 = \frac{v}{\tau} e^{-t/RC} \int e^{t(\frac{1}{RC} - \frac{1}{\tau})} dt + e^{-t/RC} \cdot C \quad \text{--- (3)}$$

i) If $\eta \neq RC$ ($\eta \neq 1$) $\Rightarrow \frac{RC}{\eta} \neq 1$

then the solution of eqn (3) is

$$V_0 = \frac{V}{\eta} e^{-t/RC} \cdot \frac{e^{t/RC} \cdot e^{-t/\eta}}{\frac{(\eta - RC)}{RC\eta}} + c \cdot e^{-t/RC}$$

$$V_0 = \frac{VRC}{(\eta - RC)} \cdot e^{-t/\eta} + c \cdot e^{-t/RC}$$

to find the value of c , apply initial conditions

At $t=0$, $V_0 = 0$

$$0 = \frac{VRC}{\eta - RC} e^{-0} + c \cdot e^{-0}$$

$$c = -\frac{VRC}{\eta - RC}$$

$$V_0 = \frac{VRC}{\eta - RC} e^{-t/\eta} - \frac{VRC}{\eta - RC} e^{-t/RC}$$

$$V_0 = \frac{VRC}{\eta - RC} \left\{ e^{-t/\eta} - e^{-t/RC} \right\}$$

let $x = \frac{t}{\eta}$, $\eta = \frac{RC}{\eta}$, $\frac{x}{\eta} = \frac{t}{RC}$

$$V_0 = \frac{VRC}{\eta(1 - \frac{RC}{\eta})} \left\{ e^{-x} - e^{-x/\eta} \right\}$$

$$V_0 = \frac{V \cdot \eta}{1 - \eta} \left\{ e^{-x} - e^{-x/\eta} \right\}$$

$$\therefore V_0 = \frac{V \cdot \eta}{(n-1)} \left\{ e^{-x/\eta} - e^{-x} \right\}$$

$$\text{ii) } \tau = RC \ (n=1) \Rightarrow \frac{RC}{\eta} = 1$$

Substitute this condition in eqn (3)

$$V_0 = \frac{V}{\eta} e^{-t/RC} \int e^{(\frac{1}{RC} - \frac{1}{\eta})t} dt + e^{-t/RC} \cdot C$$

$$V_0 = \frac{V}{\eta} e^{-t/RC} \int e^{(\frac{1}{RC} - \frac{1}{RC})t} dt + e^{-t/RC} \cdot C$$

$$V_0 = \frac{V}{\eta} e^{-t/RC} \int dt + e^{-t/RC} \cdot C$$

$$V_0 = \frac{Vt}{\eta} e^{-t/RC} + C \cdot e^{-t/RC}$$

To find the value of C , apply initial conditions
at $t=0$, $V_0=0$

$$0 = \frac{V \cdot 0}{\eta} e^{-0} + C \cdot e^{-0}$$


$$C = 0$$

$$V_0 = \frac{Vt}{\eta} e^{-t/RC}$$

$$\text{if } x = \frac{t}{\eta}, \quad n = \frac{RC}{\eta}, \quad \frac{x}{n} = \frac{t}{RC}$$

$$V_0 = V \cdot x e^{-t/\eta}$$

$$V_0 = V \cdot x e^{-x}$$

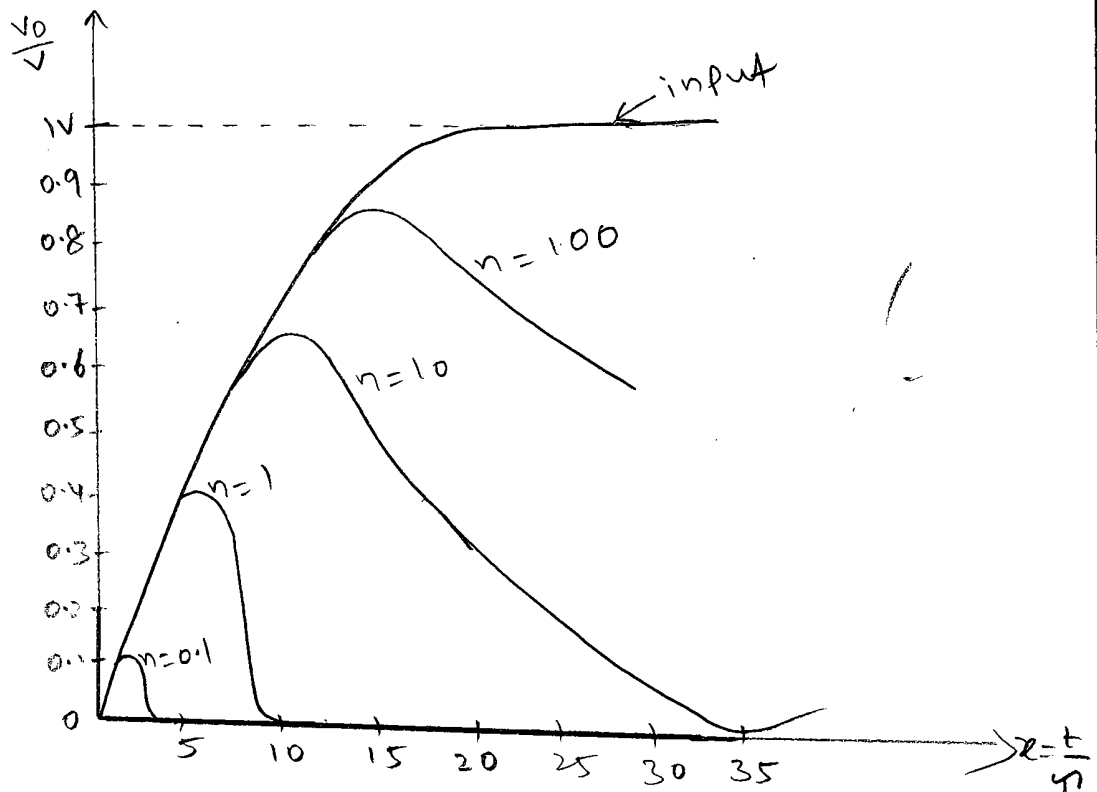

High Pass RC Circuit acts as differentiator.

"If the time constant ($\tau = RC$) is very small in comparison with the time (T) required for the input signal to make an appreciable change, the circuit is called a differentiator."

Under these circumstances the voltage drop across R will be very small in comparison with the drop across C . So, the current is determined entirely by the capacitance.

Then the current i is

$$i = C \frac{dv_o}{dt}$$

output voltage across R is

$$V_o = i R$$

$$V_o = RC \frac{dV_i}{dt}$$

hence the output is proportional to the derivative of the input.

(or)

$$\frac{dV_i}{dt} = \frac{1}{RC} V_o + \frac{dV_o}{dt}$$



$\downarrow$
 steady state response (forced response)

$\downarrow$
 transient response (natural response)

for $RC \ll T$, transient response becomes insignificant

$$\frac{dV_i}{dt} = \frac{1}{RC} V_o + 0$$
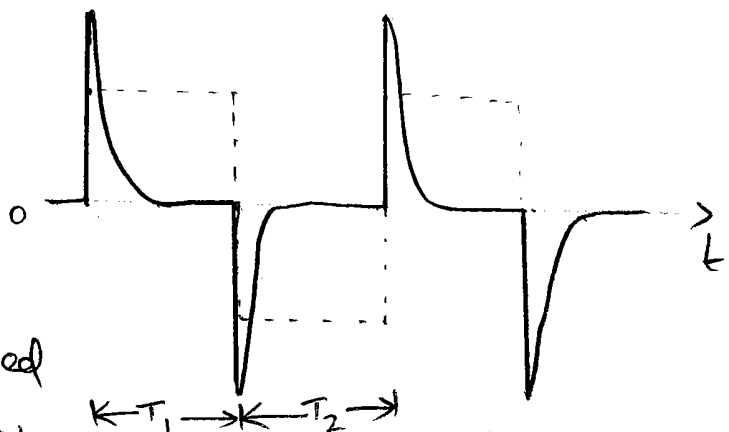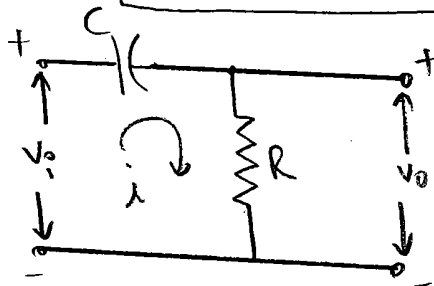
$$V_o = RC \frac{dV_i}{dt} \Rightarrow V_o \propto \frac{dV_i}{dt}$$



If a Ramp input is applied to a differentiator circuit

$$RC \ll T$$

$$V_o = RC \frac{dV_{in}}{dt}$$

$$V_o = \alpha RC$$

$$V_{in} = \alpha t$$

$$\frac{dV_{in}}{dt} = \alpha$$

→ so, the condition for High-pass RC circuit to act as differentiator is

$$RC \ll T$$

→ If a sine wave is applied to the high pass RC circuit, the output will be a sine wave shifted by a leading angle ϕ such that

$$\tan \phi = \frac{1}{\omega RC} = \frac{f_1}{f}$$

and the output will be proportional to $\sin(\omega t + \phi)$.
In order to have true differentiation we must obtain $\cos \omega t$.

i.e.; ϕ must be equal to 90°

This result can be obtained only if $R=0$ or $C=0$.

if $\omega RC = 0.1$ then $\phi = 84.3^\circ$

if $\omega RC = 0.01$ then $\phi = 89.4^\circ$ which is close to 90°

If the peak value of the input is V_m , then the output is

$$\frac{V_m R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \sin(\omega t + \phi)$$


and if $\omega RC \ll 1$, then the output is approximately equal to $V_m \omega RC \cos \omega t$.

This result agrees with the expected value,
 $RC \frac{dV_{in}}{dt}$.

∴ The condition for differentiation is $RC \ll T$.

Low pass RC circuit

Low pass RC circuit is shown below:

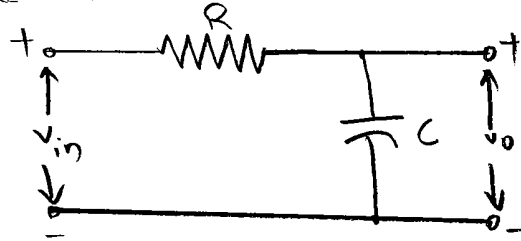

"A Low pass RC circuit is a circuit which transmits only low-frequency signals and attenuates high-frequency signals".

The capacitance reactance is

$$X_C = \frac{1}{2\pi fC}$$

The reactance of capacitor decreases with increasing frequency,

i) At higher frequencies, the reactance becomes small and capacitor almost acts a short circuit.

$$\therefore V_o = 0$$

ii) At low frequencies, the reactance becomes large and capacitor acts as open circuit, and all input appears at the output with less attenuation.

Apply KVL at input and output side

$$V_i = iR + \frac{1}{C} \int i dt$$

$$V_o = \frac{1}{C} \int i dt$$

$$i = C \frac{dV_o}{dt}$$

$$V_i = RC \frac{dV_o}{dt} + V_o$$



Divide throughout by RC

$$\frac{V_i}{RC} = \frac{1}{RC} V_o + \frac{dV_o}{dt}$$

steady state
response
(forced response)

Transient response
(natural response)

① sinusoidal input:

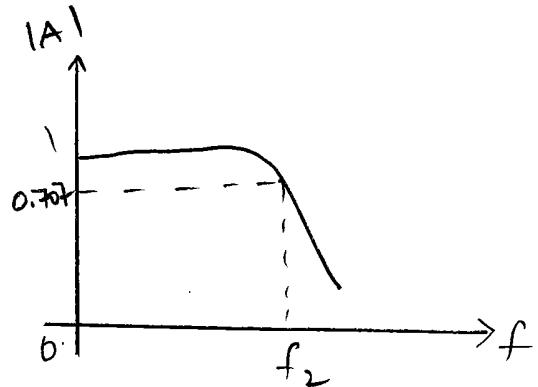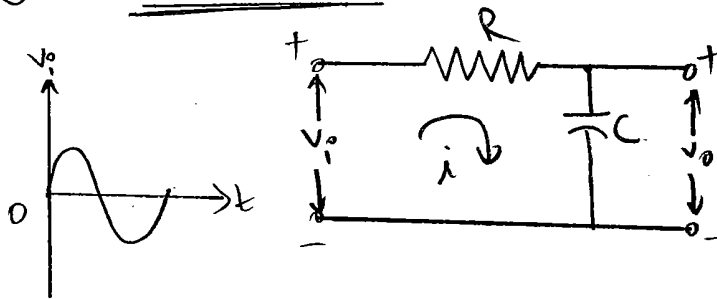

→ At low frequencies, the output is equal to the input and hence the gain is unity.

→ As the frequency increases, the output decreases and hence the gain decreases.

$$V_o = \frac{X_C I}{j}$$

$$I = \frac{V_{in}}{R + \frac{X_C}{j}}, \text{ where}$$

$$V_o = \frac{V_{in} \times \frac{X_C}{j}}{R + \frac{X_C}{j}}, \text{ where } X_C = \frac{1}{2\pi f C}$$

In Laplace transform

$$C \rightarrow \frac{1}{s}$$

$$s = j\omega$$

$$\frac{1}{j\omega C} = \frac{1}{j2\pi f C}$$

$$X_C = \frac{1}{2\pi f C} \Rightarrow \frac{X_C}{j}$$

$$V_o = \frac{V_{in} \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{V_{in} \times \frac{1}{j\omega C}}{\frac{j\omega RC + 1}{j\omega C}}$$

$$V_o = \frac{V_{in}}{1 + j\omega RC} = \frac{V_{in}}{1 + j2\pi f RC}$$

let $f_2 = \frac{1}{2\pi RC}$ = upper 3dB-frequency

$$V_o = \frac{V_{in}}{1 + j \frac{f}{f_2}}$$

$$A = \frac{V_o}{V_{in}} = \frac{1}{1 + j \frac{f}{f_2}}$$

$$|A| = \frac{1}{\sqrt{1 + (f/f_2)^2}}$$

$$\phi = \tan^{-1} \left(\frac{f}{f_2} \right)$$



At $f = f_2$

$$|A| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\phi = \tan^{-1}(1) = 45^\circ$$

② step input :

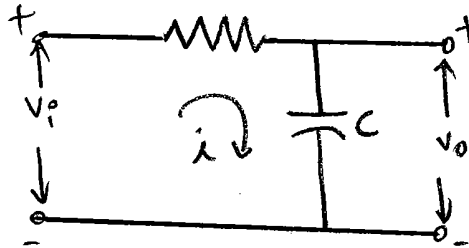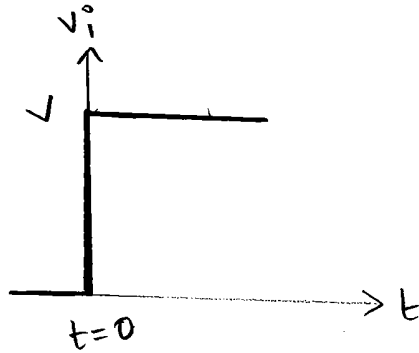A step voltage is one which maintains the value zero for all times $t < 0$ and maintains the value V for all times $t > 0$.



Applying KVL to the input side and output side

$$v_i = iR + \frac{1}{C} \int i dt \quad \text{--- (1)}$$

$$v_o = \frac{1}{C} \int i dt \quad \text{--- (2)}$$

Differentiating equ (1) with respect to t

$$\frac{dv_i}{dt} = R \frac{di}{dt} + \frac{i}{C}$$

$$v_i = V, \quad t \geq 0$$

$$\frac{dv_i}{dt} = 0$$

$$0 = R \frac{di}{dt} + \frac{i}{C}$$

$$\frac{di}{dt} + \frac{i}{RC} = 0$$

$$\left(D + \frac{1}{RC}\right) i = 0, \quad \text{since } \frac{d}{dt} = D$$

By solving above differential equation

$$\text{formula: } i \times (R \cdot f) = \int \frac{dv_i}{dt} \times R \cdot f dt + K$$

$$R \cdot f = e^{\int \frac{1}{RC} dt} = e^{\frac{t}{RC}}$$

$$i \times e^{\frac{t}{RC}} = \int 0 \times e^{\frac{t}{RC}} dt + K$$

$$i = \frac{K}{e^{\frac{t}{RC}}}$$

$$i = K e^{-\frac{t}{RC}}$$

To find K value, we have to apply initial conditions.

At $t=0$, capacitor acts as short circuit and voltage across it is zero

$$\therefore V_{in} = iR$$

$$i = \frac{V_{in}}{R}$$

$$\frac{V_{in}}{R} = K e^{-0}$$

$$K = \frac{V_{in}}{R}$$


$$\therefore i = \frac{V_{in}}{R} e^{-\frac{t}{RC}} \text{ — (3)}$$

$$\text{output voltage } (V_o) = V_i - iR \quad (\text{ie: } V_i = iR + V_o)$$

$$V_o = V - \left(\frac{V}{R} e^{-\frac{t}{RC}} \right) R$$

$$V_0 = V - V e^{-t/RC}$$

$$V_0 = V [1 - e^{-t/RC}]$$

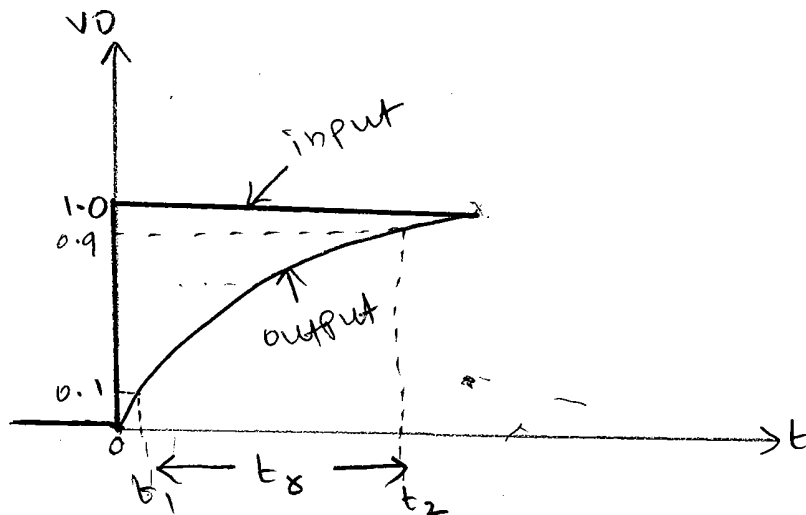

Rise time (t_r) :

"It is defined as the time it takes the voltage to rise from 0.1 to 0.9 of its final value."

Proof :

$$V_0 = V [1 - e^{-t/RC}]$$

$$0.1V = V [1 - e^{-t_1/RC}]$$

$$0.1 = 1 - e^{-t_1/RC}$$

$$e^{-t_1/RC} = 0.9$$

$$t_1 = -RC \ln 0.9 \quad \text{--- (1)}$$

$$0.9V = V [1 - e^{-t_2/RC}]$$

$$0.9 = 1 - e^{-t_2/RC}$$

$$e^{-t_2/RC} = 0.1$$

$$t_2 = -RC \ln 0.1 \quad \text{--- (2)}$$

$$\text{Rise time } (t_r) = t_2 - t_1$$

$$= -RC \ln 0.1 - (-RC \ln 0.9)$$

$$= RC [\ln 0.9 - \ln 0.1]$$

$$t_8 = 2.2RC$$

we know $f_2 = \frac{1}{2\pi RC}$

$$RC = \frac{1}{2\pi f_2}$$

$$t_8 = 2.2 \times \frac{1}{2\pi f_2}$$

$$t_8 = \frac{0.35}{f_2}$$

Thus the rise time is proportional to time constant τ and inversely proportional to upper 3-dB frequency.

Delay time:

"Time required for the output voltage to reach 50% of its final value starts from initial value".

$$V_0 = V[1 - e^{-t/RC}]$$

$$0.5V = V[1 - e^{-t_d/RC}]$$

$$0.5 = 1 - e^{-t_d/RC}$$

$$e^{-t_d/RC} = 0.5$$

$$t_d = -RC \ln 0.5$$

$$t_d = 0.69 RC$$

Time Constant:

Time required for the output voltage to reach 63.2% of its final value starts from initial value.

$$0.632V = V[1 - e^{-t/RC}]$$

$$0.632 = 1 - e^{-t/RC}$$

$$e^{-t/RC} = 1 - 0.632$$



$$e^{-t/RC} = 0.3678$$

$$t = -RC \ln 0.3678$$

$$T = RC$$

③ Pulse input:

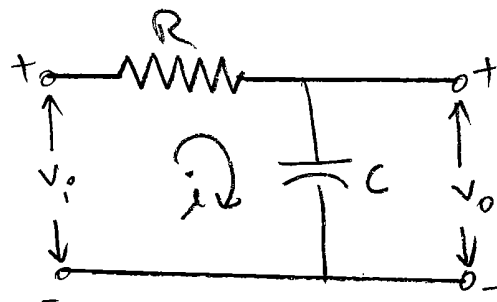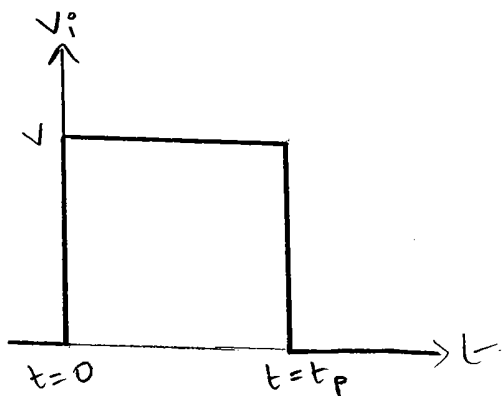An ideal pulse waveform is shown in below fig. The pulse amplitude is V and pulse duration is t_p .




→ Pulse may be considered to be the sum of step voltage $+V$ whose discontinuity occurs at $t=0$ and a step voltage whose discontinuity occurs at $t=t_p$.

→ The response to a pulse, for times less than the pulse width t_p , is same as that for a step input and is given by

$$V_p = V_0 = V [1 - e^{-t/RC}]$$

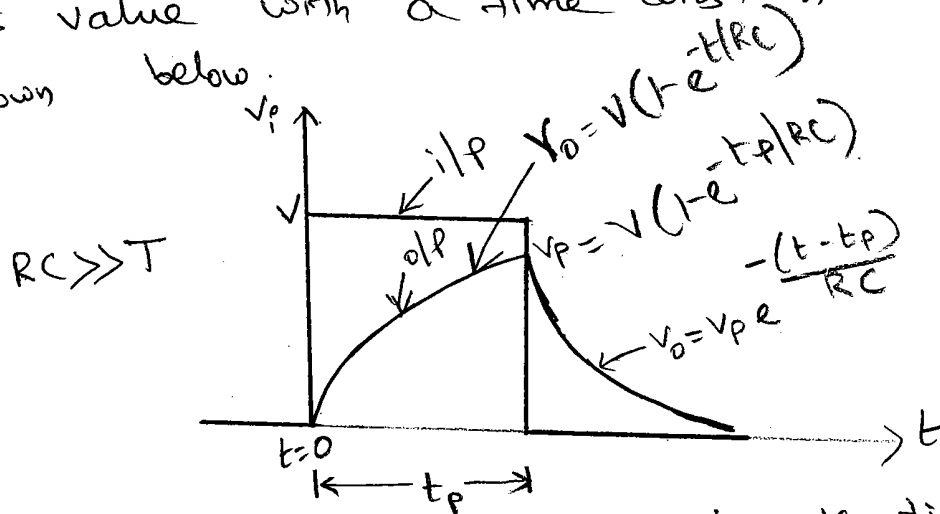→ At the end of the pulse the voltage is V_p and the output must decrease to zero from this value with a time constant RC and is shown below.




→ To minimize the distortion, the rise time must be small compared with the pulse width.

if f_2 is chosen equal to $\frac{1}{t_p}$, then

$$t_r = \frac{0.35}{f_2} = 0.35 t_p$$

the output waveform with $t_r = 0.35 t_p$ is shown

in fig.

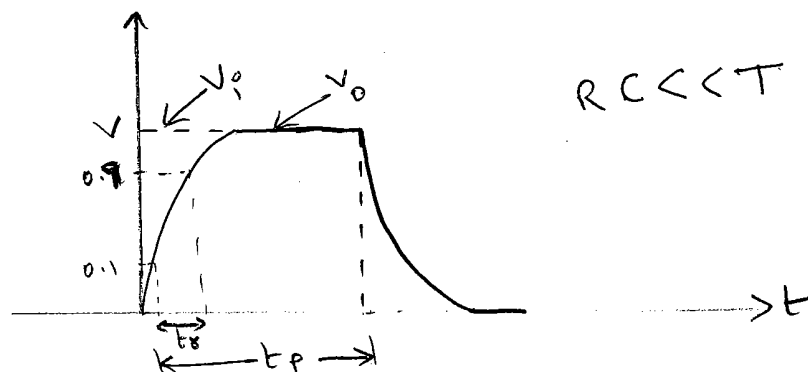

"A pulse shape will be preserved if 3-dB frequency is approximately equal to the reciprocal of the pulse width."


Thus to pass a 0.5 μ sec pulse reasonably will require a circuit with an upper 3-dB frequency of the order of 2 MHz.

④ square wave input:


A square wave is a periodic waveform which maintains itself at one constant level V' with respect to ground for a time T_1 and then changes abruptly to another level V'' and remains constant at that level for a time T_2 and repeats itself at regular intervals of time $T = T_1 + T_2$.

A square wave may be treated as a series of positive and negative steps. The shape of the output waveform for a square wave input depends on time constant of the circuit.

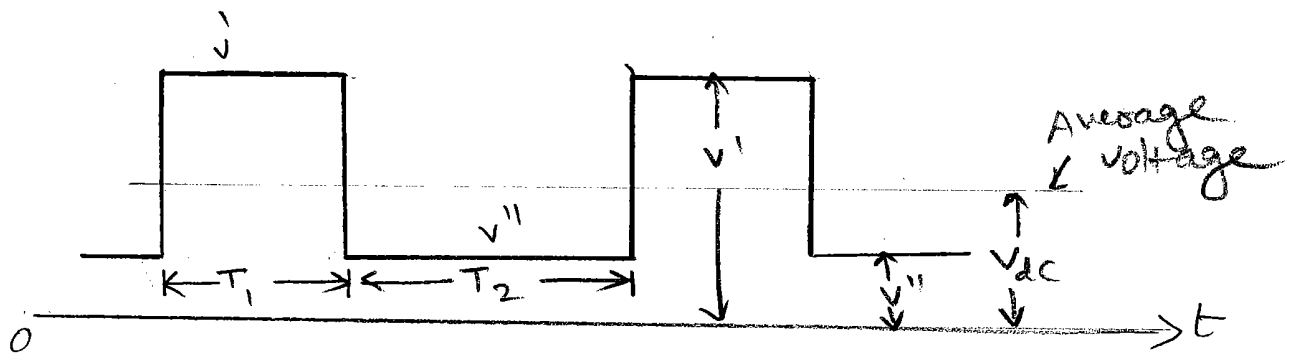
If the time constant is very small, the risetime will also be small and a reasonable reproduction of the input may be obtained.



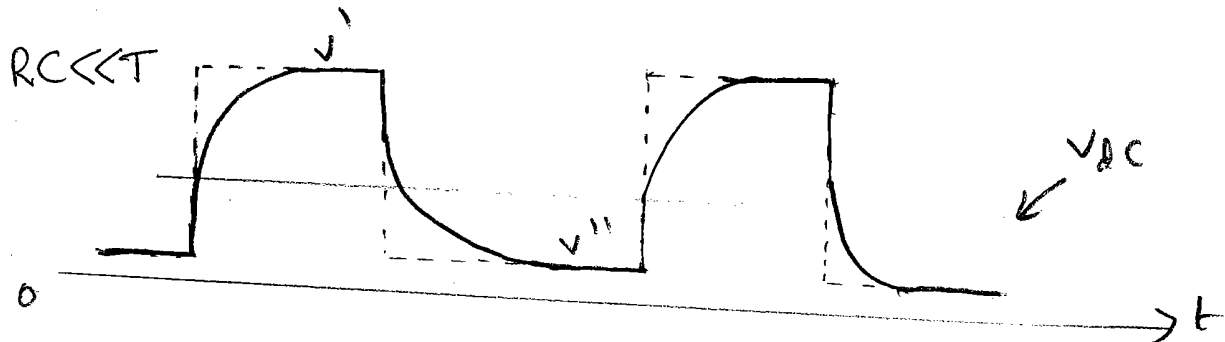
→ if rise time t_r is very small as compared with pulse width, the steady state response is shown below.



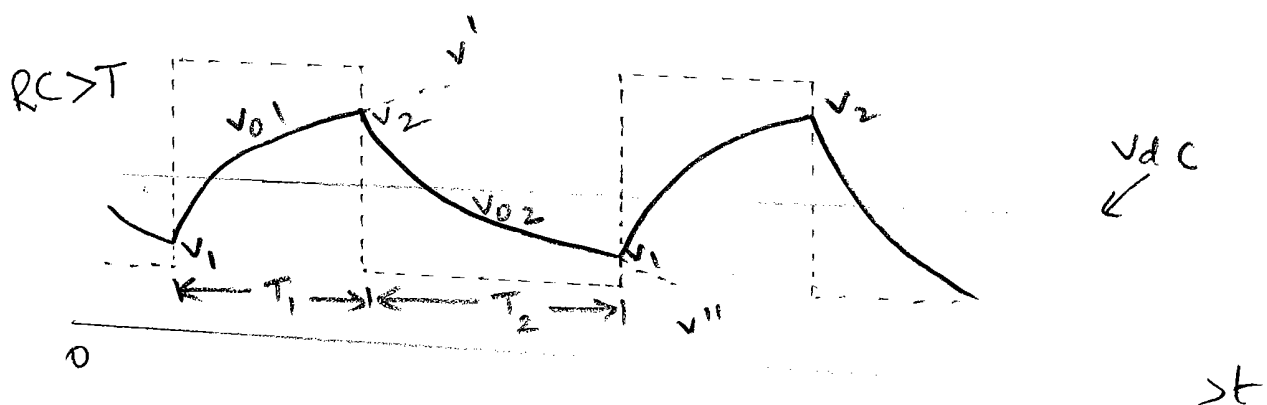→ If the time constant RC is greater or comparable with the period of the input square wave, the output is shown below.



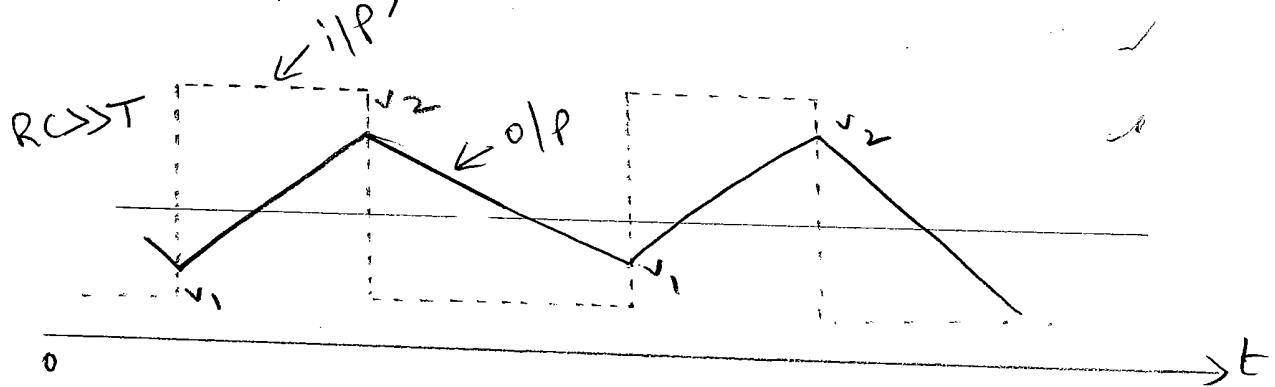→ If the time constant is very large compared with the period of the input, square wave the output consists of exponential sections which are essentially linear.



→ At any instant, to find the output voltage for a single time constant circuit having initial and final values V_i and V_f respectively.

The output voltage is given by

$$V_o = V_f + (V_i - V_f) e^{-t/RC}$$

The output voltage V_{o1} and V_{o2} is given by
for rising position

$$V_{o1} = V' + (V_1 - V') \cdot e^{-T_1/RC} \quad \text{--- (1)}$$

for falling position

$$V_{o2} = V'' + (V_2 - V'') \cdot e^{-T_2/RC} \quad \text{--- (2)}$$

if we set $v_{01} = v_2$ at $t = T_1$

and $v_{02} = v_1$ at $t = T_1 + T_2$

$$v_2 = v' + (v_1 - v') e^{-T_1/RC}$$

$$v_1 = v'' + (v_2 - v'') e^{-T_2/RC}$$

→ Since the average voltage across R is zero, then the d.c voltage at the output is same as that of the input. This average value is indicated as $V_{d.c}$.

Consider a symmetrical square wave with zero average value, so that

$$T_1 = T_2 = \frac{T}{2}$$

$$v' = -v'' = \frac{V}{2}$$

$$\text{and } v_1 = -v_2$$

$$v_2 = \frac{V}{2} + \left(-v_2 - \frac{V}{2}\right) e^{-T/2RC}$$

$$v_2 = \frac{V}{2} - v_2 e^{-T/2RC} - \frac{V}{2} e^{-T/2RC}$$

$$v_2 \left[1 + e^{-T/2RC}\right] = \frac{V}{2} \left[1 - e^{-T/2RC}\right]$$

$$v_2 = \frac{V}{2} \left[\frac{1 - e^{-T/2RC}}{1 + e^{-T/2RC}} \right] = \frac{V}{2} \left[\frac{1 - \frac{1}{e^{T/2RC}}}{1 + \frac{1}{e^{T/2RC}}} \right]$$

$$v_2 = \frac{V}{2} \left[\frac{e^{T/2RC} - 1}{e^{T/2RC} + 1} \right]$$

$$V_2 = \frac{V}{2} \left(\frac{e^{2x} - 1}{e^{2x} + 1} \right), \text{ where } x = \frac{T}{4RC}$$



$$\therefore \boxed{V_2 = \frac{V}{2} \tanh x}$$

where T = Time period of square wave

⑤ Ramp input:

A waveform which is zero for $t < 0$ and which increases linearly with time for $t > 0$.

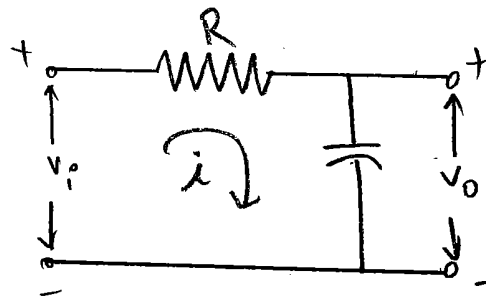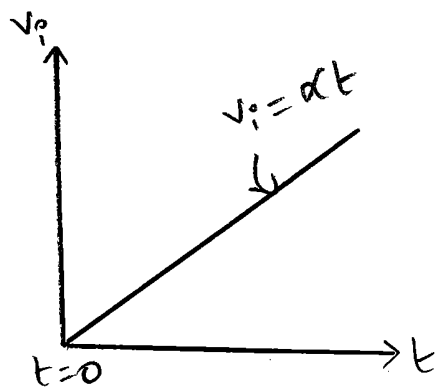$V_i = \alpha t$ is called as ramp input.



Apply KVL to the input loop & output loop

$$V_i = iR + \frac{1}{C} \int i dt$$

$$V_o = \frac{1}{C} \int i dt$$

$$V_i = iR + V_o$$

$$V_o = V_i - iR$$

$$V_o = V_i - V_R$$

From High pass RC circuit, for a ramp input the voltage across resistor R is given by

$$V_R = \alpha RC [1 - e^{-t/RC}]$$

∴ The output voltage across capacitor 'c' for Low pass RC circuit is given by

$$V_0 = V_i - V_R$$

$$V_0 = \alpha t - \alpha RC [1 - e^{-t/RC}]$$

i) If $RC \ll T$, Transients are negligible ($e^{-t/RC} \approx 0$)

$$V_0 = \alpha t - \alpha RC$$

$$\boxed{V_0 = \alpha(t - RC)}$$

ii) If $RC \gg T$, Transients are predominant.

$$V_0 = \alpha t - \alpha RC [1 - e^{-t/RC}]$$

$$e^{-x} = 1 - \frac{x}{1!} + \frac{x^2}{2!} - \frac{x^3}{3!} + \dots$$

$$V_0 = \alpha t - \alpha RC \left[1 - \left(1 - \frac{t}{RC} + \frac{t^2}{2R^2C^2} - \dots \right) \right]$$

$$V_0 = \alpha t - \alpha RC \left[\cancel{1} - \cancel{1} + \frac{t}{RC} - \frac{t^2}{2R^2C^2} \right]$$


$$V_0 = \alpha t - \alpha RC \left[\frac{t}{RC} - \frac{t^2}{2R^2C^2} \right]$$

$$V_0 = \alpha t - \alpha \cancel{RC} \times \frac{t}{\cancel{RC}} + \alpha \cancel{RC} \times \frac{t^2}{2R^2C^2}$$

$$V_0 = \alpha \cancel{t} - \alpha \cancel{t} + \frac{\alpha t^2}{2RC}$$

$$\boxed{V_0 \approx \frac{\alpha t^2}{2RC}}$$

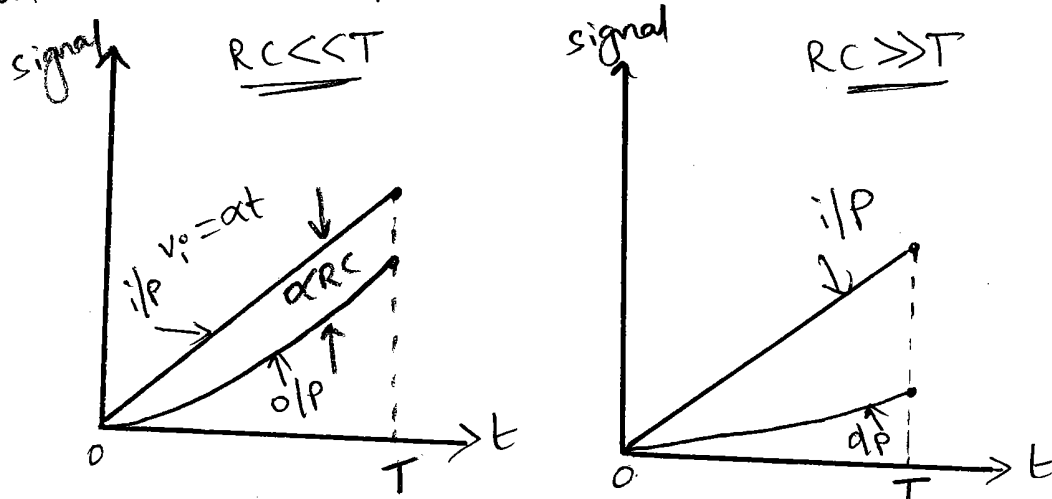The input and output waveforms for a ramp input to a Lowpass RC circuit is shown below.



To transmit the ramp signal with little distortion, a small time constant must be used relative to the total ramp input with time T .

The transmission error e_t is defined as the difference between input and output divided by the input at $t = T$.

for $RC \ll T$

$$e_t = \frac{v_i - v_o}{v_i} \bigg|_{t=T}$$

$$e_t = \frac{\alpha t - (\alpha t - \alpha RC)}{\alpha t} \bigg|_{t=T}$$

$$e_t = \frac{\cancel{\alpha T} - \cancel{\alpha T} + \alpha RC}{\alpha T}$$

$$e_t = \frac{\cancel{\alpha} RC}{\cancel{\alpha} T}$$

$$e_t = \frac{RC}{T}$$

$$f_2 = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_2}$$



$$\therefore \boxed{e_t = \frac{1}{2\pi f_2 T}}$$

where f_2 = upper 3-dB frequency.

⑥ Exponential input :

The exponential input waveform is given by

$$V_i = V [1 - e^{-t/\tau}]$$

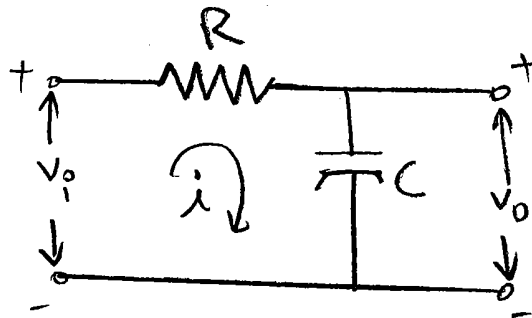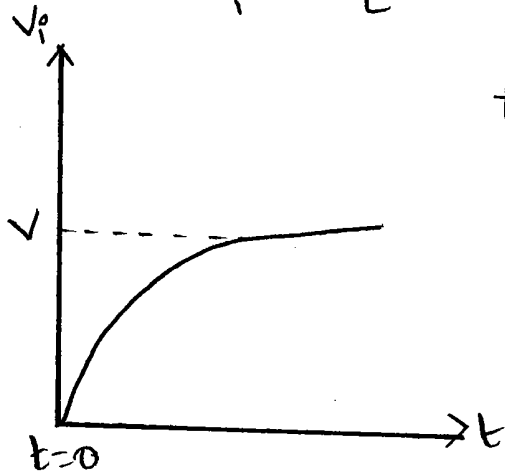

By applying KVL to the input and output loop

$$V_i = iR + \frac{1}{C} \int i dt$$

$$V_o = \frac{1}{C} \int i dt$$

$$V_i = iR + V_o$$

$$V_o = V_i - iR$$

$$V_o = V_i - V_R$$

where V_R = voltage drop across R.

The voltage drop across R in case of High pass RC circuit is

$$\text{for } n=1, \quad V_R = V \cdot x \cdot e^{-x}$$

$$\text{for } n \neq 1, \quad V_R = \frac{V \cdot n}{n-1} \left[e^{-x/n} - e^{-x} \right]$$

∴ The voltage drop across 'C' in case of Low pass RC circuit is

$$V_0 = V_i - V_R$$

$$\text{for } n=1 (RC=\tau)$$

$$V_0 = V_i - V_R$$

$$V_0 = V [1 - e^{-t/RC}] - V x e^{-x}$$

$$V_0 = V - V e^{-t/RC} - V x e^{-x}$$

$$x = \frac{t}{\tau}, \quad n = \frac{RC}{\tau}, \quad \frac{x}{n} = \frac{t}{RC}$$

$$V_0 = V - V e^{-x/n} - V x e^{-x} \quad \left(\text{since } \frac{t}{RC} = \frac{t}{\tau} \right)$$

$$V_0 = V - V e^{-x/n} - V x e^{-x}$$

$$\frac{V_0}{V} = 1 - e^{-x/n} - x e^{-x}$$

$$\frac{V_0}{V} = 1 - e^{-x/n} - x e^{-x}$$

if $n \neq 1$ ($RC \neq \tau$)

$$V_o = V_{in} - V_R$$


$$V_o = V \left[1 - e^{-t/\tau} \right] - \frac{V\tau}{n-1} \left[e^{-x/\tau} - e^{-x} \right]$$

$$V_o = V - V e^{-t/\tau} - \frac{V\tau}{n-1} e^{-x/\tau} + \frac{V\tau}{n-1} e^{-x}$$

$$V_o = V \left[1 - e^{-x} - \frac{\tau}{n-1} e^{-x/\tau} + \frac{\tau}{n-1} e^{-x} \right]$$

$$\frac{V_o}{V} = 1 - e^{-x} - \frac{\tau}{n-1} \cdot e^{-x} (e^{1/\tau} - 1)$$

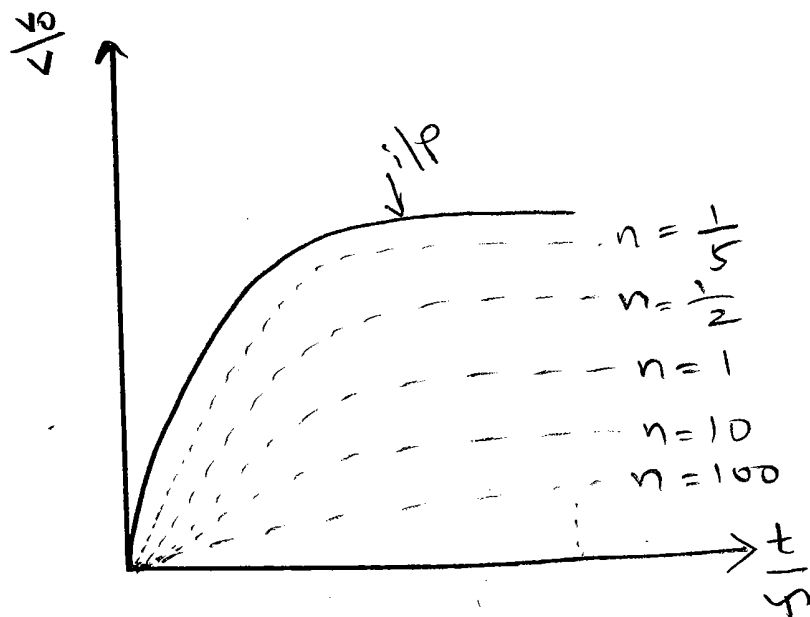The input and output waveforms for a given exponential input to a low pass RC circuit are shown below:



Low pass RC circuit acts as an Integrator

"If the time constant of an RC low-pass circuit is very large in comparison with the time required for the input signal to make an appreciable change, the circuit is called as integrator."

If the time constant of an RC low pass circuit is very large, the capacitor charges very slowly and so almost all the input voltage appears across the resistor for small values of time.

As $RC \gg T$, the voltage drop across C will be very small in comparison to the voltage drop across R and we may consider that the total input V_i appears across R, then

$$V_i = iR$$

$$i = \frac{V_i}{R}$$

For Low pass RC circuit, the output voltage V_o is given by

$$V_o = \frac{1}{C} \int i dt$$

$$V_o = \frac{1}{C} \int \frac{V_i}{R} dt$$

$$V_o = \frac{1}{RC} \int V_i dt$$

(or)

Apply KVL

$$V_i = iR + \frac{1}{C} \int i dt$$

$$V_o = \frac{1}{C} \int i dt$$

$$i = C \frac{dV_o}{dt}$$

$$V_i = RC \frac{dV_o}{dt} + V_o$$

If $RC \gg t$, transient is predominant

~~$$V_i = iR + \frac{1}{C} \int i dt$$~~

$$V_i = RC \frac{dV_o}{dt}$$

$$V_o = \frac{1}{RC} \int V_i dt$$

In terms of steady-state analysis, if we define satisfactory integration as meaning that an input sinusoid has been shifted at least 89.4° .

Then it is necessary, $RC > 15T$

where T = period of the sine wave

Advantages of Integrator over Differentiator.

Integrators are almost invariably preferred over differentiators in analog computer applications for the following reasons.

- 1) It is easier to stabilize an integrator than differentiator because the gain of an integrator decreases with frequency, whereas the gain of differentiator increases with frequency.
- 2) An integrator is less sensitive to noise voltage than a differentiator because of its limited bandwidth.
- 3) The amplifiers of a differentiator may overload if the input waveform changes very rapidly.
- 4) It is more convenient to introduce initial conditions in an amplifier.

Applications of High pass RC circuit :

- 1) AS a High pass filter, when $RC \gg T$
- 2) AS a Differentiator, when $RC \ll T$
- 3) AS a peaking circuit, when $RC \approx T$
- 4) AS a lead network.
- 5) To generate square wave from triangular wave
- 6) To generate step from ramp
- 7) To generate spikes from Rectangular or square wave form — The spikes are used as trigger pulses or synchronization pulses in circuits used in television and CRO's.

Applications of Low pass RC circuit :

- 1) AS a Low pass filter, when $RC \ll T$
- 2) AS an integrator, when $RC \gg T$
- 3) AS a lag network.
- 4) To perform mathematical integration in Analog computers.
- 5) To generate triangular wave from square wave.
- 6) To generate sawtooth wave from rectangular wave.
- 7) To trigger electronic devices.

Problems

High pass RC circuit

- 2.2) A 10Hz symmetrical square wave whose peak-to-peak amplitude is 2V is impressed upon high pass RC circuit whose lower 3-dB frequency is 5Hz. calculate and sketch the output waveform. In particular what is the peak-to-peak output amplitude?

Sol: Given data:


$$V_{p-p} = 2V$$

$$f = 10\text{ Hz}$$

$$f_L = 5\text{ Hz}$$

$$V_1 = V_1' = V_2 = V_2' = ?$$

$$V_{o p-p} = ?$$

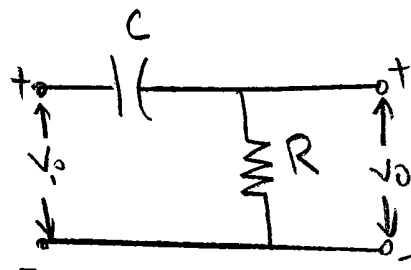

Time period T of the square wave is

$$T = \frac{1}{f} = \frac{1}{10} = 0.1\text{ sec}$$

$$f_L = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_L} = \frac{1}{2\pi \times 5} = \frac{1}{10\pi} = 0.0318\text{ sec}$$

Given symmetrical square wave

$$T_1 = T_2 = \frac{T}{2} = \frac{0.1}{2} = 0.05\text{ sec}$$

$RC < \frac{T}{2}$, so time taken by the capacitor to charge is less and discharge is also less.

For a Symmetrical square wave to a high pass RC circuit

$$V_1 = -V_2$$

$$V_1' = -V_2'$$

$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{2}{1 + e^{-0.05/0.0318}} = 1.656V$$


$$V_1' = V_1 e^{-T/2RC} = 1.656 \times e^{-0.05/0.0318} = 0.343V$$

$$V_1' = \frac{V}{1 + e^{T/2RC}} = \frac{2}{1 + e^{0.05/0.0318}} = 0.34V$$

$$\therefore V_1 = 1.66V, V_2 = -1.66V, V_1' = 0.34V, V_2' = -0.34V$$

The peak-to-peak output voltage

$$V_{O(P-P)} = |V_1| + |V_2| = 1.66 + 1.66 = \underline{3.32V}$$

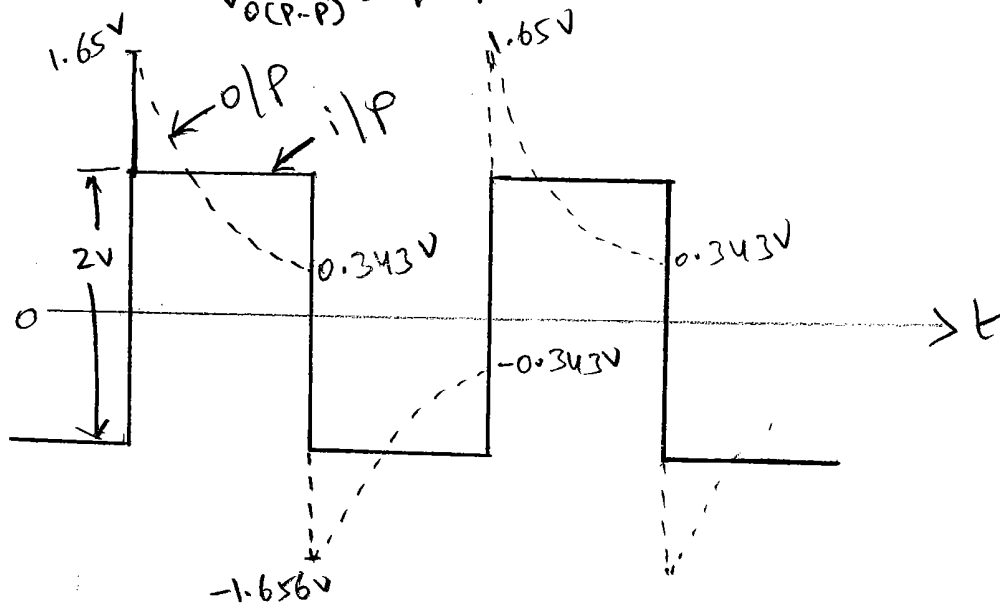

2-6) A 10-HZ square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions: The lower 3-dB frequency is a) 0.3 Hz b) 3.0 Hz c) 30 Hz.

Sol: Given data

$$f = 10 \text{ Hz}$$

$$T = \frac{1}{f} = \frac{1}{10} = 0.1 \text{ sec}$$

$$\frac{T}{2} = \frac{0.1}{2} = 0.05 \text{ sec}$$

a) $f_L = 0.3 \text{ Hz}$

$$f_L = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_L} = \frac{1}{2\pi \times 0.3} = 0.53 \text{ sec}$$

$RC \gg \frac{T}{2}$, Assume input peak-to-peak voltage is V volts and is symmetrical.


$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{V}{1 + e^{-\frac{0.05}{0.53}}} = 0.52V$$

$$V_1' = V_1 e^{-T/2RC} = 0.52 \cdot e^{-\frac{0.05}{0.53}} = 0.47V$$

$$V_2 = -V_1 = -0.52V$$

$$V_2' = -V_1' = -0.47V$$

$$\begin{aligned} \text{Peak-to-peak output voltage} &= |V_1| + |V_2| \\ &= |0.52| + |0.52| = 1.04V \end{aligned}$$

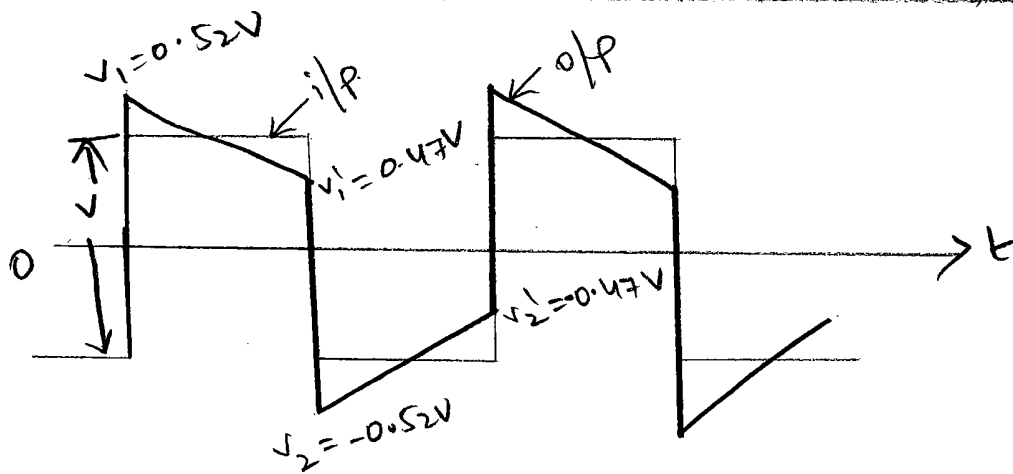

b) $f_L = 30 \text{ Hz}$

$$\frac{T}{2} = 0.05 \text{ sec}$$

$$RC = \frac{1}{2\pi f_L} = \frac{1}{2\pi \times 30} = 0.00265 \text{ sec}$$

$$RC \approx \frac{T}{2}$$


$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{V}{1 + e^{-\frac{0.05}{0.00265}}} = 0.719V$$

$$V_1' = V_1 e^{-T/2RC} = 0.719V \cdot e^{-\frac{0.05}{0.00265}} = 0.279V$$

$$V_2 = -V_1 = -0.719V$$

$$V_2' = -V_1' = -0.279V$$

Peak-to-peak output voltage = $|V_1| + |V_2|$
 $= |0.719V| + |0.719V| = 1.438V$

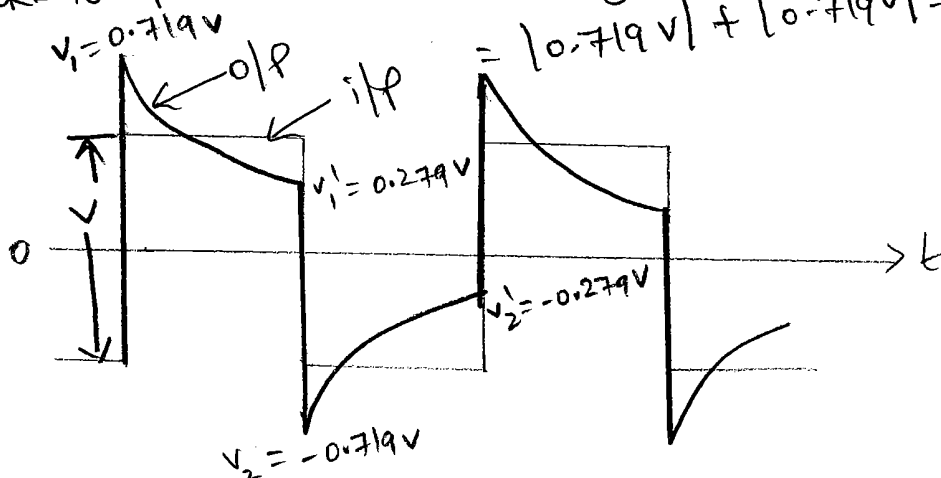

$$c) f_L = \underline{30\text{Hz}}$$

$$\frac{T}{2} = 0.05\text{sec}$$

$$RC = \frac{1}{2\pi f_L} = \frac{1}{2\pi \times 30} = 0.0053\text{sec}$$

$$RC < \frac{T}{2}$$

$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{V}{1 + e^{-\frac{0.05}{0.0053}}} = 0.99\text{V volts}$$


$$V_1' = V_1 e^{-T/2RC} = 0.99\text{V} \times e^{-\frac{0.05}{0.0053}} = 0.000079\text{V} \approx 0\text{V}$$

$$V_2 = -V_1 = -0.99\text{V}$$

$$V_2' = -V_1' = -0.000079\text{V} \approx 0\text{V}$$

Peak-to-peak voltage $V_{p-p} = |V_1| + |V_2|$

$$= |0.99\text{V}| + |0.99\text{V}| = 1.98\text{V}$$

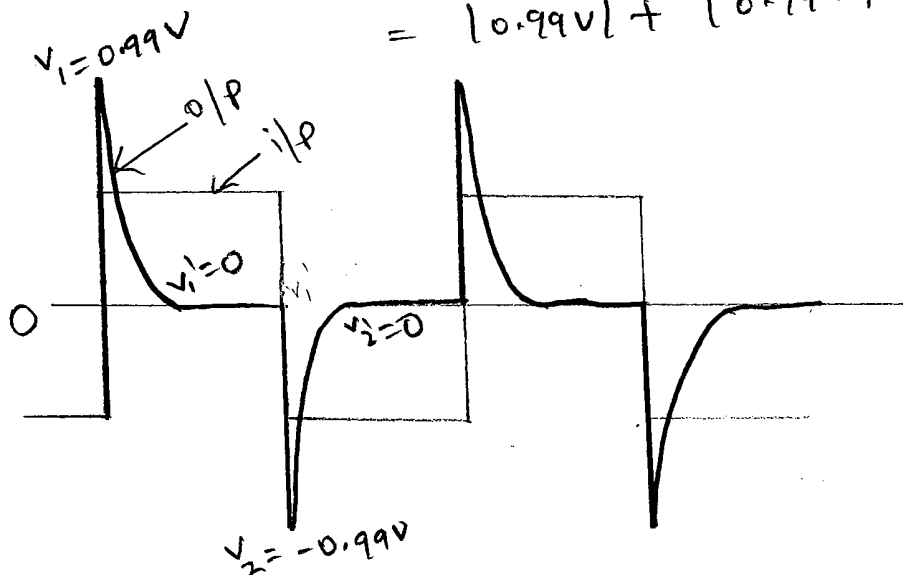

(2.4) A square wave whose peak-to-peak value is 1V extends $\pm 0.5V$ with respect to ground. The duration of positive section is 0.1 sec and negative section is 0.2 sec. If this waveform is impressed upon an RC differentiating circuit whose time constant is 0.2 sec. what are the steady state maximum and minimum values of the output waveform?

Sol: Given Data:

$$V_{i(p-p)} = 1V$$

$$V_{d.c} = 0$$

$$T_1 = 0.1 \text{ sec}$$

$$T_2 = 0.2 \text{ sec}$$

$$RC(\tau) = 0.2 \text{ sec}$$

$$V_1' = V_1 e^{-T_1/RC} \rightarrow (1)$$

$$V_2' = V_2 e^{-T_2/RC} \rightarrow (2)$$

$$V_1' - V_2 = V \rightarrow (3)$$

$$V_1 - V_2' = V \rightarrow (4)$$


sub eqn (1) in eqn (3)

$$V_1 \cdot e^{-T_1/RC} - V_2 = 1$$

sub eqn (2) in eqn (4)

$$V_1 - V_2 \cdot e^{-T_2/RC} = 1$$

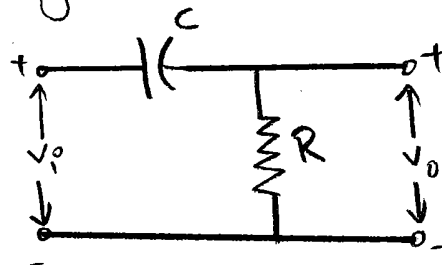Unsymmetrical square wave
High Pass RC circuit



By solving above two equations.

$$\begin{aligned} V_1 \cdot e^{-T_1/RC} - V_2 &= 1 \\ V_1 - V_2 \cdot e^{-T_2/RC} &= 1 \end{aligned}$$

$$\begin{array}{rcl} V_1 \cdot e^{-T_1/RC} - V_2 &= & 1 \\ V_1 \cdot e^{-T_1/RC} - V_2 \cdot e^{-T_2/RC} &= & e^{-T_1/RC} \\ \hline + & & \\ V_2 \left[e^{-T_1/RC} \cdot e^{-T_2/RC} - 1 \right] &= & 1 - e^{-T_1/RC} \end{array}$$

$$V_2 = \frac{1 - e^{-\frac{0.1}{0.2}}}{e^{\frac{-0.1}{0.2}} \cdot e^{\frac{-0.2}{0.2}} - 1} = \frac{0.393}{(0.606 \times 0.367 - 1)}$$

$$V_2 = \underline{\underline{-0.505 \text{ Volts}}}$$

$$V_2' = V_2 \cdot e^{-T_2/RC} = -0.505 e^{\frac{-0.2}{0.2}}$$

$$V_2' = \underline{\underline{-0.185 \text{ Volts}}}$$

$$V_1 - V_2' = 1$$


$$V_1 = 1 + V_2'$$

$$V_1 = 1 - 0.185 = \underline{\underline{0.8142 \text{ Volts}}}$$

$$V_1' - V_2 = 1$$

$$V_1' = 1 + V_2 = 1 - 0.505 = \underline{\underline{0.495 \text{ Volts}}}$$

$$\begin{aligned} \text{Peak-to-peak output voltage} &= |V_1| + |V_2| \\ &= |0.8142| + |0.505| = \underline{\underline{1.319 \text{ Volts}}} \end{aligned}$$

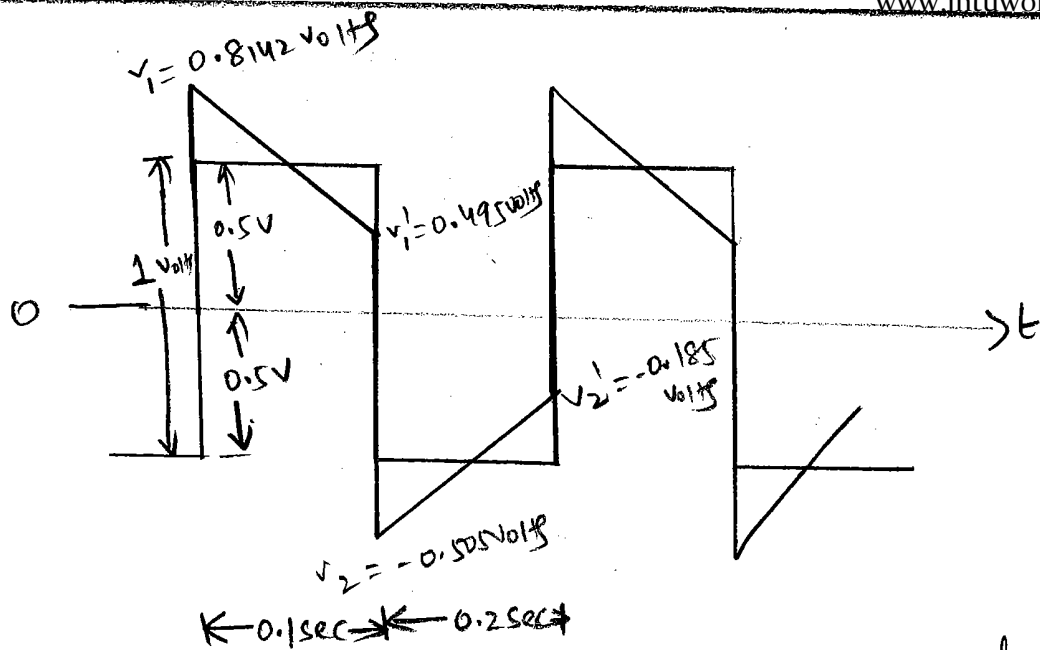

- (2.8) A square wave whose peak-to-peak value is 1V, extends ± 0.5 with respect to ground. The half period is 0.1sec. This voltage is impressed upon R.C differentiating circuit whose time constant is 0.2sec. Determine the maximum and minimum values of the output voltage in the steady state?

Sol: Given data

$$V_i(p-p) = 1V$$

$$T_1 = 0.1sec$$

$$T_2 = 0.1sec$$

$$RC(\tau) = 0.2sec$$

$$V_{dc} = 0V$$


$$V_1 = V_1' = V_2 = V_2' = ?$$

$$RC > T_1 \text{ i.e. } RC > \frac{T}{2}$$

$$\boxed{V_1 = V_1' e^{-T_1/RC}}$$

$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{1}{1 + e^{-\frac{0.2}{2 \times 0.2}}} = 0.6224 \text{ Volts} = -V_2$$
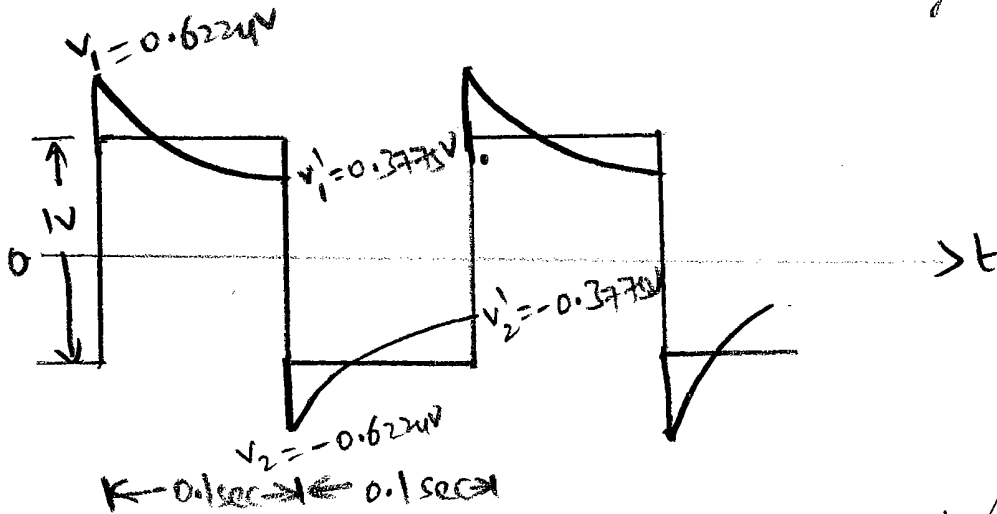
$$V_1' = V_1 e^{-T/2RC} = 0.6224 \cdot e^{-0.5} = 0.3775 \text{ Volts} = -V_2'$$



2.5) An exponential input is applied to an high pass RC circuit

- if $n \neq 1$ prove that the peak of the output pulse occurs at $x = 2.30 \frac{n}{n-1} \log n$.
- if $n = 1$ prove that the peak of the output pulse occurs at $x = 1$.

Sol:

a) For High Pass RC circuit by applying an exponential input if $T \neq RC$ or $n \neq 1$ is

$$V_o = \frac{V \cdot n}{n-1} \left[\frac{-x/n}{e} - \frac{-x}{e} \right] \quad \text{--- (1)}$$

Peak value of the output pulse occurs when

$$\frac{dV_o}{dx} = 0$$

Differentiate eqn (1) with respect to x

$$\frac{dvo}{dx} = \frac{v \cdot n}{n-1} \left[e^{-x/n} \cdot -\frac{1}{n} - e^{-x}(-1) \right]$$

$$0 = \frac{v \cdot n}{n-1} \left[-\frac{e^{-x/n}}{n} + e^{-x} \right]$$

$$0 = -\frac{vn}{n-1} \frac{e^{-x/n}}{n} + \frac{vn}{n-1} e^{-x}$$

$$\cancel{\frac{vn}{n-1}} \frac{e^{-x/n}}{n} = \cancel{\frac{vn}{n-1}} e^{-x}$$

$$e^{-x/n} = n e^{-x}$$

Taking natural log on both sides

$$-\frac{x}{n} \log_e e = \log_e n - x \log_e e, \text{ since } \log_e e = 1$$

$$-\frac{x}{n} = \log_e n - x$$

$$-\frac{x}{n} + x = \log_e n$$

$$x \left[-\frac{1}{n} + 1 \right] = \log_e n$$

$$x \left[\frac{n-1}{n} \right] = \log_e n$$

$$x = \frac{n}{n-1} \log_e n$$

$$\log_e n = \frac{\log_{10} n}{\log_{10} e}, \text{ but } \log_{10} e = \frac{\log_e e}{\log_{10} 10} = \frac{1}{2.3}$$

$$x = \frac{n}{n-1} \cdot \frac{\log_{10} n}{\frac{1}{2.3}}$$

$$x = 2.3 \cdot \frac{\eta}{\eta - 1} \log_{10} \eta$$

b) For High pass RC circuit by applying exponential input if $\tau = RC$ and $n = 1$ is

$$V_o = V \cdot x e^{-x}$$

Differentiate with respect to x

$$\frac{dV_o}{dx} = V \cdot e^{-x} + Vx e^{-x}(-1)$$

$$0 = V e^{-x} - Vx e^{-x}$$

$$0 = V e^{-x} [1 - x]$$

$$1 - x = 0$$

$$x = 1$$

$$\left| \frac{d(u \cdot v)}{dx} = u \frac{dv}{dx} + v \frac{du}{dx} \right|$$

let $u = e^{-x}$
 $v = Vx$

(2.2) The pulse from a high voltage generator (a magnetron) rises linearly for $0.05 \mu\text{sec}$ and then remains constant for $1 \mu\text{sec}$. The rate of rise of the pulse is measured with an RC differentiating circuit whose time constant is 250 psec . If the positive output voltage from the differentiator has a maximum value of 50 V , what is the peak voltage of the generator?

Sol: Given Data:

$$T = 0.05 \mu\text{sec}$$

$$RC = 250 \text{ psec} = 250 \times 10^{-12} \text{ sec}$$

$$V_o(\text{max}) = 50 \text{ V}$$

$$RC \ll T$$

By applying ramp input to high pass RC circuit

$$V_o = \alpha RC [1 - e^{-t/RC}]$$

for $RC \ll T$,

$$V_o = \alpha RC$$

$$50 = \alpha RC$$

$$\alpha = \frac{50}{RC} = \frac{50}{2.5 \times 10^{-12}} = 0.2 \times 10^{12} \text{ V/sec}$$


The peak value of the generator is

$$V_o = \alpha T$$

$$V_o = 0.2 \times 10^{12} \times 0.05 \text{ Vsec}$$


$$V_o = 10000 \text{ V}$$

$$V_{o(\text{max})} = 10 \text{ kV}$$

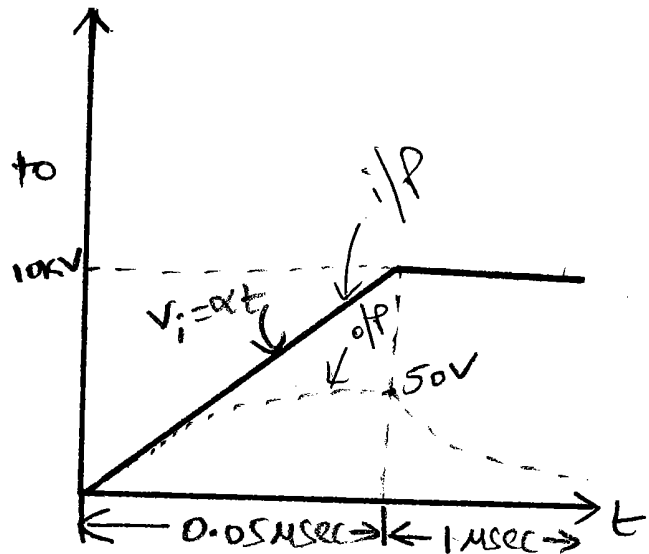

- (2.11) The Limited ramp is applied to an RC differentiator, what is the peak of the output waveform and draw to scale, the output waveform for the cases:
 a) $T = RC$ b) $T = 0.2 RC$ c) $T = 5 RC$

Sol:

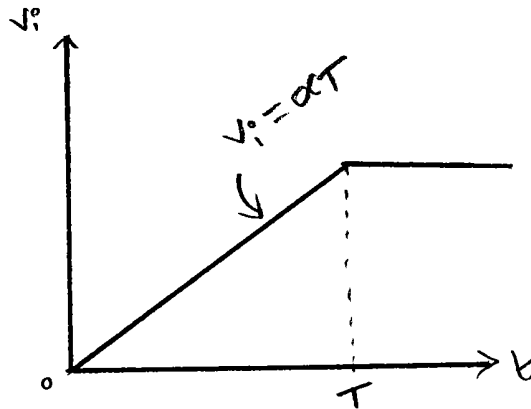

- a) The ramp input is applied to an RC high pass circuit, the output voltage is given by

$$V_o = \alpha RC [1 - e^{-t/RC}]$$

$$V_i = \alpha T$$

$$\alpha = \frac{V_i}{T}$$

$$V_o = \frac{V_i RC}{T} [1 - e^{-t/RC}]$$

at $T = RC$

$$V_o = \frac{V_i \cancel{RC}}{\cancel{RC}} [1 - e^{-\cancel{RC}/\cancel{RC}}]$$

$$V_o = V_i [1 - e^{-1}] = V_i [1 - 0.368]$$

$$\therefore \underline{V_o = 0.632 V_i}$$

b) at $T = \underline{0.2RC}$

$$V_o = \frac{V_i RC}{0.2RC} \left[1 - e^{-\frac{0.2RC}{RC}} \right]$$

$$V_o = \frac{V_i}{0.2} [1 - e^{-0.2}] = \frac{V_i}{0.2} [1 - 0.818]$$

$$\underline{V_o = 0.90 V_i}$$


c) at $T = \underline{5RC}$

$$V_o = \frac{V_i RC}{5RC} [1 - e^{-\frac{5RC}{RC}}]$$

$$V_o = \frac{V_i}{5} [1 - e^{-5}] = \frac{V_i}{5} [1 - 0.737 \times 10^{-3}]$$

$$\underline{V_o = 0.198 V_i}$$

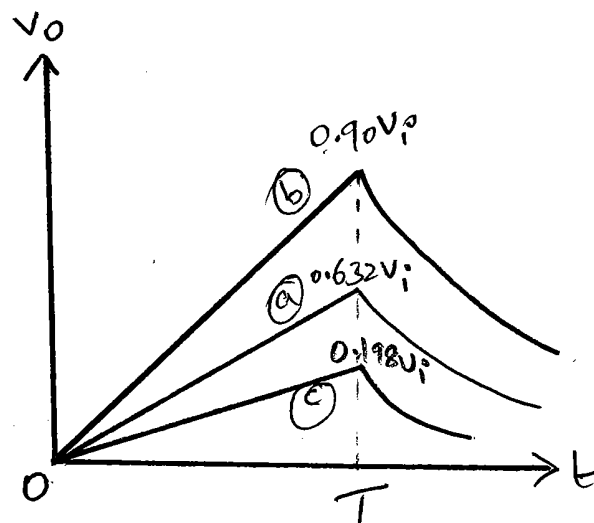The output waveform for different cases are shown below:




(2.1) A pulse of shown below is applied to a high-pass RC circuit. prove by direct integration that the area under the curve of fig shown below is zero.

Sol: for $t < t_p$

$$\text{Area} = \int_0^{t_p} v \cdot e^{-t/RC} dt$$

$$= v \int_0^{t_p} e^{-t/RC} dt$$

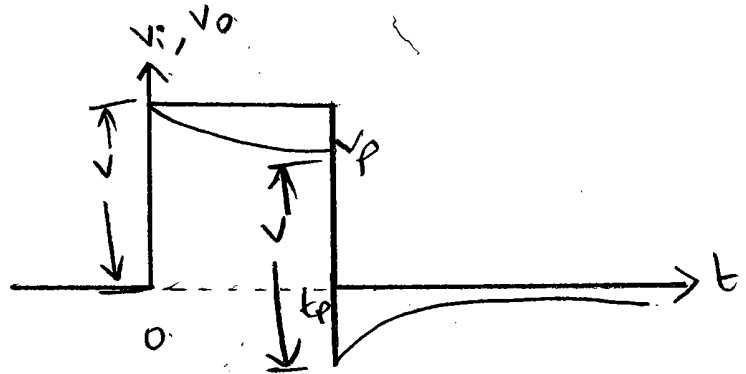

$$A_1 = v \left[\frac{e^{-t/RC}}{-1/RC} \right]_0^{t_p} = -vRC \left[e^{-t_p/RC} - e^0 \right]$$

$$A_1 = -vRC \left[e^{-t_p/RC} - 1 \right] \quad \text{--- (1)}$$

As $t > t_p$

$$\text{Area} = \int_{t_p}^{\infty} (v_p - v) \cdot e^{-\frac{(t-t_p)}{RC}} dt$$

$$A_2 = \int_{t_p}^{\infty} (v_p e^{-t_p/RC} - v) \cdot e^{-\frac{(t-t_p)}{RC}} dt$$

$$= v \int_{t_p}^{\infty} \cancel{e^{-t_p/RC}} \cdot e^{-t/RC} \cdot \cancel{e^{t_p/RC}} - e^{-\frac{(t-t_p)}{RC}} dt$$

$$= v \int_{t_p}^{\infty} e^{-t/RC} - e^{-\frac{t}{RC} + \frac{t_p}{RC}} dt$$

$$= V \left[\left(\frac{e^{-t/RC}}{-1/RC} \right)_{t_p} - \frac{t_p}{RC} \cdot \left(\frac{e^{-t/RC}}{-1/RC} \right)_{t_p} \right]$$

$$= -VRC \left[e^{-\frac{t_p}{RC}} - e^{\frac{t_p}{RC}} \left(e^{-\frac{t_p}{RC}} - e^{-\frac{t_p}{RC}} \right) \right] \quad \begin{matrix} \infty \\ e=0 \end{matrix}$$

$$= -VRC \left[-e^{-\frac{t_p}{RC}} - e^{\frac{t_p}{RC}} \times -e^{-\frac{t_p}{RC}} \right]$$

$$= -VRC \left[-e^{-\frac{t_p}{RC}} + e^{\frac{t_p}{RC}} \right]$$

$$= -VRC \left[-e^{-\frac{t_p}{RC}} + 1 \right]$$

$$A_2 = VRC \left[e^{-\frac{t_p}{RC}} - 1 \right] \quad \text{--- (2)}$$

$$\text{Total area (A)} = A_1 + A_2$$

$$= -VRC \left[e^{-\frac{t_p}{RC}} - 1 \right] + VRC \left[e^{-\frac{t_p}{RC}} - 1 \right]$$

$$\text{Total area} = A = 0$$

- ① An oscilloscope has a coupling capacitor $C_c = 1 \mu F$. When the input resistance $R_i = 1 M\Omega$, determine the minimum square wave frequency that can be displayed if the tilt is not to exceed 1%?

Sol: Given data:

$$R_i = 1 M\Omega$$

$$C_c = 1 \mu F$$

$$\% \text{ tilt} = 1\%$$

$$f = ?$$

$$\% \text{ tilt} = \frac{T}{2RC} \times 100$$

$$T = 2RC \times \% \text{ tilt} \times 100$$

$$T = 2 \times 1 \times 10^6 \times 1 \times 10^{-6} \times \frac{1}{100} \times 100$$

$$T = 0.01 \times 2 = 0.02 \text{ sec}$$

$$f = \frac{1}{T} = \frac{1}{0.02} = \underline{\underline{50 \text{ Hz}}}$$

- ② Calculate the lowest square wave frequency that can be passed by an amplifier with a cut-off frequency of 10 Hz, if the output tilt is not to exceed 2%?

Sol: Given data


$$f_1 = 10 \text{ Hz}, \% \text{ tilt} = 2\%$$

$$\% \text{ tilt} = \frac{\pi f_1}{f} \times 100$$

$$2\% = \frac{\pi \times 10}{f} \times 100$$

$$f = \frac{\pi \times 10 \times 100}{2} = \underline{\underline{1570.8 \text{ Hz}}}$$

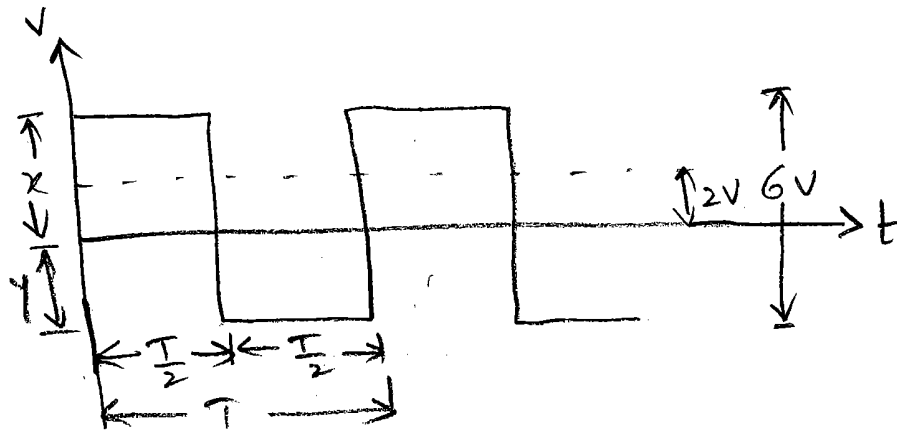- ③ A DC voltmeter indicates 2V when measuring a square wave with a peak-to-peak amplitude of 6V. Calculate the positive and negative amplitudes of the square wave.



Sol: Let T = period of square wave
 x = amplitude of positive peak
 y = amplitude of negative peak

Given peak-to-peak amplitude = $x + y = 6V$ — (1)

Since DC voltmeter indicates average value

$$V_{dc} = \frac{\text{Positive area} - \text{negative area}}{\text{period}} = \frac{x(\frac{T}{2}) - y(\frac{T}{2})}{\frac{T}{2} + \frac{T}{2}}$$

$$V_{dc} = \frac{x - y}{2}$$

$$\therefore \text{e}, \frac{x-y}{2} = 2$$

$$x-y = 4 \quad \text{--- (2)}$$

solving (1) & (2)

$$\begin{array}{r} x+y=6 \\ x-y=4 \\ \hline + \quad + \quad - \\ \hline 2y=2 \end{array}$$

$$y = \underline{1}$$

sub y value in eqn (1)



$$x+y=6$$

$$x+1=6$$

$$x = \underline{5}$$

$\therefore$ positive peak amplitude = 5V
negative peak amplitude = 1V

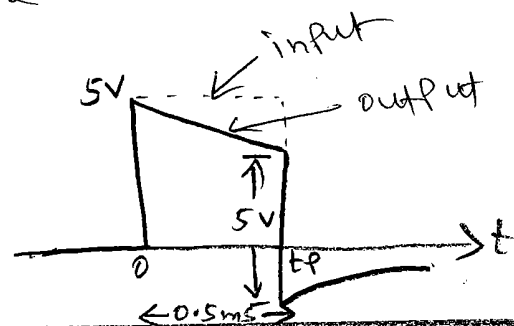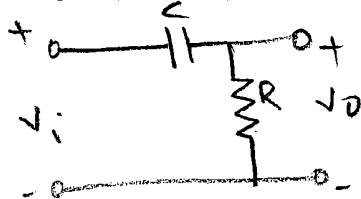④ A pulse of 5V amplitude and 0.5ms duration is applied to an RC high pass circuit with $R=22k\Omega$ and $C=0.47\mu F$. Sketch the output waveform and determine the percentage tilt in the output?



Sol : Given Data :

$$R = 22k\Omega$$

$$C = 0.47\mu F$$

$$V = 5V$$

$$t_p = 0.5ms$$

$$\tau = RC = 22 \times 10^3 \times 0.47 \times 10^{-6} = 10.34ms$$

$$\therefore RC \gg t_p$$

i) $0 < t < t_p$

$$V_o = V e^{-t/RC} = 5 e^{-t/RC}$$

ii) at $t = t_p$

$$V_p = V_o = 5 e^{-t_p/RC} = 5 e^{-0.5/10.34} = \underline{\underline{4.763 \text{ volt}}}$$

iii) at $t > t_p$

$$V_o = (V_p - V) e^{-(t-t_p)/RC}$$

$$V_o = (4.763 - 5) e^{-(t-0.5 \times 10^{-3})/10.34 \times 10^{-3}}$$



$$V_o = -0.237 e^{-(t-0.5 \times 10^{-3})/10.34 \times 10^{-3}}$$

$$\% \text{ tilt (P)} = \frac{V_1 - V_1'}{V/2} \times 100$$

$$= \frac{5 - 4.763}{5/2} \times 100$$

$$P = \underline{\underline{\quad\quad\quad}}$$

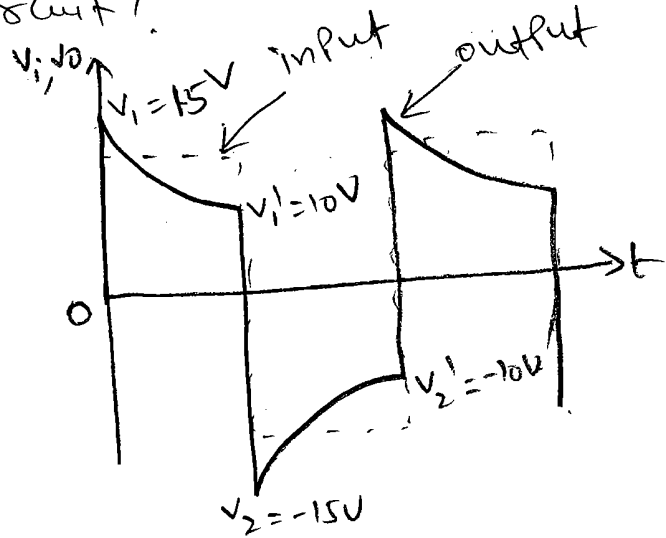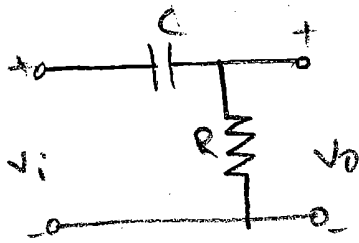- ⑤ If a square wave of 5KHz is applied to an RC high pass circuit and resultant waveform measured on a CRO was tilted from 15V to 10V, find out the lower 3-dB frequency of the high-pass circuit?



Given data:

Sol:

$$f = 5 \text{ KHz}$$

$$V_1 = 15 \text{ V}$$

$$V_1' = 10 \text{ V}$$

$$f_1 = ?$$

$$\text{Peak to peak voltage (V)} = |V_1| + |V_2| = 15 + 15 = 30$$

$$\% \text{ tilt} = \frac{V_1 - V_1'}{\frac{V}{2}} \times 100$$

$$P = \frac{15 - 10}{30/2} \times 100$$

$$P = 33.33\%$$

$$P = \frac{\pi f_1}{f} \times 100$$



$$33.33 = \frac{3.14 \times f_1}{5 \times 10^3} \times 100$$

$$f_1 = 530.56 \text{ Hz}$$

⑥ A symmetrical square wave is applied to high-pass circuit having $R = 20 \text{ k}\Omega$, $C = 0.05 \mu\text{F}$

a) If the frequency of input signal is 1 kHz and signal swings between $\pm 5 \text{ V}$, draw the output waveform and indicate the voltages.

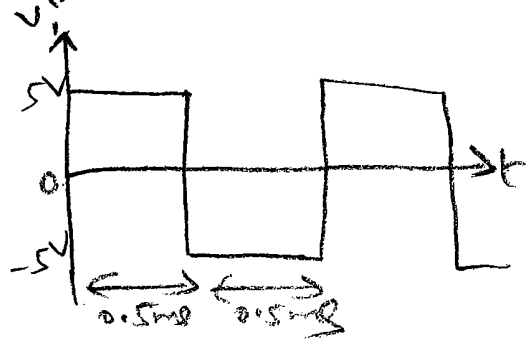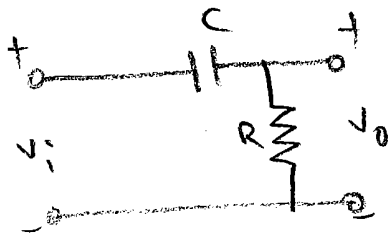b) What happens if the frequency of the signal is reduced to 100 Hz ? Show the output waveform?



Sol: $\tau = RC = 20 \times 10^3 \times 0.05 \times 10^{-6} = 1 \text{ ms}$

Given $f = 1 \text{ kHz}$

$$\therefore T = \frac{1}{f} = 1 \text{ ms}$$

$$T/2 = 0.5 \text{ ms}$$

$$V_1 = \frac{V}{1 + e^{-T/2RC}} = \frac{10}{1 + e^{-0.5 \times 10^{-3} / 10^{-3}}} = 6.23 \text{ V}$$

$$V_1' = \frac{V}{1 + e^{T/2RC}} = \frac{10}{1 + e^{0.5}} = 3.78 \text{ V}$$

$$V_2 = -V_1 = -6.23 \text{ V}$$

$$V_2' = -V_1' = -3.78 \text{ V}$$

b) If f is reduced to 100 Hz

$$T = \frac{1}{f} = \frac{1}{100} = 10 \text{ ms}$$



$$V_1 = \frac{V}{1 + e^{-\pi/2 RC}} = \frac{10}{1 + e^{-5}} = 9.93 \text{ V}$$

$$V_2 = -V_1 = -9.93 \text{ V}$$

$$V_1' = \frac{V}{1 + e^{\pi/2 RC}} = \frac{10}{1 + e^5} = 0.067 \text{ V}$$

$$V_2' = -V_1' = -0.067 \text{ V}$$

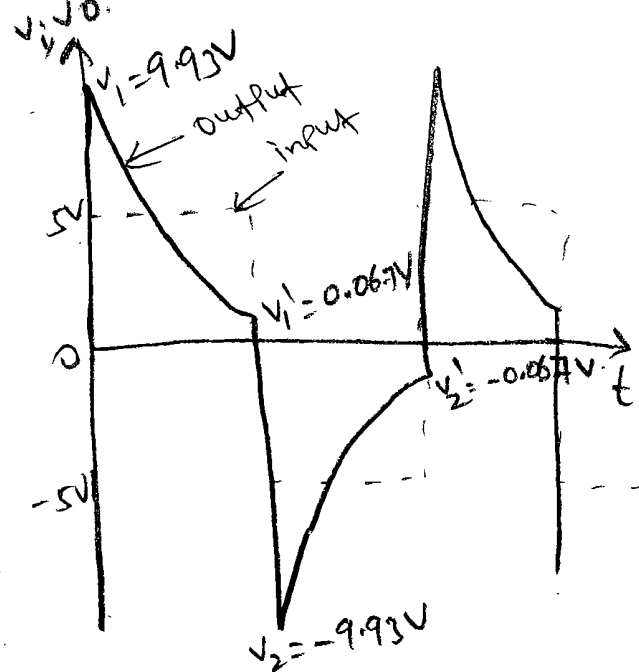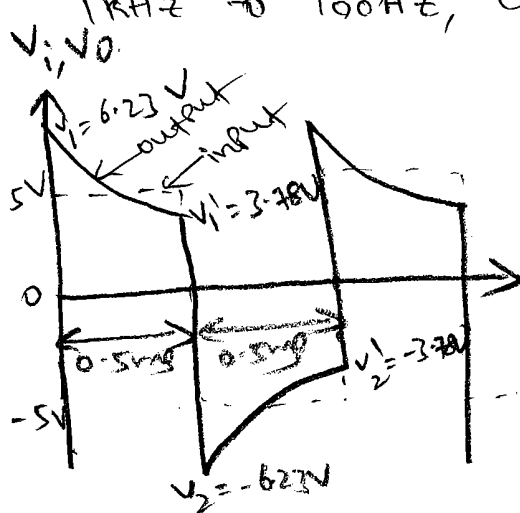$\therefore$ when i/p signal frequency is reduced from 1 KHz to 100 Hz, CM acts as differentiator.



⑦ A 100Hz triangular wave with peak-to-peak amplitude of 9V is applied to a differentiating circuit with $R=1M\Omega$, $C=100pF$. Calculate and sketch the waveform of the output?

Sol: time constant (τ) = $RC = 1 \times 10^6 \times 100 \times 10^{-12} = 100 \mu s$

frequency of triangular wave (f) = 100Hz

time period (T) = $\frac{1}{f} = \frac{1}{100} = 0.01s = 10ms$

$RC \ll T$, so it acts as differentiator

for positive rising


$$V_o = \alpha RC$$

but $\alpha = \frac{V_i}{T} = \frac{9}{5ms}$

$$V_o = \frac{9}{5 \times 10^{-3}} \times 100 \times 10^{-6} =$$

for negative rising
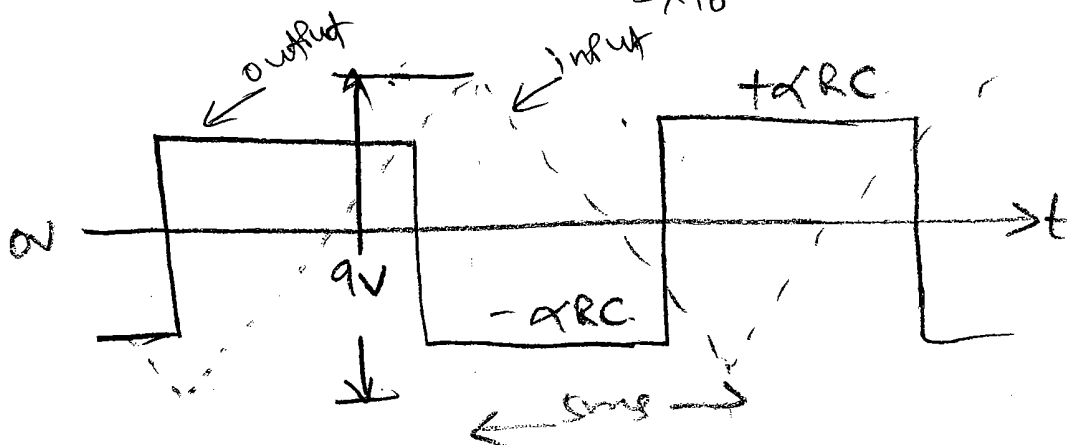
$$V_o = -\alpha RC = -\frac{9}{5 \times 10^{-3}} \times 100 \times 10^{-6} =$$



Low pass RC circuit

(2-16) An ideal 1 μ -sec pulse is fed to an amplifier. Calculate and plot the output waveform under the following conditions. The upper 3-dB frequency is

- a) 10 MHz b) 1 MHz c) 0.1 MHz

Sol: Given data:

$$t_p = 1 \mu\text{-sec}$$

given upper 3-dB frequency, Low pass RC circuit

a) $f_2 = 10 \text{ MHz}$

$$f_2 = \frac{1}{2\pi RC}$$


$$RC = \frac{1}{2\pi f_2} = \frac{1}{2\pi \times 10 \times 10^6} = 0.015 \mu\text{sec.}$$

$$RC \ll t_p$$

$$V_o = V_{in} [1 - e^{-t_p/RC}]$$

$$V_o = V [1 - e^{-1/0.015}]$$

$$V_o \approx V_{in} \text{ volts}$$

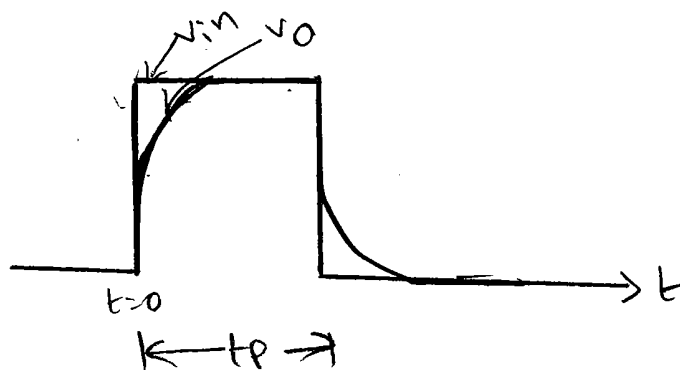

b) $f_2 = \underline{1 \text{ MHz}}$

$$f_2 = \frac{1}{2\pi RC}$$


$$RC = \frac{1}{2\pi f_2} = \frac{1}{2\pi \times 10^6} = 0.154 \text{ sec}$$

$$RC < t_p$$

$$V_o = V_{in} [1 - e^{-t_p/RC}]$$

$$V_o = V_{in} [1 - e^{-1/0.15}]$$

$$V_o \approx 0.99 V_{in}$$

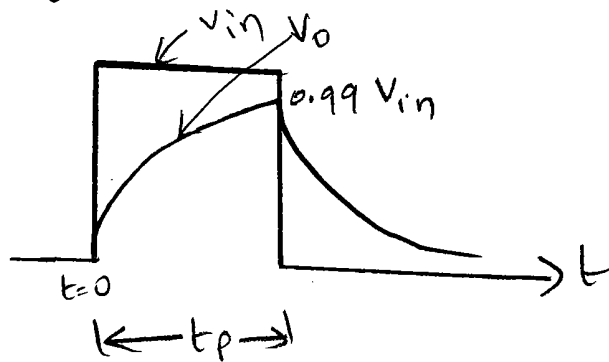

c) $f_2 = \underline{0.1 \text{ MHz}}$

$$f_2 = \frac{1}{2\pi RC}$$


$$RC = \frac{1}{2\pi f_2} = \frac{1}{2\pi \times 0.1 \times 10^6} = 1.59 \mu\text{sec}$$

$$RC > t_p$$

$$V_o = V_{in} [1 - e^{-t_p/RC}]$$

$$V_o = V_{in} [1 - e^{-1/1.59}]$$

$$V_o = \underline{0.46 V_{in}}$$

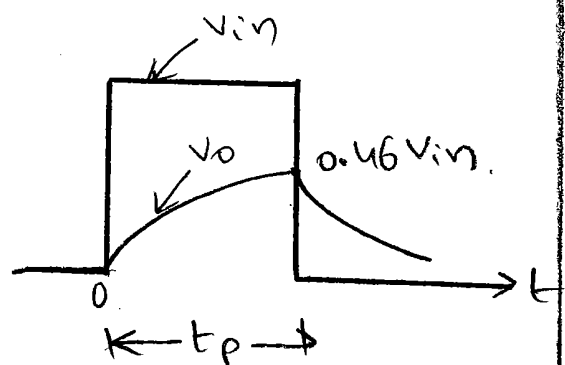


$$V_{i(p-p)} = 2V$$

$$V_{d.c} = 0V$$

$$RC = \frac{T}{2}$$

i.e., $RC < T$

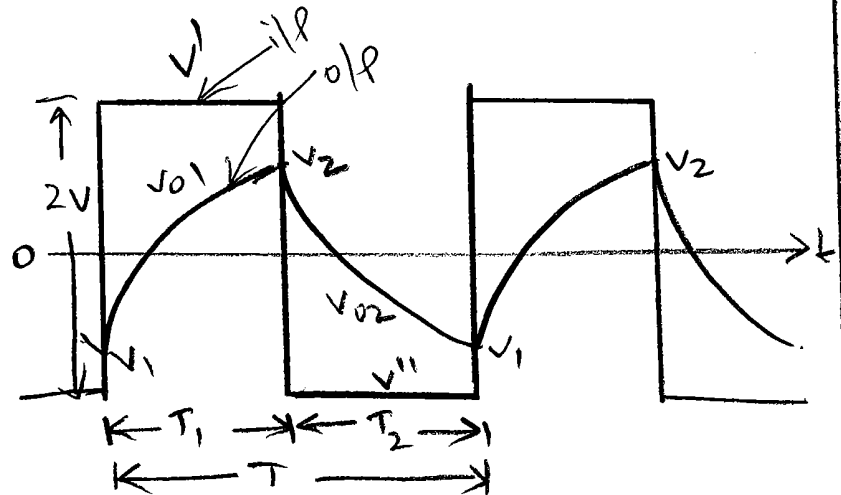

During positive half cycle

$$v_o = v_f + (v_i - v_f) e^{-t/\tau}$$

$$v_{o1} = v' + (v_i - v') e^{-t/RC}$$

$$v_{01} = v' + (v_1 - v') \hat{e}$$

$$v' = -v'' = 1V, \text{ at } t = T_1, v_0 = v_{01} = v_2$$

$$V_2 = 1 + (V_1 - 1) e^{\frac{-T_1' / RC}{-T_1/2 / T_1/2}}$$

$$v_2 = 1 + (v_1 - 1) \bar{e}$$

$$v_2 = 1 + (v_1 - 1)e^{-1}$$

$$V_2 = 1 + V_1 e^{-1} - e^{-1}$$

$$V_2 = V_1 e^{-1} + 0.632$$

$$v_1 e^{-1} = v_2 - 0.632 \quad \text{--- (1)}$$

Symmetrical wave so

$$T_1 = T_2 = \frac{T}{2}$$

During negative half cycle

$$V_0 = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_{02} = V'' + (V_2 - V'') e^{-t/RC}$$

at $t = T_2 = \frac{T}{2}$, $V_0 = V_{02} = V_1$, $V'' = -1$

$$V_1 = -1 + (V_2 + 1) e^{-T_2/RC}$$

$$V_1 = -1 + (V_2 + 1) e^{-T/2 / \pi/2}$$

$$V_1 = -1 + (V_2 + 1) e^{-1}$$

$$V_1 = -1 + V_2 e^{-1} + e^{-1}$$

$$V_1 = V_2 e^{-1} - 0.632 \quad \text{--- (1)}$$

$$V_2 e^{-1} = V_1 + 0.632 \quad \text{--- (2)}$$

Solving eqn (1) and eqn (2)

$$V_1 e^{-1} = V_2 - 0.632$$

$$V_2 e^{-1} = V_1 + 0.632$$

Solving (1) & (2)

$$V_1 e^{-1} = V_2 - 0.632$$

$$\frac{V_1}{e} = V_2 e^{-1} - 0.632$$

$$V_1 e^{-1} = V_2 - 0.632$$

$$V_1 e^{-1} = V_2 e^{-2} - 0.632 e^{-1}$$

$$V_2 (1 - e^{-2}) + 0.632 (e^{-1} - 1)$$

$$V_2(1 - e^{-2}) = 0.632 \times 0.367 - 0.632$$

$$V_2(1 - 0.135) = 0.23 - 0.632$$

$$V_2 \times 0.865 = -0.4$$

$$V_2 = \underline{\underline{-0.46 \text{ Volts}}}$$

Solving (1) & (2)

$$V_1 = V_2 e^{-1} - 0.632$$

$$V_1 e^{-1} = V_2 - 0.632$$

$$\frac{V_1 e^{-1}}{V_1 e^{-1}} = \frac{V_2 e^{-2} - 0.632 e^{-1}}{V_2 e^{-1} - 0.632}$$

$$\frac{V_1 e^{-1}}{V_1 e^{-1}} = \frac{V_2 e^{-2} - 0.632 e^{-1}}{V_2 e^{-1} - 0.632}$$

$$0 = V_2(e^{-2} - 1) + 0.632(1 - e^{-1})$$

$$V_2(e^{-2} - 1) = -0.632(1 - e^{-1})$$

$$V_2 = \frac{-0.399}{-0.864} = \underline{\underline{0.461 \text{ Volts}}}$$

sub V_2 in eqn (2)

$$V_1 = 0.461 \times e^{-1} - 0.632$$

$$V_1 = \underline{\underline{-0.462 \text{ Volts}}}$$

∴ Peak-to-peak output voltage = $|V_1| + |V_2|$

$$V_{O-P-P} = 0.461 + 0.462$$

$$V_{O-P-P} = \underline{\underline{0.922 \text{ Volts}}}$$

(or)

$$V_2 = \frac{V}{2} \tanh x$$

$$\text{where } x = \frac{T}{4RC}$$

$$V_2 = -V_1 = \frac{V}{2} \left[\frac{1 - e^{-T/2RC}}{1 + e^{-T/2RC}} \right]$$


(2.20) The periodic waveform shown below is applied to an RC integrating network whose time constant is $10\mu\text{s}$. Sketch the output waveform. Calculate the maximum and minimum values of the output voltage with respect to ground under steady state conditions. Also, calculate and plot the output for the first two cycles of the input.

Sol: Given data:

$$RC = 10\mu\text{s}$$

$$T_1 = 10\mu\text{s}$$

$$T_2 = 1\mu\text{s}$$

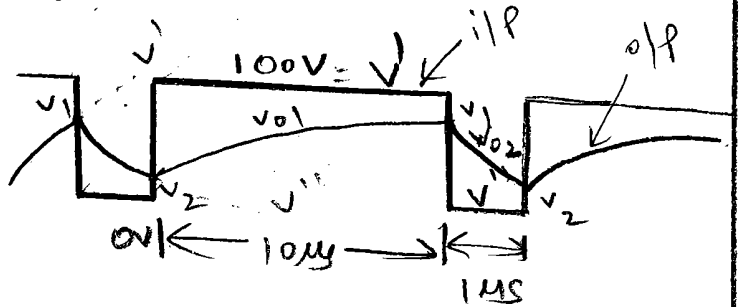

i) between $0 < t < 10\mu\text{s}$:

$$v_i' = 100\text{V}$$

for rising portion

$$v_o = v_f + (v_i - v_f) e^{-t/RC}$$

$$v_{o1} = v_i' + (v_2 - v_i') e^{-t/10}$$

$$v_{o1} = 100 + (v_2 - 100) e^{-t/10}$$

ii) At $t_1 = 10\mu\text{s}$, $v_{o1} = v_1$

$$v_1 = v_i' + (v_2 - v_i') e^{-t_1/RC}$$

$$v_1 = 100 + (v_2 - 100) e^{-10/10}$$

$$v_1 = 63.21 + 0.368 v_2 \quad \text{--- (1)}$$

iii) between $10\mu\text{s} < t < 11\mu\text{s}$ $v_i'' = 0\text{V}$

$$v_{o2} = v_i'' + (v_1 - v_i'') e^{-(t - T_1)/RC}$$

$$v_{o2} = 0 + (v_1 - 0) e^{-(t - 10)/10}$$

iv) at $t = 11 \mu s$, $v_{02} = v_2$

$$v_2 = 0 + v_1 e^{-1/10} = 0.905 v_1 \quad \text{--- (2)}$$

Substitute eqn (2) in eq (4)

$$v_1 = 63.22 + 0.368 v_2$$

$$v_1 = 63.22 + 0.368 \times 0.905 v_1$$

$$v_1 = 63.22 + 0.33 v_1$$

$$v_1 - 0.33 v_1 = 63.22$$

$$v_1 (1 - 0.33) = 63.22$$

$$v_1 = \frac{63.22}{0.67} = 94.35 \text{ V}$$

$$\underline{v_1 = 94.35 \text{ V}}$$

Substitute v_1 in eqn (2)

$$v_2 = 0.905 v_1 = 0.905 \times 94.35$$

$$\underline{v_2 = 85.39 \text{ V}}$$

(2-21) A symmetrical square wave whose average value is zero has a peak-to-peak amplitude of 20V and a period of 24 sec. This waveform is applied to a Low pass RC circuit whose upper 3-dB frequency is $\frac{1}{2\pi} \text{ MHz}$. Calculate and sketch the steady-state output waveform. In particular, what is the peak-to-peak amplitude?

Sol: Given data:

$$V_{(P-P)} = 20V$$

$$T = 2\mu\text{sec}$$

$$f_2 = \frac{1}{2\pi} \text{MHz}$$

$$T_1 = T_2 = \frac{T}{2} = 1\mu\text{sec}.$$

$$f_2 = \frac{1}{2\pi RC} = 10^{-6} \text{sec} = 1\mu\text{sec}.$$

$$RC = \frac{1}{2\pi f_2} = \frac{1}{2\pi \times \frac{1}{2\pi} \times 10^6}$$

$$V_0 = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_{01} = V_1' + (V_i - V_1') e^{-t/RC}$$

$$\text{at } t = T_1, V_{01} = V_2$$

$$V_2 = 10 + (V_1 - 10) e^{-\frac{1\mu\text{sec}}{1\mu\text{sec}}}$$

$$V_2 = 10 + (V_1 - 10) e^{-1}$$


$$\text{Due to Symmetry, } V_1 = -V_2$$

$$V_2 = 10 + (-V_2 - 10) e^{-1}$$

$$V_2 = 4.619V$$

$$\therefore V_1 = -4.619V$$

$$V_{O(P-P)} = |V_1| + |V_2| = 2 \times 4.619 = \underline{\underline{9.23 \text{ volts}}}$$

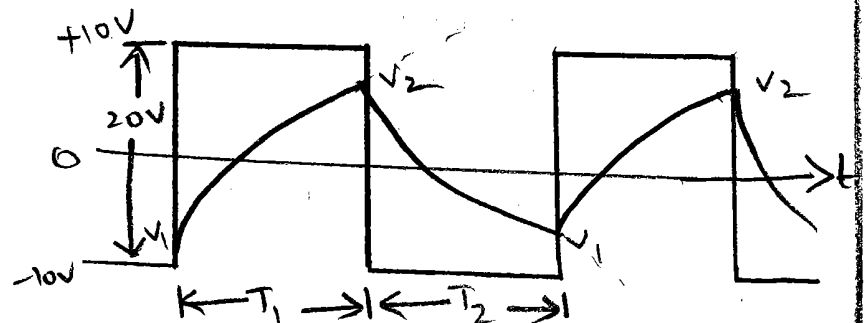

2-22 A square wave whose peak-to-peak amplitude is 2V extends $\pm 1V$ with respect to ground. The duration of positive section is 0.1 sec and that of the negative section is 0.2 sec. If this waveform is impressed upon an RC integrating circuit whose time constant is 0.2 sec. what are the steady-state maximum and minimum values of the output waveform?

Sol: Given data:

$$V_{p-p} = 2V$$


$$T_1 = 0.1 \text{ sec}$$

$$T_2 = 0.2 \text{ sec}$$

$$RC(\tau) = 0.2 \text{ sec}$$

$$T = T_1 + T_2 = 0.3 \text{ sec}$$

$$RC > T_1, RC = T_2$$

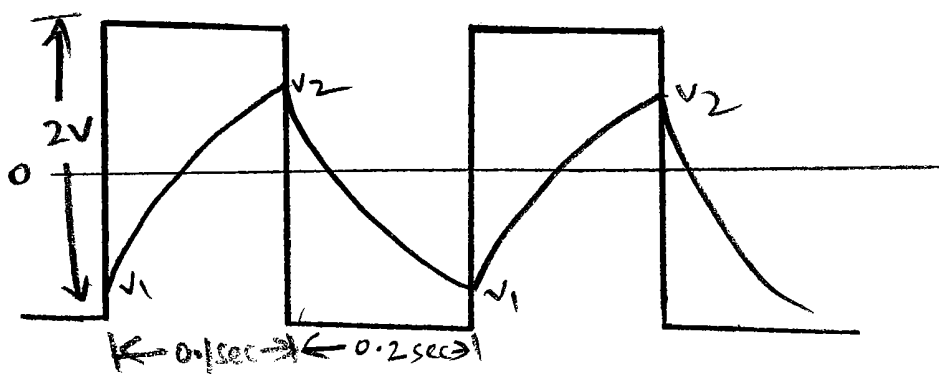

$$V_0 = V_f + (V_i - V_f) e^{-t/RC}$$

for $t = T_1$: $V_0 = V_2$, $V_f = V_1 = 1V$, $V_{in} = V_1$,

$$V_2 = 1 + (V_1 - 1) e^{-T_1/RC}$$

$$V_2 = 1 + (V_1 - 1) e^{\frac{-0.1}{0.2}}$$

$$V_2 = 1 + (V_1 - 1) e^{-\frac{1}{2}}$$

$$V_2 = 1 + 0.606 V_1 - 0.606$$

$$0.606 V_1 - V_2 = -0.393 \quad \text{--- (1)}$$

for $t = T_2$, $V_0 = V_1$, $V_f = V'' = -1$, $V_{in} = V_2$

$$V_1 = -1 + (V_2 + 1) e^{\frac{-0.2}{0.2}}$$

$$V_1 = -1 + 0.368 V_2 + 0.368$$

$$V_1 - 0.368 V_2 = -0.632 \quad \text{--- (2)}$$

Solving (1) & (2)

$$0.606 V_1 - V_2 = -0.393$$

$$V_1 - 0.368 V_2 = -0.632$$

$$\begin{array}{r} 0.606 V_1 - V_2 = -0.393 \\ 0.606 V_1 - 0.223 V_2 = -0.3829 \\ \hline -0.777 V_2 = -0.01 \end{array}$$

$$\therefore V_2 = \underline{0.012 \text{ volt}}$$

Sub V_2 in eqn (1)

$$0.606 V_1 - 0.012 = -0.393$$

$$\therefore V_1 = \underline{-0.628 \text{ volt}}$$

2-26) The Limited ramp of below fig is applied to a Low-pass RC integrating circuit. Draw to scale the output waveforms for the cases:

- a) $T = RC$ b) $T = 0.2 RC$ c) $T = 5 RC$

Sol:

- a) $T = RC$

By applying ramp input to high-pass RC circuit

output voltage

$$V_o = \alpha RC [1 - e^{-t/RC}]$$

By applying to Low-pass RC circuit output voltage

$$V_o = \alpha t - \alpha RC (1 - e^{-t/RC})$$

if $T = RC$

$$V_o = \alpha RC - \alpha RC (1 - e^{-RC/RC})$$


$$V_o = \cancel{\alpha RC} - \cancel{\alpha RC} + \alpha RC e^{-1}$$

$$V_o = \alpha RC \times 0.367 \text{ volts}$$

$$V_i = \alpha t \Rightarrow \alpha = \frac{V_i}{t} = \frac{V}{RC}$$

$$V_o = \frac{V}{\cancel{RC}} \cdot \cancel{RC} \times 0.367$$
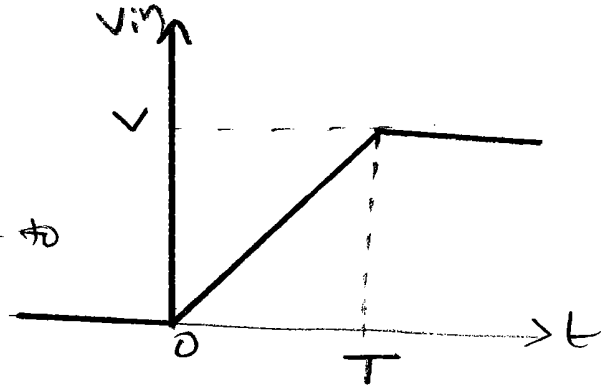
$$V_o = \underline{\underline{0.367 V \text{ volts}}}$$



b) $T = \underline{0.2RC}$

$$V_0 = \alpha t - \alpha RC (1 - e^{-T/RC})$$

$$V_0 = \alpha RC (0.2) - \alpha RC + \alpha RC e^{-\frac{0.2RC}{RC}}$$

$$V_0 = \alpha RC (0.2 - 1 + e^{-0.2})$$

$$V_0 = \alpha RC \times 0.018$$

$$V_0 = \frac{V}{0.2RC} \cdot RC \times 0.018$$

$$V_0 = 0.093V$$

$$V_0 \approx \underline{0.1V \text{ volts}}$$

c) $T = \underline{5RC}$

$$V_0 = \alpha T - \alpha RC (1 - e^{-T/RC})$$


$$V_0 = 5\alpha RC - \alpha RC (1 - e^{-5RC/RC})$$

$$V_0 = \alpha RC (5 - 1 + e^{-5})$$

$$V_0 = \alpha RC \times 4.0067$$

$$V_0 = \frac{V}{5RC} \cdot RC \times 4.0067$$

$$V_0 = \underline{0.8V \text{ volts}}$$

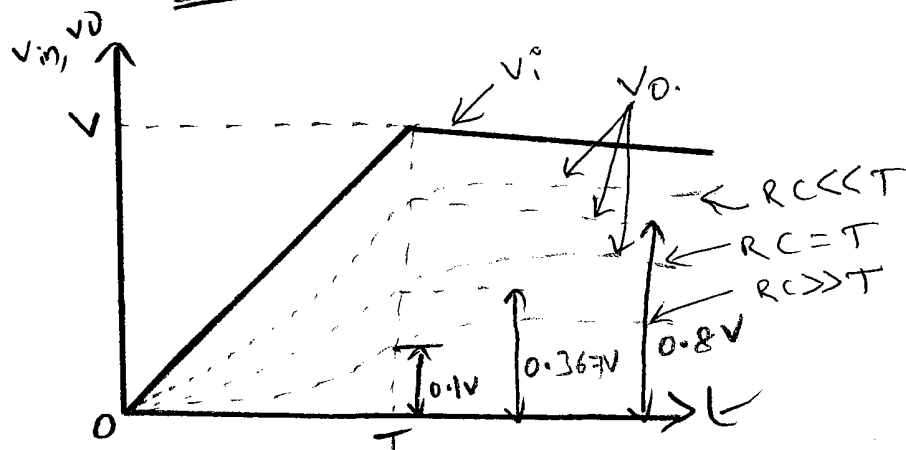

Problem:

The output waveform from an amplifier under pulse test has a rise time of $1 \mu\text{sec}$. Determine the upper 3-dB frequency of the amplifier?

Sol: Given data:

$$t_r = 1 \mu\text{sec}$$

$$f_2 = ?$$

$$f_2 = \frac{0.35}{t_r} = \frac{0.35}{1 \times 10^{-6}} = \underline{\underline{350 \text{ KHz}}}$$

"
→ For two stages whose individual rise times are t_{r1} and t_{r2} respectively. The resultant rise time t_r is given by.

$$t_r = 1.05 \sqrt{t_{r1}^2 + t_{r2}^2}$$

Problem:

A pulse wave with a rise time of $10 \mu\text{sec}$ is applied to an amplifier which has an upper cut-off frequency of 350 KHz . Calculate the risetime in the output waveform.

Sol:

$$\text{rise time} \rightarrow t_{rs} = 10 \mu\text{sec}$$

$$\text{rise time} \rightarrow t_{rc} = \frac{0.35}{f_h} = \frac{0.35}{350 \text{ KHz}} = 1 \mu\text{sec}$$

output rise time is

$$t_r = 1.05 \sqrt{(t_{rs})^2 + (t_{rc})^2}$$

$$t_r = 1.05 \sqrt{(10 \times 10^{-6})^2 + (1 \times 10^{-6})^2}$$

$$t_r = 1.05 \sqrt{10^{-10} + 10^{-12}}$$

$$t_r = 1.055 \times 10^{-5}$$

$$t_r \approx \underline{\underline{10.55 \mu\text{sec}}}$$

→ Let the time of individual stages be $t_{r1}, t_{r2}, \dots, t_{rn}$ and let the input waveform rise time be t_{r0} , then the output signal rise time is given by


$$t_r = 1.1 \sqrt{t_{r0}^2 + t_{r1}^2 + t_{r2}^2 + \dots}$$

(2-28) a) Prove that an RC circuit behaves as a reasonably good integrator if $RC \gg 15T$, where T is the period of an input sinusoid $E_m \sin \omega t$. [08]

The condition for good integration is $RC \gg 15T$

b) Show that the output is approximately

$$-\left[\frac{E_m}{\omega RC}\right] \cos \omega t.$$

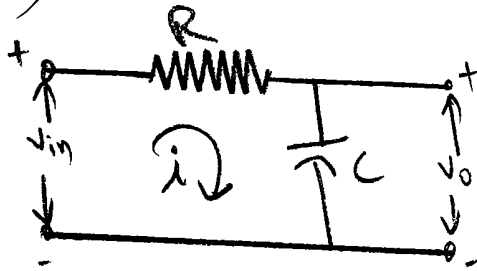Sol: a)

Apply KVL at output side

$$V_o = \frac{X_C \times I}{j}$$

$$\text{where } I = \frac{V_{in}}{R + \frac{X_C}{j}}, \quad X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$

$$V_o = \frac{1/j\omega C}{R + 1/j\omega C} \times V_{in}$$

$$V_o = \frac{V_{in}}{1 + j\omega RC}$$

$$\text{if } V_i = E_m \sin \omega t$$

$$V_o = \frac{E_m \sin \omega t}{1 + j\omega RC}$$

$$\therefore |V_o| = \frac{V_m}{\sqrt{1 + \omega^2 R^2 C^2}} \sin(\omega t - \phi)$$

$$\text{where } \phi = \tan^{-1}(\omega RC)$$

$$\phi = \tan^{-1}(2\pi f RC)$$

$$\phi = \tan^{-1}\left(\frac{2\pi}{T} RC\right)$$

Low Pass RC circuit acts as an integrator if ϕ reaches near to 90° .

$$\phi = \tan^{-1} \left(\frac{2\pi}{T} \times RC \right)$$

if $RC \gg 15T$ then at $RC = 15T$

$$\phi = \tan^{-1} \left(\frac{2\pi}{T} \times 15T \right)$$

$$\phi = \tan^{-1}(30\pi)$$

$$\phi = \underline{\underline{89.4^\circ}}$$

If we define satisfactory integration, means that input sinusoid has been shifted at least 89.4° or 90° , then it is necessary that $RC > 15T$.

where T = Time period of the sine wave.

$$b) V_o = \frac{V_i^\circ}{1 + j\omega RC}$$

$$V_o = \frac{V_i^\circ}{1 + j(\text{large } \omega RC)}, \text{ since } \omega RC \gg 1, \text{ we can neglect } 1$$

$$V_o = \frac{V_i^\circ}{j(\text{large } \omega RC)}$$

$$V_o = \frac{-V_i^\circ j}{\omega RC}$$



$$\text{but } V_i^\circ = E_m \sin \omega t$$

$$V_o = \frac{-j E_m \sin \omega t}{\omega RC} = -\frac{E_m}{\omega RC} \cos \omega t, \text{ since } j \sin \omega t = \cos \omega t$$

$$\therefore \boxed{V_o = -\frac{E_m}{\omega RC} \cos \omega t}$$

2-17) A pulse is applied to a Low pass RC circuit. Prove by direct integration that the area under the pulse is the same as the area under the output waveform across the capacitor. Explain the result physically?

Sol:

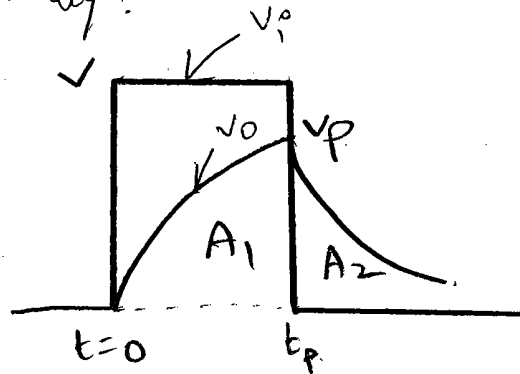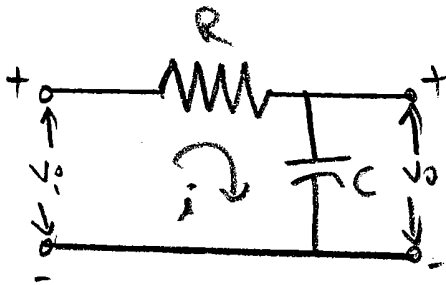

i) During pulse duration, $t < t_p$

Area under output waveform is A_1 ,

$$A_1 = \int_0^{t_p} V_p \cdot dt$$

$$A_1 = \int_0^{t_p} V [1 - e^{-t/RC}] dt$$

$$A_1 = V \left[\int_0^{t_p} 1 dt - \int_0^{t_p} e^{-t/RC} dt \right]$$

$$A_1 = V \left[t_p - \left(\frac{e^{-t/RC}}{-1/RC} \right)_0^{t_p} \right]$$

$$A_1 = V \left[t_p + RC (e^{-t_p/RC} - e^0) \right]$$

$$A_1 = V t_p + VRC [e^{-t_p/RC} - 1] \quad \text{--- (1)}$$

ii) At $t > t_p$:

area under the output waveform is

$$A_2 = \int_{t_p}^{\infty} V_p \cdot e^{-\frac{(t-t_p)}{RC}} dt$$

$$A_2 = \int_{t_p}^{\infty} V(1 - e^{-t_p/RC}) \cdot e^{-\frac{(t-t_p)}{RC}} dt$$

$$A_2 = V \int_{t_p}^{\infty} e^{-\frac{(t-t_p)}{RC}} - e^{-\frac{t_p}{RC}} \cdot e^{-\frac{(t-t_p)}{RC}} dt$$

$$A_2 = V \cdot \int_{t_p}^{\infty} e^{-\frac{t}{RC}} \cdot e^{\frac{t_p}{RC}} - e^{-\frac{t_p}{RC}} \cdot e^{-\frac{t}{RC}} \cdot e^{\frac{t_p}{RC}} dt$$

$$A_2 = V e^{\frac{t_p}{RC}} \int_{t_p}^{\infty} e^{-\frac{t}{RC}} dt$$

$$A_2 = V \int_{t_p}^{\infty} e^{-\frac{t}{RC}} \cdot e^{\frac{t_p}{RC}} - e^{-\frac{t}{RC}} \cdot 1 dt$$

$$= V e^{\frac{t_p}{RC}} \int_{t_p}^{\infty} e^{-\frac{t}{RC}} - \int_{t_p}^{\infty} e^{-\frac{t}{RC}} dt$$

$$= V e^{\frac{t_p}{RC}} \left[\frac{e^{-\frac{t}{RC}}}{-1/RC} \right]_{t_p}^{\infty} - V \left[\frac{e^{-\frac{t}{RC}}}{-1/RC} \right]_{t_p}^{\infty}$$

$$= -VRC e^{\frac{t_p}{RC}} \left(e^{-\infty} - e^{-\frac{t_p}{RC}} \right) + VRC \left(e^{-\infty} - e^{-\frac{t_p}{RC}} \right)$$

$$= +VRC e^{\frac{t_p}{RC}} e^{-\frac{t_p}{RC}} - VRC e^{-\frac{t_p}{RC}}$$


$$A_2 = VRC - VRC e^{-\frac{t_p}{RC}} \quad \text{--- (2)}$$


$$\text{Total Area} = A_1 + A_2 = V t_p + VRC \left(e^{-\frac{t_p}{RC}} - 1 \right) + VRC - VRC e^{-\frac{t_p}{RC}}$$

$$A = V t_p$$

which is equal to the area under the curve.

A diagram of a rectangular pulse. The vertical axis is labeled with a double-headed arrow and the number 1. The horizontal axis is labeled with a double-headed arrow and the symbol t_p .

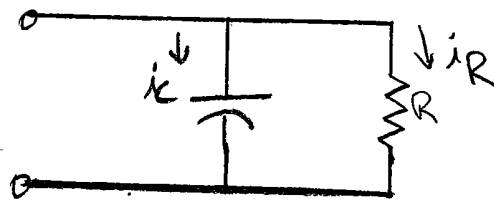

$$I_c = I_0 e^{-t_p/RC}, \quad t < t_p$$
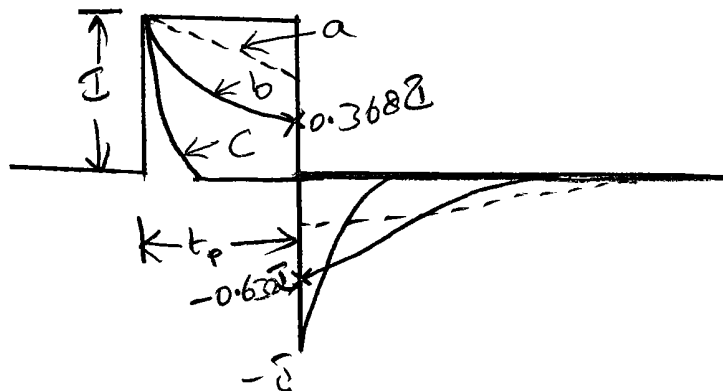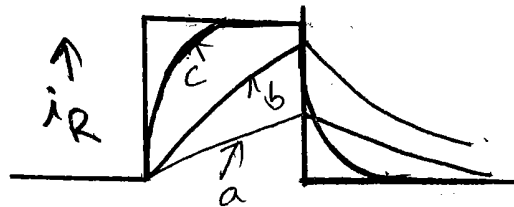
$$I_c = I_0 \left(e^{-t_p/RC} - 1 \right) \cdot e^{-\frac{(t-t_p)}{RC}}, \quad t > t_p$$


Repeat the above problem to sketch i_R waveform for different cases.

$$i_R = \mathcal{E}(1 - e^{-t/RC}), \quad 0 < t < t_p$$

$$i_R = \mathcal{E}(1 - e^{-t_p/RC}) \cdot e^{-\frac{(t-t_p)}{RC}}, \quad t > t_p$$



- ① A pulse generator with an output resistance $R_s = 500 \Omega$ is connected to an oscilloscope with an input capacitance $C_i = 30 \text{ pF}$. Determine the fastest rise time that can be displayed?

sol: $t_r = 2.2RC = 2.2 \times 500 \times 30 \times 10^{-12} = \underline{33 \text{ ns}}$

- ② A 10V step is switched on to a $50 \text{ k}\Omega$ resistor in series with a 500 pF capacitor. calculate a) the rise time of the capacitor voltage b) The time for the capacitor to charge to 63.2% of its maximum voltage and c) The time for the capacitor to be completely charged?

sol: Given data :

$$R = 50 \text{ k}\Omega$$

$$C = 500 \text{ pF}$$

a) $t_r = 2.2RC = 2.2 \times 50 \text{ k} \times 500 \text{ p} = \underline{55 \mu\text{s}}$

b) $\tau = RC = 50 \text{ k} \times 500 \text{ p} = \underline{25 \mu\text{s}}$

c) $5\tau = 5RC = 5 \times 25 \mu\text{s} = \underline{125 \mu\text{s}}$


RL circuits

→ Suppose the capacitor C and resistor R of the preceding sections are replaced by a resistor R' and an inductor L respectively, then if the time constant $\frac{L}{R'}$ equals the time constant RC , all the preceding results remain unchanged.

Disadvantage of Inductor at large time constant:

- 1) A large value of inductance is obtained only with an iron-core inductor which is physically large, heavy and expensive relative to the cost of a capacitor for a similar application.
- 2) The non-linear properties of the iron cause distortion, which may be undesirable.

High-pass RL circuit

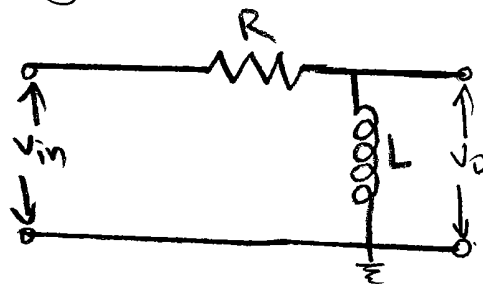

we know $X_L = 2\pi fL$


- i) At low frequencies, the inductance reactance decreases and the inductor acts as short-circuit. So, for lower frequency signals, the output voltage across inductor is zero.

$$V_o = 0$$

ii) At higher frequencies, the inductive reactance increases and the inductor acts as open circuit.
 $\therefore$ All high frequency signals are blocked and the signal appears at the output.

"As the higher frequency signals appear at the output, it is called High Pass RL circuit."

Step response of High Pass RL circuit :

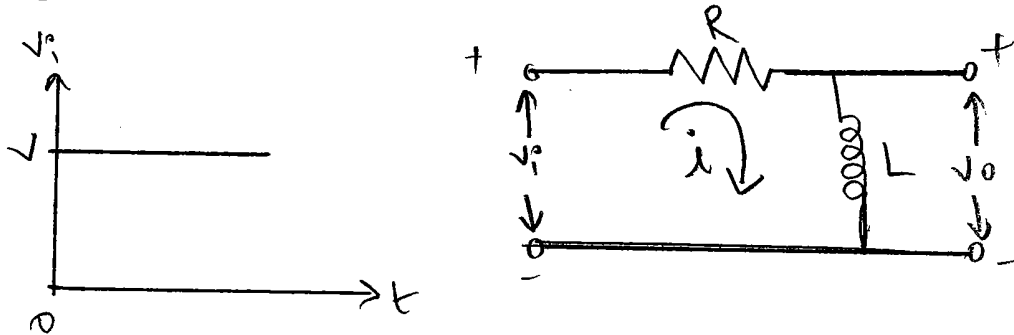

By applying KVL to the input Loop circuit & output

$$V_i = iR + L \frac{di}{dt} \quad \text{--- (1)}$$

$$V_o = L \frac{di}{dt} \quad \text{--- (2)}$$

divide equation (1) with L , we get

$$\frac{V_i}{L} = \frac{R}{L} i + \frac{di}{dt}$$

$$\left(1 + \frac{R}{L}\right) i = \frac{V_i}{L}$$

The solution of above differential equation is

formula $i \times \mathcal{E}.F = \int \frac{R \cdot V_i}{L} \times \mathcal{E}.f dt + K$ $\mathcal{E}.f = e^{\frac{R}{L}t} = e^{\frac{R}{L}t}$
--

$$i \times e^{\frac{R}{L}t} = \int \frac{V_0}{L} e^{\frac{R}{L}t} dt + K$$

$$i e^{\frac{R}{L}t} = \frac{V_0}{L} \frac{e^{\frac{R}{L}t}}{\frac{R}{L}} + K$$

$$i e^{\frac{R}{L}t} = \frac{V_0}{\cancel{L} \times \frac{R}{\cancel{L}}} e^{\frac{R}{L}t} + K$$

$$i e^{\frac{R}{L}t} = \frac{V_0}{R} e^{\frac{R}{L}t} + K$$

$$i = \frac{V_0}{R} e^{\frac{R}{L}t} \times e^{-\frac{R}{L}t} + K e^{-\frac{R}{L}t}$$

$$i = \frac{V_0}{R} + K \cdot e^{-\frac{R}{L}t}$$

to find the value of K , apply initial conditions

at $t=0$, the current in the inductor is zero, since the inductor does not allow sudden changes in currents.

$$\therefore \text{at } t=0, i=0$$

$$0 = \frac{V_0}{R} + K e^{-\frac{R}{L}t}$$

$$0 = \frac{V_0}{R} + K$$

$$K = -\frac{V_0}{R}$$

$$i = \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t}$$

$$i = \frac{V_0}{R} \left[1 - e^{-\frac{R}{L}t} \right] \quad \text{--- (3)}$$

substitute eqn (3) in eqn (2)

$$V_0 = L \frac{di}{dt}$$

$$V_0 = L \times \frac{d}{dt} \left[\frac{V_i}{R} \left(1 - e^{-R/Lt} \right) \right]$$

$$V_0 = L \times \frac{V_i}{R} \left(-e^{-R/Lt} \times \frac{-R}{Lt} \right)$$

$$V_0 = \cancel{L} \times \frac{V_i}{\cancel{R}} \times \frac{\cancel{R}}{\cancel{L}} \cdot e^{-R/Lt}$$

$$\therefore V_0 = V_i e^{-R/Lt}$$


where $V_i = V$, at $t > 0$

$$\therefore V_0 = V e^{-R/Lt}$$

Comparing this equation with output response of an High Pass RC circuit.

$$V_0 = V_{in} e^{-\frac{t}{RC}}$$

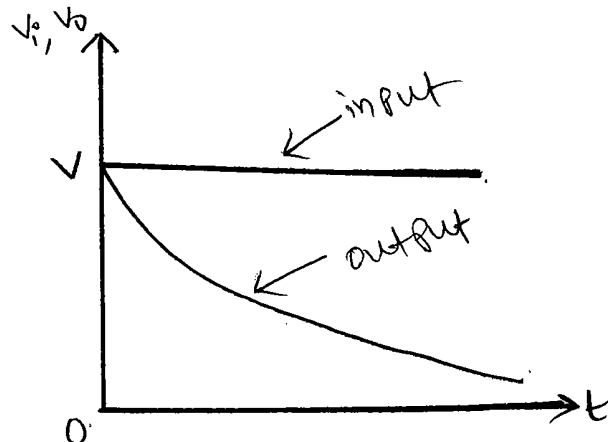$\therefore RC = \frac{L}{R}$ where $\frac{L}{R} =$ time constant of an High Pass RL circuit.



High pass RL circuit acts as differentiator

$$V_i = iR + L \frac{di}{dt}$$

$$\text{but } V_0 = L \frac{di}{dt}$$

$$V_i = iR + V_0$$

$$\text{but } i = \frac{V_{in}}{R} [1 - e^{-R/L t}]$$

$$\text{if } \frac{L}{R} \ll t$$

$$i = \frac{V_{in}}{R}$$

$$V_0 = L \frac{d}{dt} \frac{V_{in}}{R}$$

$$V_0 = \frac{L}{R} \frac{dV_{in}}{dt}$$

$$V_i = iR + L \frac{di}{dt}$$

$$V_0 = L \frac{di}{dt} \Rightarrow i = \int \frac{V_0}{L} dt$$

$$V_i = R \int \frac{V_0}{L} dt + V_0$$

Differentiating both sides

$$\frac{dV_i}{dt} = \frac{R}{L} V_0 + \frac{dV_0}{dt}$$


$\downarrow$ steady state response $\downarrow$ transient response

If $\frac{L}{R} \ll t$, transient response is negligible.

$$\therefore V_0 = \frac{L}{R} \frac{dV_i}{dt}$$

$\therefore$ output voltage is directly proportional to the derivative of the input.

Low-pass RL circuit:

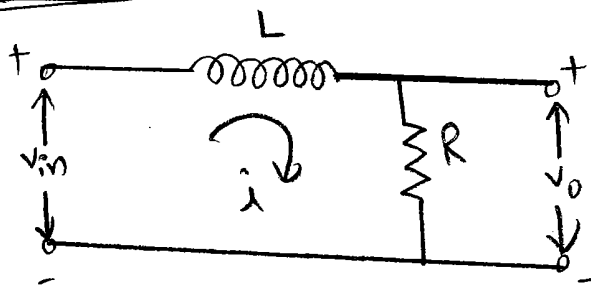

$$X_L = 2\pi fL$$



At Low frequencies (or D.C), the inductive reactance decreases and inductor acts as short circuit, so the low frequency signals will appear at the output.

At high frequencies, the inductive reactance increases and it opposes the signal to pass through it. Therefore output is zero.

$$V_o = 0$$

"As lower frequency signals appear at the output, it is called as Low Pass RL circuit."

step response of Low Pass RL circuit :

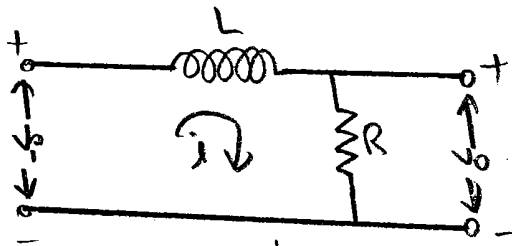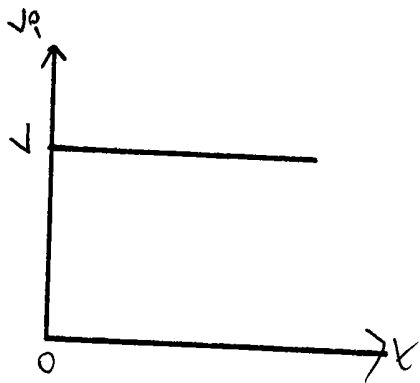


$$V_o = L \frac{di}{dt} + iR$$

$$\text{but } V_o = iR$$

$$\text{we know } i = \frac{V_{in}}{R} [1 - e^{-R/Lt}]$$

$$V_o = \frac{V_{in}}{R} [1 - e^{-R/Lt}] \times R$$

$$V_o = V_{in} (1 - e^{-R/Lt})$$

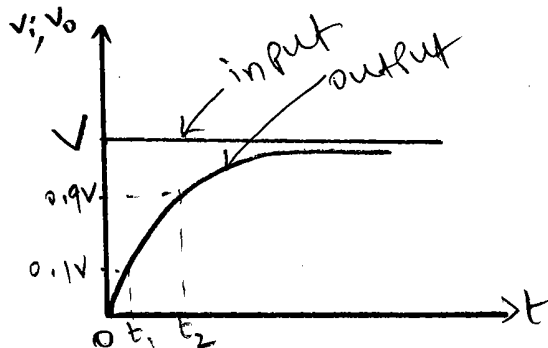

$$\text{Rise time } (t_r) = 2.2 \tau$$

$$\tau = 2.2 \times \frac{L}{R}$$

$$V_o = V_{in} (1 - e^{-R/Lt})$$

$$\text{at } t = t_1, V_o = 0.1V$$

$$0.1V = V (1 - e^{-\frac{R}{L}t_1})$$

$$e^{-\frac{R}{L}t_1} = 0.9$$

$$t_1 = 0.1 \frac{L}{R}$$

$$\text{at } t = t_2, V_o = 0.9V$$

$$0.9V = V (1 - e^{-\frac{R}{L}t_2})$$

$$e^{-\frac{R}{L}t_2} = 0.1$$

$$t_2 = 2.3 \frac{L}{R}$$

$$t_r = t_2 - t_1$$

$$t_r = 2.3 \frac{L}{R} - 0.1 \frac{L}{R}$$

$$\therefore t_r = 2.2 \frac{L}{R}$$

Low pass RL circuit acts as an Integrator:

$$V_i = L \frac{di}{dt} + V_o$$

$$V_o = iR$$

$$i = \frac{V_o}{R}$$

$$V_i = L \frac{d}{dt} \left(\frac{V_o}{R} \right) + iR$$

$$V_i = \frac{L}{R} \frac{dV_o}{dt} + iR$$

$\downarrow$ transient response steady state response
 $\downarrow$

If $\frac{L}{R} \gg t$, transient response is predominant

$$V_i = \frac{L}{R} \frac{dV_o}{dt}$$

$$V_o = \frac{R}{L} \int V_i dt$$

$\therefore$ The output voltage is directly proportional to the integral of the input.

Why RC Differentiator is Superior to RL Differentiator

- 1) Capacitor C is relatively cheaper than inductor L .
- 2) The size of capacitor is small when compared to inductor L , so space occupied by RC circuit is less than RL circuit.

$$3) \text{ Inductor } (L) = \frac{N^2}{S} = \frac{N^2}{\frac{4\pi\mu_0\mu_r}{l}A} = \frac{N^2 A \mu_0 \mu_r}{l}$$

L = Directly proportional to the number of turns N , so to have large inductance, number of turns must be increased and the inductance will be bulky.

L = Directly proportional to μ_r , so to have large inductance, relative permeability (μ_r) of the material should be more.

- 4) Inductance (L) is effected easily by rise in temperature.


As temperature increases, μ_r decreases, in turn L decreases.

As $\tau = \frac{L}{R}$, if L decreases, time constant (τ) decreases.

$\therefore$ Because of all the above reasons, RC Differentiator is mostly preferred over RL Differentiator circuit.

RLC circuits

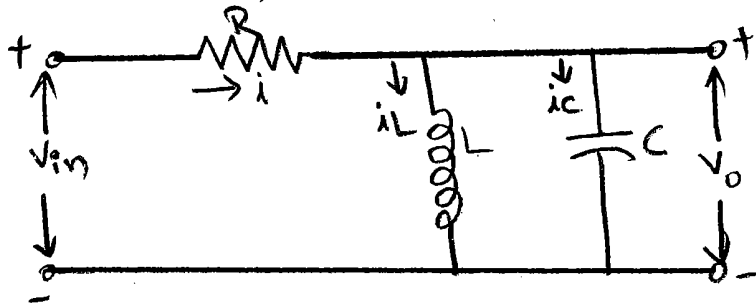→ if Capacitance C is the effect of coil winding capacitance, output capacitance and stray capacitance to ground. By including the effect of this capacitance into consideration, the circuit is shown below:



The above fig. shows a signal v_i applied through a resistor R to a parallel LC circuit.

If " i " is the current flowing through R and " i_L " is the current flowing through L and " i_C " is the current flowing through C .

$$\text{then } i = i_L + i_C$$

$$\text{but } i_L = \frac{1}{L} \int v_o dt$$

$$i_C = C \frac{dv_o}{dt}$$

$$i = \frac{1}{L} \int v_o dt + C \frac{dv_o}{dt} \quad \text{--- (1)}$$

$$v_{in} = iR + v_o$$

$$v_{in} = \left[\frac{1}{L} \int v_o dt + C \frac{dv_o}{dt} \right] R + v_o$$

$$v_{in} = \frac{R}{L} \int v_o dt + RC \frac{dv_o}{dt} + v_o \quad \text{--- (2)}$$

→ By applying step input to RLC circuit and differentiate above eqn (2) with respect to ' t ', we get

$$\frac{dV_{in}}{dt} = \frac{R}{L} V_0 + RC \frac{d^2 V_0}{dt^2} + \frac{dV_0}{dt}$$

$$\text{but } \frac{dV_{in}}{dt} = \frac{dV}{dt} = 0$$

$$0 = \frac{R}{L} V_0 + RC \frac{d^2 V_0}{dt^2} + \frac{dV_0}{dt}$$

$$\left(D^2 RC + D + \frac{R}{L} \right) V_0 = 0$$

where $D^2 RC + D + \frac{R}{L}$ is called as characteristic equation.

The roots of the characteristic equation are.

$$\text{roots} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\text{where } a = RC, \quad b = 1, \quad c = \frac{R}{L}$$

$$s_{1,2} = \frac{-1 \pm \sqrt{1^2 - 4 \times RC \times \frac{R}{L}}}{2RC}$$

$$s_{1,2} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{4RC \times \frac{R}{L}}{(2RC)^2}}$$

$$s_{1,2} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{\cancel{4} \cancel{R} \times \frac{R}{L}}{\cancel{4} \cancel{R}^2 \cancel{C}^2}}$$

$$s_{1,2} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\text{if } K = \text{Damping Constant} = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$f_0 = \text{Natural frequency or frequency of undamped oscillations} = \frac{1}{2\pi\sqrt{LC}}$$

$$T_0 = \text{resonant or undamped time period} = 2\pi\sqrt{LC}$$

$$K = \frac{1}{2R} \sqrt{\frac{L}{C}}, \quad T_0 = 2\pi \sqrt{LC}$$

$$\frac{K}{T_0} = \frac{1}{2R} \sqrt{\frac{L}{C}} \times \frac{1}{2\pi \sqrt{LC}}$$

$$\frac{K}{T_0} = \frac{1}{4\pi R} \sqrt{\frac{K}{C}} \times \frac{1}{\sqrt{KC}}$$

$$\frac{K}{T_0} = \frac{1}{4\pi RC}$$

$$S_{1,2} = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4R^2C^2} - \frac{1}{LC}}$$

$$S_{1,2} = -\frac{2\pi K}{T_0} \pm \sqrt{\frac{4\pi^2 K^2}{T_0^2} - \frac{4\pi^2}{T_0^2}}$$

$$S_{1,2} = -\frac{2\pi K}{T_0} \pm \frac{2\pi}{T_0} \sqrt{K^2 - 1}$$

$$S_{1,2} = -\frac{2\pi K}{T_0} \pm \frac{2\pi}{T_0} \sqrt{1-K^2}$$

$$S_{1,2} = -\frac{2\pi K}{T_0} \pm j \frac{2\pi}{T_0} \sqrt{1-K^2}$$

$$\frac{2\pi K}{T_0} = \cancel{2\pi} \times \frac{1}{\cancel{4\pi} RC}$$

$$\frac{2\pi K}{T_0} = \frac{1}{2RC}$$

$$\frac{4\pi^2 K^2}{T_0^2} = \frac{\cancel{4\pi^2} \times 1}{\cancel{4\pi^2} \cancel{R^2} C^2}$$

$$\frac{4\pi^2 K^2}{T_0^2} = \frac{1}{4R^2 C^2}$$

$$\frac{4\pi^2}{T_0^2} = \frac{\cancel{4\pi^2}}{\cancel{4\pi^2} (LC)^2}$$

$$\frac{4\pi^2}{T_0^2} = \frac{1}{LC}$$

$$S_1 = -\frac{2\pi K}{T_0} + j \frac{2\pi}{T_0} \sqrt{1-K^2}, \quad S_2 = -\frac{2\pi K}{T_0} - j \frac{2\pi}{T_0} \sqrt{1-K^2}$$

1) If $K=0$, $S_1 = +j \frac{2\pi}{T_0}$ and $S_2 = -j \frac{2\pi}{T_0}$, both roots S_1 and S_2 are imaginary and the response is an "undamped sinusoid of time period T_0 ".



2) If $K=1$, $S_1 = -\frac{2\pi}{T_0}$ and $S_2 = -\frac{2\pi}{T_0}$, the two roots are real and equal which represents "critical damping".

3) if $K > 1$, the circuit becomes "over damped" and there are no oscillations of the output.

4) if $K < 1$, the output is a sinusoid whose amplitude progressively decays with time. This represents "under damped response".

→ Let the forcing function (input) be a step response of magnitude V . Let it be assumed that the circuit is relaxed at $t = 0$ i.e. there is no initial inductor current or initial capacitor voltage.

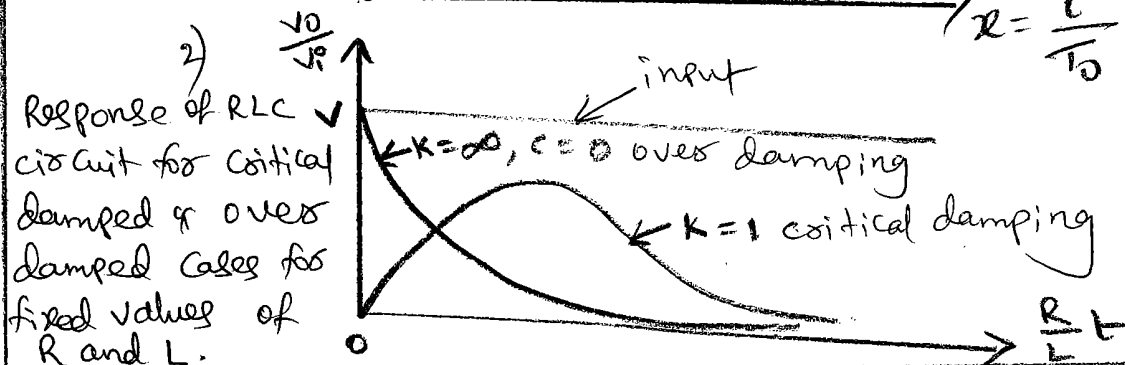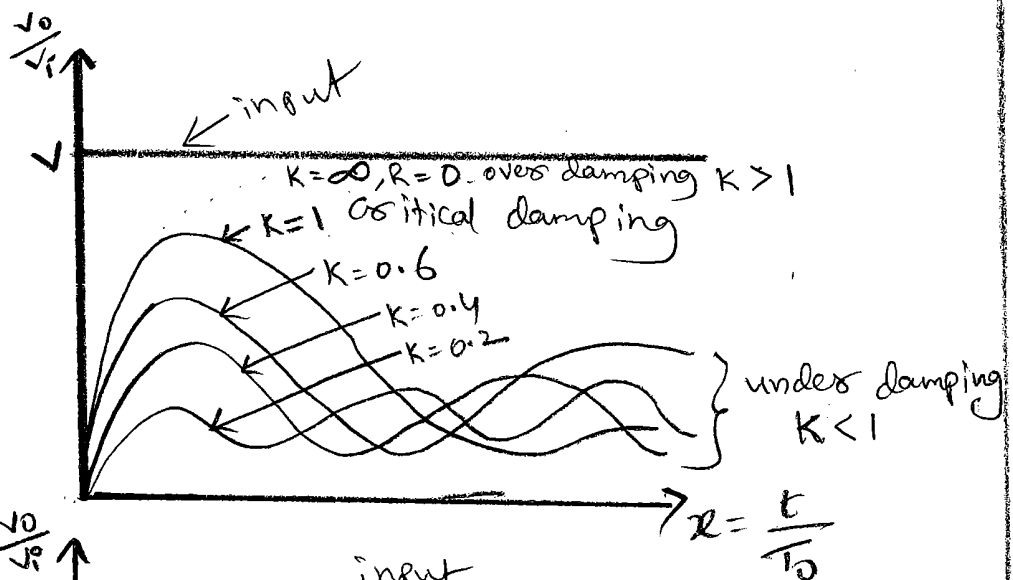1) Response of RLC circuit for critical damping, over damping under damping cases for a fixed value of L and C are shown below when the input is a step signal:



1) undamped

If $K=0$, roots are purely imaginary $s_1 = +j\frac{2\pi}{T_0}$, $s_2 = -j\frac{2\pi}{T_0}$

then
$$v_0 = c_1 \cos \frac{2\pi}{T_0} t + c_2 \sin \frac{2\pi}{T_0} t \quad \text{--- (1)}$$

To find c_1 and c_2 values we have to apply initial conditions.

i.e., at $t=0$, $v_0=0$

$$0 = c_1 \times 1 + c_2 \times 0 \quad \left(\begin{array}{l} \cos 2\pi t = 1 \\ \sin 2\pi t = 0 \end{array} \right)$$

$$c_1 = 0$$

Differentiate eqn (1) with respect to t

$$\frac{dv_0}{dt} = -c_1 \sin \frac{2\pi}{T_0} t \times \frac{2\pi}{T_0} + c_2 \cos \frac{2\pi}{T_0} t \times \frac{2\pi}{T_0}$$

Since differentiation of $\cos$ is $-\sin$
 $\sin$ is $+\cos$

Integration of $\cos$ is $+\sin$
 $\sin$ is $-\cos$

at $t=0$, c_1 is 0 and acts as short circuit

$$\frac{dv_0}{dt} = c_2 \cos \frac{2\pi}{T_0} t \times \frac{2\pi}{T_0}$$

$$V_{in} = iR$$

$$i = \frac{V_{in}}{R}$$

but $i = C \frac{dv_0}{dt}$

$$\frac{dv_0}{dt} = \frac{i}{C} = \frac{V_{in}}{RC}$$

by substituting in the above equation, we get

$$\frac{V_{in}}{RC} = C_2 \times 1 \times \frac{2\pi}{T_0}, \text{ since } \cos \frac{2\pi t}{T_0} = 1$$

$$C_2 = \frac{V_{in} T_0}{2\pi RC}$$

By substituting C_1 and C_2 values in equation ①, we get

$$V_0 = \frac{V_{in}}{2\pi RC} T_0 \cdot \sin \frac{2\pi}{T_0} t$$

2) critical damping

If $\zeta = 1$, $s_1 = s_2 = -\frac{2\pi}{T_0}$ the roots are real and equal

$$V_0 = (C_1 + C_2 t) e^{-\frac{2\pi}{T_0} t} \quad \text{--- ①}$$

at $t=0$, $V_0=0$

formula:

$$u v = u dv + v du$$

$$\therefore C_1 = 0$$

$$\text{let } C_1 + C_2 t = v$$

$$e^{-\frac{2\pi}{T_0} t} = u$$

Differentiate eqn ① with respect to 't' on both sides

$$\frac{dV_0}{dt} = e^{-\frac{2\pi}{T_0} t} \frac{d}{dt} (C_1 + C_2 t) + (C_1 + C_2 t) \frac{d}{dt} e^{-\frac{2\pi}{T_0} t}$$

$$\frac{dV_0}{dt} = C_2 e^{-\frac{2\pi}{T_0} t} + (C_1 + C_2 t) e^{-\frac{2\pi}{T_0} t} \times -\frac{2\pi}{T_0}$$

Applying initial conditions

$$\text{at } t=0, \frac{dV_0}{dt} = \frac{V_{in}}{RC}$$

$$\therefore \frac{V_{in}}{RC} = c_2 e^{-0} + (0+0) e^{-0}$$

$$\frac{V_{in}}{RC} = c_2$$

Substituting c_1 and c_2 values in eqn (1)

$$V_o = \left(0 + \frac{V_{in}}{RC} t \right) e^{-\frac{2\pi}{T_0} t}$$

$$V_o = \frac{V_{in}}{RC} \cdot t \cdot e^{-\frac{2\pi}{T_0} t} \quad \text{--- (2)}$$

we know $\frac{K}{T_0} = \frac{1}{4\pi RC}$

$$\boxed{\begin{aligned} 4\pi RC K &= \frac{1}{T_0} \\ \pi RC &= \frac{1}{4T_0} \end{aligned}}$$

$$\frac{1}{RC} = \frac{4\pi K}{T_0}$$

but $K = 1$

$$\therefore \frac{1}{RC} = \frac{4\pi}{T_0}$$

$$V_o = V_{in} \times \frac{4\pi}{T_0} t \cdot e^{-\frac{2\pi}{T_0} t}$$

, $V_{in} = V$

let $x = \frac{t}{T_0}$

$$\boxed{\frac{V_o}{V} = 4\pi x \cdot e^{-2\pi x}}$$

we know

$$K = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

and $T_0 = 2\pi\sqrt{LC}$

squaring on both sides

$$\frac{K}{T_0} = \frac{1}{4\pi RC}$$

$$K^2 = \frac{1}{4R^2} \cdot \frac{L}{C}$$

if $K=1$

if $K=1$

$$T_0 = 4\pi RC$$

$$1 = \frac{L}{4R^2 C}$$

$$T_0 = 4\pi \times \frac{L}{4R}$$

$$RC = \frac{L}{4R}$$

$$T_0 = \frac{\pi L}{R}$$


$$\frac{1}{RC} = \frac{4R}{L}$$

sub these values in equation (2)

$$V_0 = \frac{V_{in}}{RC} t e^{-\frac{2\pi}{T_0} t}$$

$$V_0 = \frac{4R}{L} \cdot V_{in} t e^{-\frac{2\pi R}{L} t}$$
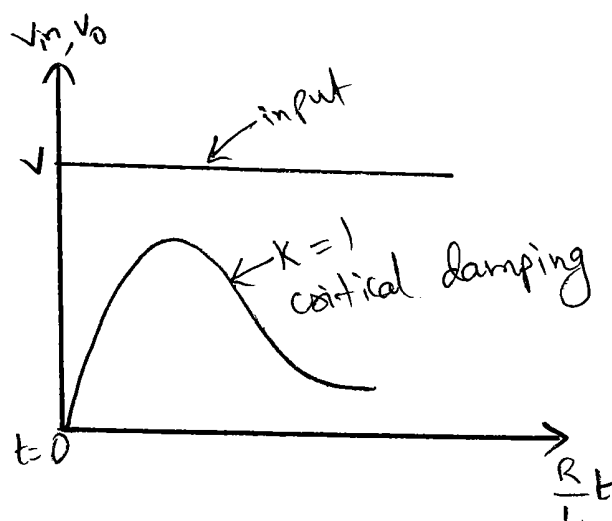
$$V_0 = \left(\frac{4R}{L} \right) V_{in} t e^{-\frac{2R}{L} t}$$



3)

over dampingif $k > 1$, we get over damping

$$s_{1,2} = -\frac{2\pi}{T_0} K \pm \frac{2\pi}{T_0} \sqrt{k^2 - 1}$$

$$s_{1,2} = -\frac{2\pi}{T_0} K \pm \frac{2\pi}{T_0} K \sqrt{1 - \frac{1}{k^2}}$$

$$s_{1,2} = -\frac{2\pi}{T_0} K \pm \frac{2\pi}{T_0} K \left(1 - \frac{1}{k^2}\right)^{1/2}$$

formula: Using Binomial expansion

$$\text{let } \frac{1}{k^2} = x, \quad \frac{1}{2} = n.$$

$$(1-x)^n = 1 - \frac{n x}{1!} + \frac{n(n-1)}{2!} x^2 - \dots$$

$$s_{1,2} = -\frac{2\pi}{T_0} K \pm \frac{2\pi K}{T_0} \left[1 - \frac{\frac{1}{2} \cdot \frac{1}{k^2}}{1!} + \frac{\frac{1}{2}(\frac{1}{2}-1)}{2!} \left(\frac{1}{k^2}\right)^2 - \dots \right]$$

if $k > 1$, $\frac{1}{k^2} \ll 1$, so we can ignore

$$s_{1,2} = -\frac{2\pi K}{T_0} \pm \frac{2\pi K}{T_0} \left[1 - \frac{1}{2k^2} \right]$$

let us solve the two roots

$$s_1 = -\frac{2\pi K}{T_0} + \frac{2\pi K}{T_0} \left(1 - \frac{1}{2k^2}\right)$$

$$s_1 = -\cancel{\frac{2\pi K}{T_0}} + \cancel{\frac{2\pi K}{T_0}} - \cancel{\frac{2\pi K}{T_0}} \times \frac{1}{2k^2}$$

$$\therefore s_1 = -\frac{\pi}{KT_0}$$

$$S_2 = \frac{-2\pi K}{T_0} - \frac{2\pi K}{T_0} \left[1 - \frac{1}{2k^2} \right]$$

$$S_2 = \frac{-2\pi K}{T_0} \left[1 + 1 - \frac{1}{2k^2} \right]$$

$$S_2 = \frac{-2\pi K}{T_0} \left[2 - \frac{1}{2k^2} \right]$$

$$S_2 = \frac{-4\pi K}{T_0} + \frac{2\pi K}{T_0} \times \frac{1}{2k^2}$$

if $k > 1$, $\frac{1}{k^2} \ll 1$ so when compared to 2, $\frac{1}{2k^2}$ can be ignored.

$$\therefore S_2 = \frac{-4\pi K}{T_0}$$

two roots are real and unequal.

$$\therefore v_0 = C_1 e^{\frac{-\pi}{KT_0} t} + C_2 e^{\frac{-4\pi K}{T_0} t} \quad \text{--- (1)}$$

$$\text{at } t=0, v_0=0$$

$$0 = C_1 e^0 + C_2 e^0$$

$$0 = C_1 + C_2$$

$$C_1 = -C_2 \quad \text{--- (2)}$$

Differentiate equation (1) with respect to t .

$$\frac{dv_0}{dt} = C_1 e^{\frac{-\pi}{KT_0} t} \times \frac{-\pi}{KT_0} + C_2 e^{\frac{-4\pi K}{T_0} t} \times \frac{-4\pi K}{T_0}$$

$$\frac{dv_0}{dt} = -\pi_0$$

$$\frac{dV_0}{dt} = -\frac{\pi}{KT_0} \cdot C_1 e^{-\frac{\pi}{KT_0} t} - \frac{4\pi}{T_0} K C_2 e^{-\frac{4\pi K}{T_0} t}$$

$$\text{at } t=0, \frac{dV_0}{dt} = \frac{V_{in}}{RC}$$

$$\frac{V_{in}}{RC} = -\frac{\pi}{KT_0} C_1 e^{-0} - \frac{4\pi}{T_0} K C_2 e^{-0}$$

$$\frac{V_{in}}{RC} = -\frac{\pi}{KT_0} C_1 - \frac{4\pi}{T_0} K C_2$$

$$\text{Sub } C_1 = -C_2$$

$$\frac{V_{in}}{RC} = \frac{\pi C_2}{KT_0} - \frac{4\pi}{T_0} K C_2$$

$$\frac{V_{in}}{RC} = \frac{\pi}{T_0} C_2 \left[\frac{1}{K} - 4K \right]$$

$$C_2 = \frac{V_{in} T_0}{RC \pi \left(\frac{1}{K} - 4K \right)}$$

$$\text{but } \frac{K}{T_0} = \frac{1}{4\pi RC}$$

$$4\pi RC K = T_0$$

$$\pi RC = \frac{T_0}{4K}$$

$$\frac{1}{\pi RC} = \frac{4K}{T_0}$$

$$C_2 = \frac{V_{in} 4K \cancel{T_0}}{\cancel{T_0} \left(\frac{1}{K} - 4K \right)}$$

$$C_2 = \frac{V_{in} 4K}{-4K \left(1 - \frac{1}{4K^2} \right)}$$

$$C_2 = \frac{-V_{in}}{1 - \frac{1}{4k^2}}$$

if $k \gg 1$, $\frac{1}{4k^2} \ll 1$ so when compared to 1, $\frac{1}{4k^2}$ we can neglect.

$$\therefore C_2 = -V_{in}, \quad C_1 = V_{in}$$

Substitute C_1 and C_2 values in equation (1)

$$V_0 = C_1 e^{\frac{-\pi}{KT_0} t} + C_2 e^{\frac{-4\pi}{T_0} k t}$$

$$V_0 = V_{in} e^{\frac{-\pi}{KT_0} t} - V_{in} e^{\frac{-4\pi k}{T_0} t}$$

$$V_0 = V_{in} e^{\frac{-\pi}{KT_0} t} - V_{in} e^{\frac{-\pi}{KT_0} t (4k^2)}$$

$$k \gg 1 \text{ means } \frac{1}{k} < 1$$

So the first term is less than 1 except at $t=0$.
The second term is equal to the first term raised to the power $4k^2$. Hence, the second term is negligible compared with the first term except at near the origin.

$$\therefore V_0 \approx V_{in} e^{\frac{-\pi x t}{KT_0}} \quad \text{--- (3)}$$

$$\text{but } KT_0 = \frac{1}{2R} \sqrt{\frac{L}{C}} \times 2\pi \sqrt{LC}$$

$$KT_0 = \frac{\pi L}{R}$$

$$V_0 \approx V_{in} e^{\frac{-\pi R}{\pi L} t}$$

$$V_0 \approx V_{in} e^{\frac{-R}{L} t}$$

from equation (3)

$$V_0 \simeq V_{in} e^{-\frac{\pi}{KT_0} t}$$

we know $\frac{t}{T_0} = x$

$$\therefore V_0 \simeq V_{in} e^{-\frac{\pi x}{K}}$$



input and output waveforms are shown below:

$$K = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

for $K > 1$

if $R=0$ or $C=0$

then $K = \infty$

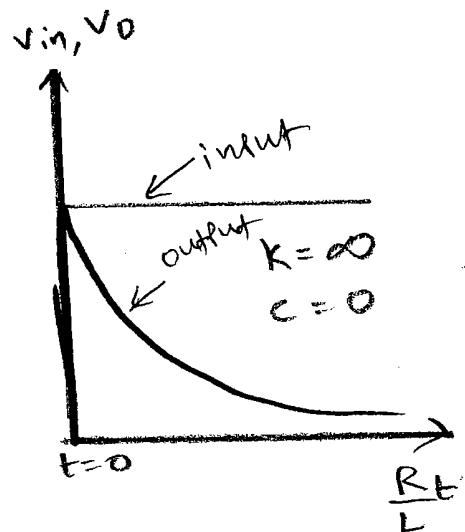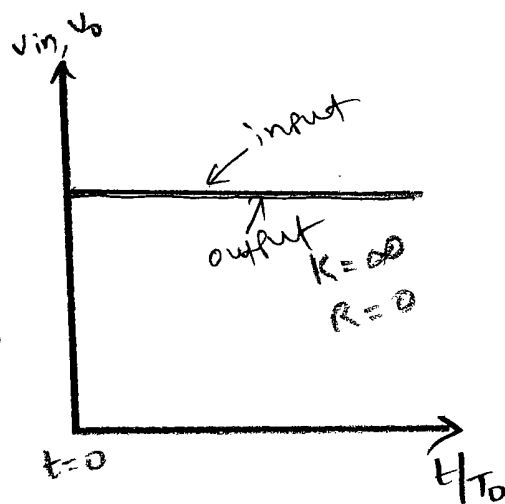

4)

Under damping.

$$s_{1,2} = -\frac{2\pi K}{T_0} \pm j \frac{2\pi}{T_0} \sqrt{1-K^2}$$

Since the roots are complex, so

$$V_0 = e^{-\frac{2\pi K}{T_0} t} \left[C_1 \cos \frac{2\pi}{T_0} \sqrt{1-K^2} \cdot t + C_2 \sin \frac{2\pi}{T_0} \sqrt{1-K^2} \cdot t \right] \quad \text{--- (1)}$$

Applying initial conditions at $t=0$, $V_0 = 0$.

$$0 = e^{-0} [C_1 \cos 0 + C_2 \sin 0]$$

$$0 = e^{-0} [C_1 + 0]$$

$$C_1 = 0$$

Differentiating equation (1) with respect to 't'.

$$\frac{dV_0}{dt} = e^{-\frac{2\pi}{T_0} k \cdot t} \left[-C_1 \sin \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t \times \frac{2\pi}{T_0} \sqrt{1-k^2} + C_2 \cos \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t \times \frac{2\pi}{T_0} \sqrt{1-k^2} \right] + e^{-\frac{2\pi}{T_0} k \cdot t} \times -\frac{2\pi}{T_0} k \left[C_1 \cos \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t + C_2 \sin \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t \right]$$

formula:

$$\frac{d}{dt}[uv] = u \frac{dv}{dt} + v \frac{du}{dt}$$

$$\text{let } u = e^{-\frac{2\pi}{T_0} k \cdot t}, \quad v = C_1 \cos \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t + C_2 \sin \frac{2\pi}{T_0} \sqrt{1-k^2} \cdot t$$

$$\text{at } t=0, \quad \frac{dV_0}{dt} = \frac{V_{in}}{RC}$$

~~$$\frac{V_{in}}{RC} = e^{-0} \left[-C_1 \sin 0 + C_2 \cos 0 \right] + e^{-0} \times -\frac{2\pi}{T_0} k \left[C_1 \cos 0 + C_2 \sin 0 \right]$$~~

~~$$\frac{V_{in}}{RC} = 1 \left[0 + C_2 \right] + 1 \times -\frac{2\pi}{T_0} k \left[C_1 + 0 \right]$$~~

$$\frac{V_{in}}{RC} = e^{-0} \left[-C_1 \sin 0 \times \frac{2\pi}{T_0} \sqrt{1-k^2} + C_2 \cos 0 \times \frac{2\pi}{T_0} \sqrt{1-k^2} \right] + e^{-0} \times -\frac{2\pi}{T_0} k \left[C_1 \cos 0 + C_2 \sin 0 \right]$$

$$\frac{V_{in}}{RC} = 1 \left[0 + C_2 \frac{2\pi}{T_0} \sqrt{1-k^2} \right] + 1 \times -\frac{2\pi}{T_0} k (C_1)$$

$$\text{but } C_1 = 0$$

$$\frac{V_{in}}{RC} = C_2 \times \frac{2\pi}{T_0} \sqrt{1-k^2}$$

$$C_2 = \frac{T_0 \times V_{in}}{2\pi\sqrt{1-k^2} \times RC}$$

$$\text{but } \frac{1}{RC} = \frac{4\pi K}{T_0}$$

$$C_2 = \frac{T_0}{\cancel{2\pi}\sqrt{1-k^2}} \times V_{in} \times \frac{\cancel{4\pi}K}{T_0}$$

$$\frac{K}{T_0} = \frac{1}{4\pi RC}$$

$$\frac{1}{RC} = \frac{4\pi K}{T_0}$$

$$C_2 = \frac{2V_{in} K}{\sqrt{1-k^2}}$$

Substitute the values of C_1 and C_2 in equation (1)

$$V_0 = e^{-\frac{2\pi}{T_0} K t} \left[C_1 \cos \frac{2\pi}{T_0} \sqrt{1-k^2} t + C_2 \sin \frac{2\pi}{T_0} \sqrt{1-k^2} t \right]$$

$$V_0 = e^{-\frac{2\pi}{T_0} K t} \left[0 + \frac{2K}{\sqrt{1-k^2}} V_{in} \sin \frac{2\pi}{T_0} \sqrt{1-k^2} t \right]$$

$$V_0 = e^{-\frac{2\pi}{T_0} K t} \cdot \frac{2K}{\sqrt{1-k^2}} \cdot V_{in} \cdot \sin \frac{2\pi}{T_0} \sqrt{1-k^2} t$$

$$\frac{V_0}{V_{in}} = \frac{2K}{\sqrt{1-k^2}} \cdot e^{-2\pi K x} \sin 2\pi \sqrt{1-k^2} \cdot x$$

$$\text{where } x = \frac{t}{T_0}$$

$\therefore$ for $K < 1$, the output is a sinusoidal whose amplitude progressively decays with time. This represents under damped response.

Ring circuit:

→ Uses:

- 1) To generate a sequence of pulses regularly spaced in time.
- 2) It is used in many timing operations.

→ Def:

"The circuit which gives nearly undamped oscillation ($K < 1$ or $K = 0$) for a given step input voltage is called as Ringing circuit."

→ If K is small the circuit will ring for many cycles.

→ If Q is the Quality factor of a parallel RLC circuit and K is the damping factor.

we know

$$\text{Quality factor } (Q) = \omega_0 RC$$

$$Q = \frac{2\pi}{T_0} RC, \text{ where } \omega_0 = 2\pi f_0 = \frac{2\pi}{T_0}$$

$$\text{but } \frac{K}{T_0} = \frac{1}{4\pi RC} \Rightarrow RC = \frac{T_0}{4\pi K}$$

$$Q = \frac{2\pi}{T_0} \times \frac{T_0}{4\pi K}$$

$$Q = \frac{1}{2K} \quad \text{--- (1)} \Rightarrow 2KQ = 1$$

If k is small, Q is large and the circuit will oscillate (ring) for more number of cycles.

for $k < 1$

$$V_0 = \frac{2k}{\sqrt{1-k^2}} \cdot V_{in} \cdot e^{-\frac{2\pi \cdot t \cdot k}{T_0}} \cdot \sin \sqrt{1-k^2} \cdot \frac{2\pi}{T_0} \cdot t$$

$\therefore$ "It is required to find a value of a circuit which is to ring for a given number N cycles before the amplitude reduces to $1/e$ ($e^{-1} = 37\%$) of its initial value".

$$\frac{2\pi}{T_0} k \cdot t = 1$$

given N no. of cycles

$$t = NT_0$$

$$\frac{2\pi}{T_0} \cdot k \cdot NT_0 = 1$$


$$2\pi k N = 1 \quad \text{--- (2)}$$

equate (1) and (2)

$$2\pi k N = 2\pi Q$$

$$\therefore \boxed{Q = \pi N, \quad N = \frac{Q}{\pi}}$$

where N = number of cycles (ringing)

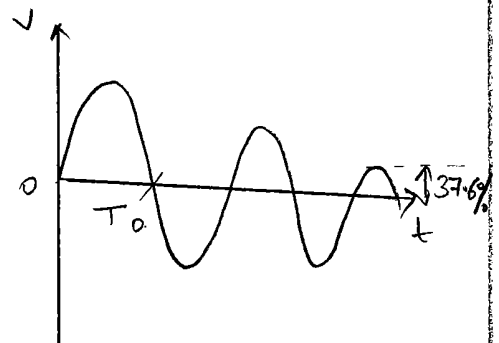


Ex: If $Q=12$, then $N = \frac{12}{3.14} \approx 4$ cycles of oscillation

$\therefore$ The circuit will ring for 4 cycles before the amplitude reduces to 37% ($\frac{1}{e} = e^{-1}$) of its initial value.

Attenuators

→ "Attenuator is one which is used to reduce the amplitude of the signal waveform".

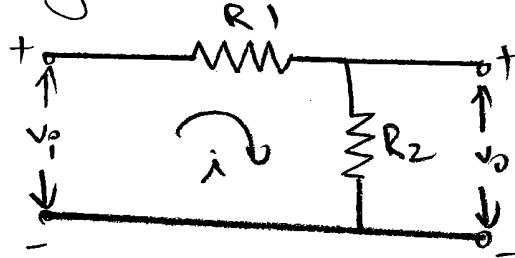→ An attenuator is basically a resistance potential divider arrangement as shown below:



$$V_o = iR_2$$

$$\text{but } i = \frac{V_p}{R_1 + R_2}$$

$$V_o = \frac{R_2 \cdot V_p}{R_1 + R_2}$$


$$V_o = aV_p$$

$$\text{where } a = \frac{R_2}{R_1 + R_2}$$


→ The simple resistance combination would multiply the input signal by the ratio $a = \frac{R_2}{R_1 + R_2}$ which is independent of frequency.

→ Theoretically the waveform of the input signal is preserved, although its amplitude has changed. Thus there is no distortion produced due to the transmission of the signal through the attenuator.

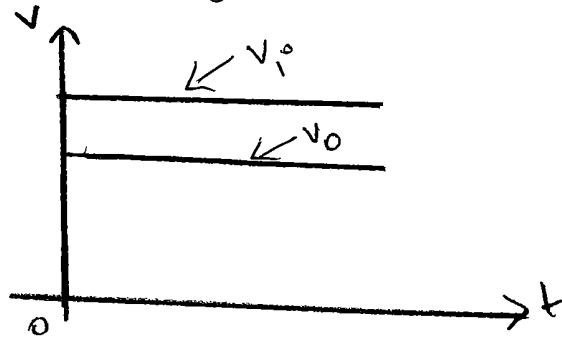The input and output waveforms are shown.
Assuming the input signal to be a step voltage.



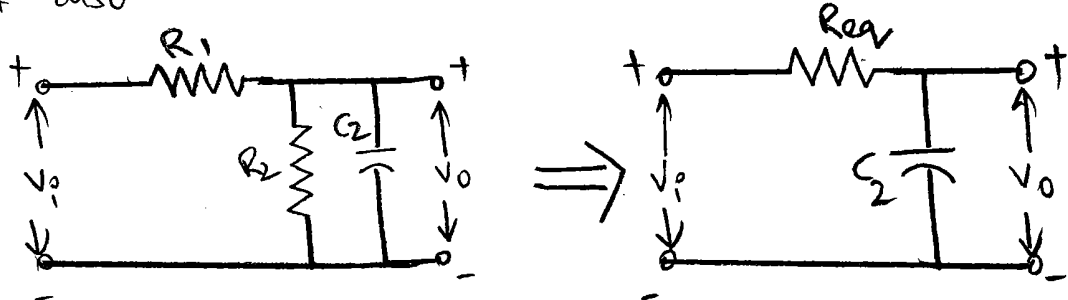→ The attenuator circuit is considered to be a purely resistive circuit. But in practice it is not so. A distributed capacitance C_2 shunting the resistance R_2 must also be taken into consideration.



The attenuation now is not independent of frequency.

R_{eq} = Parallel combination of R_1 and R_2 .

→ R_1 and R_2 values to be large because the input impedance of the attenuator may be large enough to prevent loading down the input signal.

So, if R_1 and R_2 are large, the rise time

$$t_r = \left(\frac{R_1 R_2}{R_1 + R_2} \right) C_2 \text{ will be large}$$

and a large rise time is normally unacceptable, and also the effect of the capacitance C_2 is to distort the wave shape of the input signal.

ex: If $R_1 = R_2 = 1\text{M}\Omega$, $C_2 = 15\text{pF}$

the $t_0 = 2.2 \times 0.5\text{M} \times 15\text{p} = 16.5\mu\text{sec}$

$\therefore$ The undesirable effect of this is normally overcome by providing necessary and adequate compensation.

$\Rightarrow$ The attenuator may be compensated, so that its attenuation is once again independent of the frequency by shunting R_1 by a capacitor C_1 as shown below:


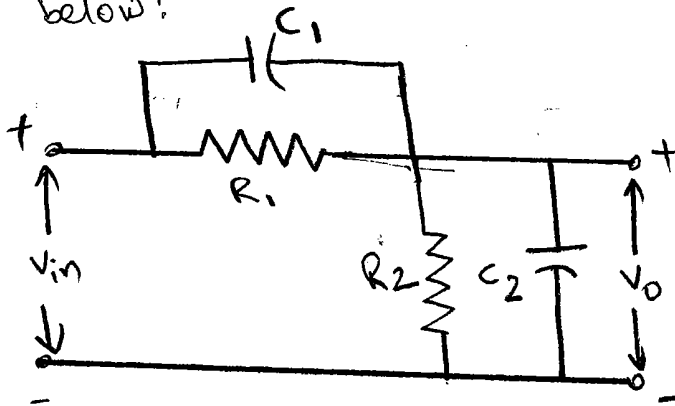


fig: compensated attenuator

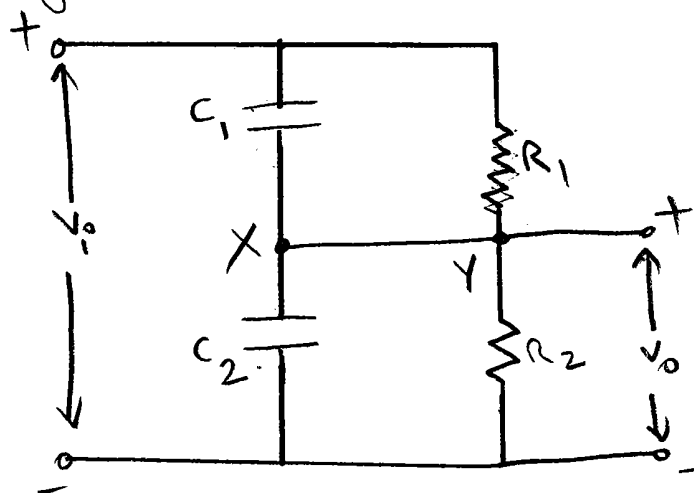$\rightarrow$ The above compensated attenuator is redrawn as a bridge which is shown below:



→ In the above fig. the two resistors and two capacitors may be viewed as four arms of the bridge.

→ If $R_1 C_1 = R_2 C_2$, the bridge will be balanced and no current will flow in the branch

connecting the point X to the point Y.

→ For the purpose computing the output, the branch X-Y may be omitted and the output across R_2 is

$$\frac{R_2 V_i}{R_1 + R_2} = a V_i$$

independent of the frequency. The capacitor C_1 is the adjustable capacitor.

→ For final adjustment for compensation is made experimentally by the method of square-wave testing.

Response of attenuator to a step input:

Let us consider a step voltage input of amplitude V which changes abruptly by V at $t=0$.

As input changes abruptly, the voltage across C_1 and C_2 also changes abruptly, this happens

because at $t=0$, capacitor acts as short-circuit and a very large (ideally infinite) current flows through the capacitor for an infinitesimally small time. So, a finite charge $q = \int_0^{0^+} i(t) dt$ is delivered to each capacitor.

The voltage across $C_1 = \frac{q}{C_1}$

The voltage across $C_2 = \frac{q}{C_2}$

i) By applying KVL at $t=0^+$ i.e; immediately after the input signal is applied, the capacitor acts as short-circuit and hence resistors go out of the circuit.

input signal $V_i(0^+) = V_1 + V_2$

$$V_i(0^+) = \frac{q}{C_1} + \frac{q}{C_2}$$

$$V_i(0^+) = q \left(\frac{C_1 + C_2}{C_1 C_2} \right)$$

$$q = V_i(0^+) \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

The output voltage is

$$V_o(0^+) = \frac{q}{C_2} = \frac{V C_1 C_2}{(C_1 + C_2) C_2}, \text{ since } V_i(0^+) = V$$

$$\boxed{V_o(0^+) = \frac{V C_1}{C_1 + C_2}} \quad \text{--- (1)}$$

ii) at $t = \infty$

at this condition, steady state has been reached and the capacitor acts as open-circuit and final output voltage is determined by the resistors R_1, R_2

$$\therefore V_o(\infty) = i R_2$$

$$\text{but } i = \frac{V_i(\infty)}{R_1 + R_2}$$

$$\boxed{V_o(\infty) = \frac{R_2 V}{R_1 + R_2}} \quad \text{--- (2)}$$

perfect compensation is obtained if

$$V_o(0^+) = V_o(\infty)$$


$$\frac{\cancel{V} C_1}{C_1 + C_2} = \frac{\cancel{V} R_2}{R_1 + R_2}$$

$$R_1 C_1 + \cancel{R_2} \cancel{C_1} = \cancel{R_2} \cancel{C_1} + R_2 C_2$$

$$\therefore \boxed{\begin{aligned} R_1 C_1 &= R_2 C_2 \\ \text{or} \\ C_1 &= \frac{R_2 C_2}{R_1} = C_p \end{aligned}}$$

which is the balanced bridge condition is obtained for perfect compensation.

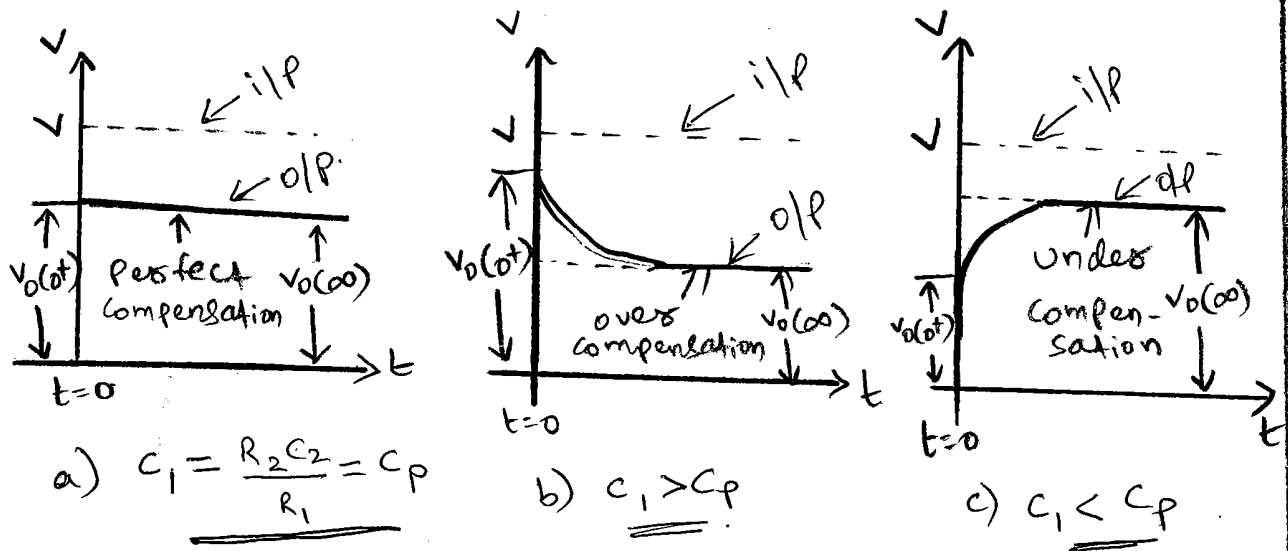The response of an attenuator to a step input is shown below:



Application of Attenuator as a Cathode ray oscilloscope probe:

To observe the waveform, the signal point of a circuit is connected to the input terminals of an oscilloscope. If the signal point is at far distance from CRO terminals and if the signal appears at a high impedance level, then shielded cable is used to connect the signal to the oscilloscope.

Shielding of the cable is necessary to isolate the input lead from stray fields. The capacitance looking into several feet of cable may be as high as 100 to 150 pF, this combination of high input capacitance together with the high output impedance of the signal source will make it impossible to make faithful observations of fast waveforms.

A probe assembly which uses shielded cable keeps the capacitance low as shown below.

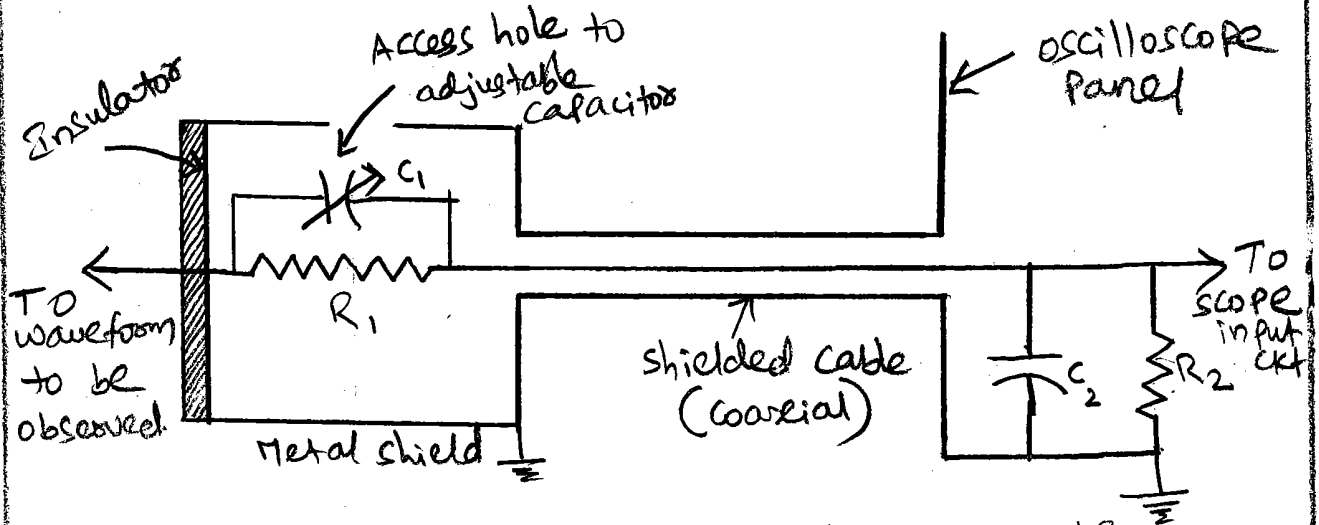


Fig: A Cathode-Ray oscilloscope probe

The attenuation introduced through use of the probe assembly is 10 (or) 20 and the input capacitance to the probe assembly is about 20 (or) 10 pF respectively.

Problems - Attenuators

(2-3) Compute and draw to scale the output waveform for $C = 100 \text{ pF}$, $C = 150 \text{ pF}$ and $C = 50 \text{ pF}$ and the input is a 25 V step.

Sol: Given data:


$$R_1 = 2 \text{ M}\Omega$$

$$R_2 = 2 \text{ M}\Omega$$

$$C_2 = 100 \text{ pF}$$

$$V_i = 25 \text{ V step}$$

$$C_1 = ?$$

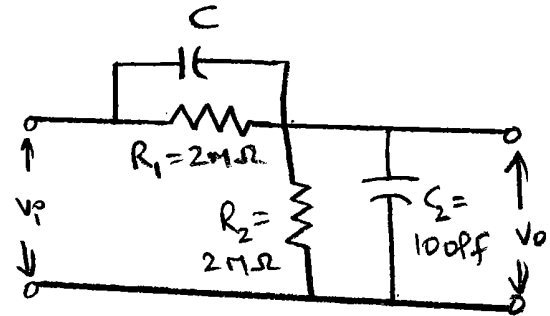

for perfect Compensation

$$R_1 C_1 = R_2 C_2$$

$$C_1 = \frac{R_2 C_2}{R_1}$$

$$C_1 = \frac{2 \times 10^6 \times 100 \times 10^{-12}}{2 \times 10^6}$$

$$C_1 = 100 \text{ pF}$$

a) $C_1 = 100 \text{ pF}$

$$V_o(0^+) = \frac{V C_1}{C_1 + C_2} = \frac{25 \times 100 \times 10^{-12}}{100 \times 10^{-12} + 100 \times 10^{-12}} = 12.5 \text{ V}$$

$$V_o(\infty) = \frac{V R_2}{R_1 + R_2} = \frac{25 \times 2 \times 10^6}{2 \times 10^6 + 2 \times 10^6} = 12.5 \text{ V}$$

b) $C_1 = 150 \text{ pF}$


$$V_o(0^+) = \frac{V C_1}{C_1 + C_2} = \frac{25 \times 150 \times 10^{-12}}{150 \times 10^{-12} + 100 \times 10^{-12}} = 15 \text{ V}$$

$$V_o(\infty) = \frac{V R_2}{R_1 + R_2} = \frac{25 \times 2 \times 10^6}{2 \times 10^6 + 2 \times 10^6} = 12.5 \text{ V}$$

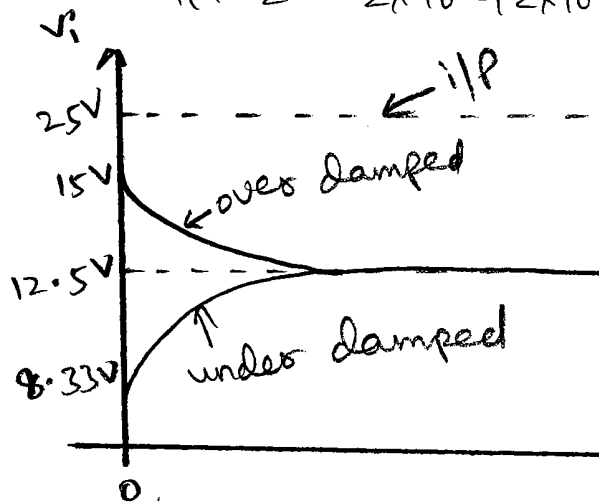9) $C_1 = 50 \text{ pF}$


$$V_0(0+) = \frac{V C_1}{C_1 + C_2} = \frac{25 \times 50 \times 10^{-12}}{50 \times 10^{-12} + 100 \times 10^{-12}} = 8.33 \text{ V}$$

$$V_0(\infty) = \frac{V R_2}{R_1 + R_2} = \frac{25 \times 2 \times 10^6}{2 \times 10^6 + 2 \times 10^6} = 12.5 \text{ V}$$



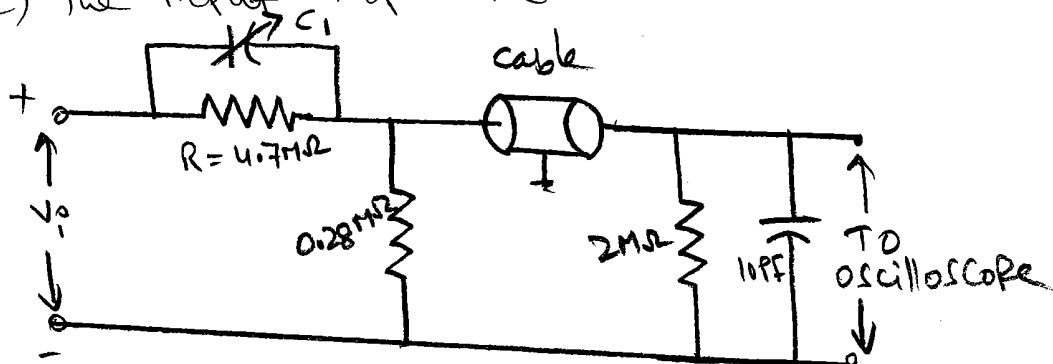(2-29) An oscilloscope test probe is indicated. Assume that the cable capacitance is 100 pF . The input impedance of the scope is $2 \text{ M}\Omega$ in parallel with 10 pF . What is the

- Attenuation of the probe.
- C_1 for best response.
- The input impedance of the compensated probe.



Sol: Given data:

cable capacitance = 100 pF

$R_1 = 2 \text{ M}\Omega$

$C = 10 \text{ pF}$

$$\text{Net Capacitance} = \text{Cable Capacitance} + 10 \text{ pF} = 100 + 10 = 110 \text{ pF} = C_2$$

$$\text{Net resistance} = 2 \text{ M}\Omega // 0.28 \text{ M}\Omega = \frac{2 \times 0.28}{2 + 0.28} = 0.245 \text{ M}\Omega = R_2$$

a) Attenuation of the probe

$$a = \frac{R_2}{R_1 + R_2}$$

$$a = \frac{0.245}{4.7 + 0.245}$$

$$a = \underline{\underline{0.05}}$$

b) For perfect compensation

$$R_1 C_1 = R_2 C_2$$

$$C_1 = \frac{R_2 C_2}{R_1}$$

$$C_1 = \frac{0.245 \times 110 \times 10^{-12} \times 10^6}{4.7 \times 10^6}$$

$$C_1 = \underline{\underline{5.74 \text{ pF}}}$$

c) Input impedance

$$Z_i = R_1 + R_2$$

$$Z_i = 4.7 + 0.245$$

$$Z_i = \underline{\underline{4.95 \text{ M}\Omega}}$$

