 


COMBINATIONAL CIRCUITS

Combinational ckt:—

- logic ckt for digital systems may be combinational or sequential.
- A combinational ckt consists of logic gates whose o/p's at any time are determined from the present combination of inputs.
- It performs an operation that can be specified logically by a set of Boolean functions.
- It consists of input variables, logic gates and o/p variables.
- The logic gates accept signals from the inputs and generate signals to the outputs.



- The  $n$  i/p binary variables come from an external source; The  $m$  output variables go to an external destination.
- For  $n$  input variables, there are  $2^n$  possible o/p values for each combination. For each possible input combination, there is one possible output value. Thus a combinational ckt can be specified with a truth table that lists the o/p values for each combination of input variables.

Analysis procedure:—


- The first step in the analysis is to make sure that the ckt is combinational and not a sequential.

- The diagram of a combinational ckt has logic gates with  $G$  paths or memory elements. A feedback path is a connection from the o/p of one gate to the input of a second gate forms part of the input to the first stage.

- Once the logic diagram is verified as a combinational ckt one can proceed to obtain o/p Boolean function or truth table.

- To obtain the o/p boolean function from a logic diagram, proceed as follows.

 1. Label all gate o/p's that are a function of i/p variables with arbitrary symbols. Determine the boolean functions for each gate o/p.
2. Label the gates that are a fn of input variables and previously labeled gates with other arbitrary symbols.
3. Repeat the process of step 2 until the o/p's of the ckt are obtained.
4. By repeated substitution of previously defined functions, obtain the o/p boolean functions in terms of input variables.





$$G_1 \rightarrow ABC \quad G_2 \rightarrow A+B+C \quad G_3 = AB \quad G_4 \rightarrow AC \quad G_5 \rightarrow BC$$

$$G_6 \rightarrow AB+AC+BC = F_2$$

$$\begin{aligned} G_6' &\rightarrow (AB+AC+BC)' = \overline{AB} \cdot \overline{AC} \cdot \overline{BC} \\ &= (\overline{A+B}) (\overline{A+C}) (\overline{B+C}) \end{aligned}$$

$$\begin{aligned} G_7 &\rightarrow (A+B+C) (\overline{A+B}) (\overline{A+C}) (\overline{B+C}) \\ &= (A+B+C) (\overline{A} \cdot \overline{A} + \overline{A} \overline{C} + \overline{A} \overline{B} + \overline{B} \overline{C}) (\overline{B+C}) \\ &= \overline{A} \overline{B} + \overline{A} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{C} + \overline{A} \overline{B} + \overline{A} \overline{B} \overline{C} + \overline{B} \overline{C} + \overline{B} \overline{C} \\ &= \overline{A} \overline{B} + \overline{A} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{B} \overline{C} \\ &= (A+B+C) (\overline{A} \overline{B} + \overline{A} \overline{C} + \overline{A} \overline{B} \overline{C}) \overline{B} \overline{C} \\ &= \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} \end{aligned}$$

$$G_8 \rightarrow \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C}$$

— To obtain the truth table directly from logic diagram through the derivation of boolean functions.

1. Determine the no. of i/p variables in ckt. for  $n$ -inputs, there possible i/p combination and list the binary numbers from 0 to  $2^n - 1$ .
2. Label the o/ps of selected gates with the arbitrary symbols.
3. obtain the truth table for o/ps of those gates that are a function of i/p variables only.
4. proceed to obtain the T.T for o/ps of those gates that are fn of previously defined values until columns for all o/ps are determined.

A	B	C	G <sub>1</sub>	G <sub>2</sub>	G <sub>3</sub>	G <sub>4</sub>	G <sub>5</sub>	G <sub>6</sub>	G <sub>6</sub>	G <sub>7</sub>	G <sub>8</sub>
0	0	0	0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	0	1	1	1
0	0	1	0	1	0	0	0	0	1	1	1
0	1	0	0	1	0	0	0	0	1	0	0
0	1	1	0	1	0	0	1	1	0	1	1
1	0	0	0	1	0	0	0	0	1	0	0
1	0	1	0	1	0	0	0	1	0	0	0
1	1	0	0	1	1	0	0	1	0	0	0
1	1	1	1	1	1	1	1	1	0	0	1

### Design procedure:

The design procedure starts from the Specification of the problem and ends up with a logic diagram or a set of boolean functions from which the logic diagram can be obtained.

1. From the Specifications of the ckt, determine the required no. of inputs and o/p's and assign a symbol to each.
2. Derive the truth table that defines the required relationship b/w inputs and outputs.
3. Obtain the Simplified boolean functions for each o/p as a fn of i/p variables.
4. Draw the logic diagram and Verify the correctness of the design.

- A truth table for a Combinational ckt consists of input columns and o/p columns.

- Input columns are obtained from the  $2^n$  binary numbers for the  $n$  input variables. The binary values for the o/p's are

★ determined from the stated specifications.

- o/p functions specified in the truth table give the exact definition of combinational ckt.

- The o/p binary functions listed in the truth table are simplified by any available method such as algebraic manipulation, the map method.

- The o/p binary functions listed in the truth table are simplified by any available method such as algebraic manipulation, the map method.

### Code Conversion Example

- code converter is a ckt that makes the two systems even though each uses a different binary code.

Ex: BCD to Excess-3 code

Input is BCD and the o/p is Excess-3 code. The o/p BCD has numbers starting from 0 to 9 which uses 4-bits to represent. The Excess-3 code for 0 is 3, 1 is 4, ... 9 is 12 which is also represented by 4 bits. So, therefore, we need 4 input as well as 4 output variables.

- Designate four i/p binary variables by A, B, C, D and four o/p by w, x, y & z.






Input BCD

Output Excess-3 Code

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	0
1	1	0	1	1	1	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	0	0

 These are don't Care  
Conditions for BCD.



	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

$$z = \bar{D}$$

AB\CD	00	01	11	10
00	1		1	
01	1		1	
11	X		X	X
10	1		X	X


$$y = \bar{C}\bar{D} + CD$$

AB\CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$x = \bar{B}D + \bar{B}C + B\bar{C}\bar{D}$$

AB\CD	00	01	11	10
00				1
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$w = A + BD + BC$$

 

BCD to Excess-3 code.

# BINARY ADDER - SUBTRACTOR


- Digital Computers perform a variety of information processing. The most basic arithmetic operation is the addition of two binary digits.
- When both augend & addend bits are equal to 1, the binary sum consists of two digits. The higher significant bit of this result is called a carry.
- A combinational ckt that performs the addition of two bits is called a half adder.

One performs the addition of three bits is a full adder.

## Half adder


The ckt needs two binary i/p's & two binary o/p. Let the i/p's are  $x$  &  $y$  and o/p are  $S$  &  $C$ .

$x$	$y$	$S$	$C$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

 

$$S = xy' + x'y = x \oplus y$$

$$C = xy$$

 




1 adder:

full adder is a combinational ckt performs the sum of three bits. It consists of three inputs and two o/p's. Two of i/p's are x and y, represents two significant bits to be added. The third i/p, z represents the carry from previous LSB. The two o/p's are s & c. The s o/p is equal to 1 when only one i/p is equal to 1 or when all three i/p's are equal to 1. The c o/p has carry to 1 if two or three i/p's are equal to 1.


x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$s = x'y'z + x'y'z' + xy'z + xy'z'$$

$$= x'(y'z + y'z') + x(y'z + y'z')$$


$$= x \oplus y \oplus z$$

 


$$c = yz + xy + xz$$

$$= x'(y \oplus z) + x(y \oplus z)$$

$$= x \oplus y \oplus z$$

 

 Implementation of F.A with two H.A and an OR Gate.



1)  $x \oplus y$    2)  $x \oplus y \oplus z$    3)  $xy$    4)  $(x \oplus y)(z) = (x'y + zy')$

$$= x'yz + zy'z$$

5)  $(x'yz + zy'z) + xy$

$$x'yz + zy'z + xy$$


$$\Sigma m(3, 5, 7, 6)$$

### Binary Adder - (parallel Binary Adder)

A binary adder is a digital ckt that produces the arithmetic sum of two binary numbers. It can be constructed with full adders connected in cascade, with the o/p carry from each F.A connected to the i/p carry to the next F.A.

Let two binary numbers  $A = 1011_2$   $B = 0011$

Subscript P :	3	2	1	0	
i/p carry	0	1	1	0	$c_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
o/p carry	0	0	1	1	$c_{i+1}$

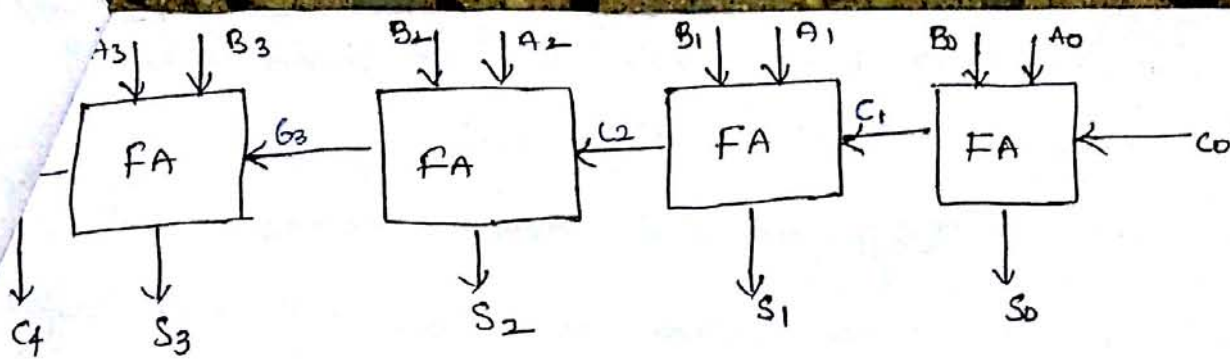

The bits are added with F.A, starting from least significant position, to form the sum & carry. The i/p carry  $C_0$  in the LSB must be 0. The value of  $C_{i+1}$  in a given significant position is the o/p carry of F.A. This is transferred into the i/p carry of F.A that adds the bits one higher significant position to left.

Extra

### Carry propagation

- The add of two binary numbers in parallel implies that all the bits of the augend and addend are available for computation at the same time. In any comb. ckt, the sig must propagate through the gates before the correct o/p sum is available in o/p terminals.

- The total propagation time is equal to the propagation delay of typical gate times and the no. of gate levels in the ckt.

- Inputs  $A_3$  &  $B_3$  are available as soon as i/p sigs are applied. However,  $C_3$  does not settle to its final value until  $C_2$  is available from the previous stage.

The no. of gate levels for the carry propagation can be found from the ckt of the F.A. The i/p & o/p variables use the subscript  $i$  to denote a typical stage in the adder.



The signals at  $P_i$  &  $G_i$  settle to their steady state after they propagate through their respective gates.

- A comb. ckt will always have some value at its o/p terminals. O/p's will not be correct unless the signals are given enough time to propagate through the gates connected from i/p's to o/p's.

As, the arithmetic operations are implemented by successive additions time consumed during the addition process is very critical.

For reducing the carry propagation delay time, employ faster gates with reduced delays.

Consider the F.A designed with two H.A. Define two new binary variables.

$$P_i = A_i \oplus B_i \quad \& \quad G_i = A_i B_i$$

$G_i$  - Carry generate

$$S_i = P_i \oplus C_i, \quad C_{i+1} = G_i + P_i C_i$$

$P_i$  - Carry propagate.


$$C_0 = \text{i/p Carry.}$$


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 C_1) = G_2 + P_2 G_1 + P_2 P_1 C_1$$

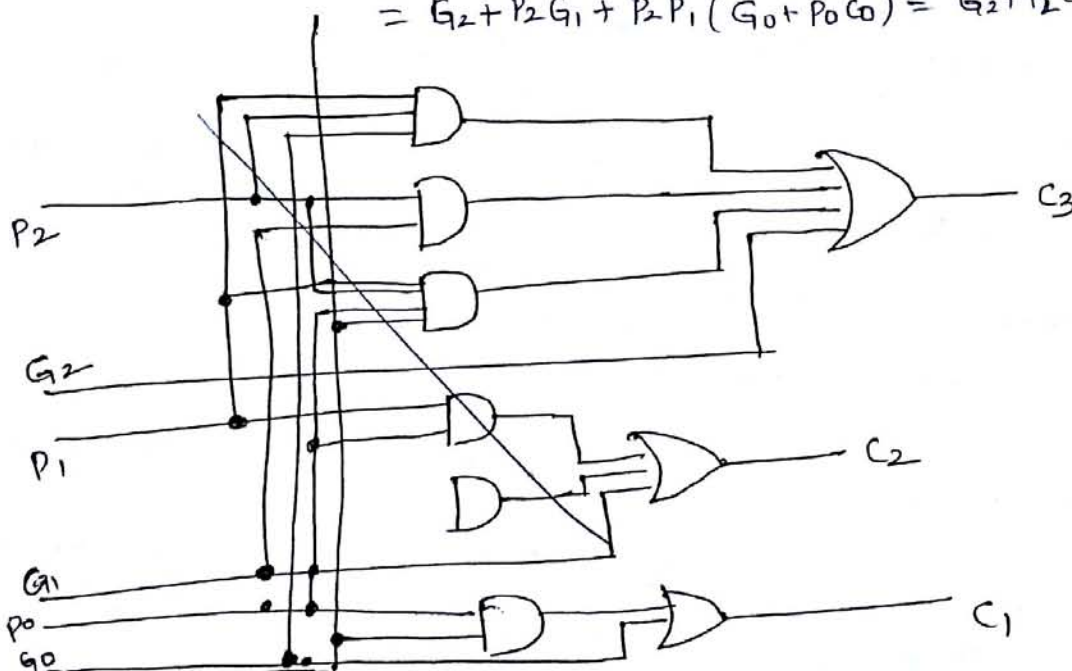
$$= G_2 + P_2 G_1 + P_2 P_1 (G_0 + P_0 C_0) = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$



 

Binary Subtractor : The subtraction of unsigned binary numbers can be done by means of complements.

 $A - B$  can be done by taking 2's complement of  $B$  and adding it to  $A$ . The 2's complement can be obtained by taking the 1's complement and adding one to LSB. The 1's complement can be obtained with inverters and a one can be added to the sum through the i/p carry.





The mode i/p  $m$  controls the operation.

When  $m=0$ , the ckt is an adder, because when  $m=0$ ,  $B \oplus 1 = B$ .  
 The full adder receives the value of  $B$ , the i/p carry is 0,  
 the ckt performs  $A + B$ .

When  $m=1$ ,  $B \oplus 1 = B'$  and  $co=1$ . The  $B$  inputs are all complemented and a 1 is added through the i/p carry. The ckt performs the operation  $A + \text{2's Complement of } B$ .

Decimal Adder:

Computers or Calculators that perform arithmetic operation in decimal number system represent decimal numbers in binary coded form

A dec. adder requires a min of nine i/p's and five since five bits are required to code each decimal digit and the ckt must have an i/p & o/p carry.

BCD Adder:

Consider the arithmetic addition of two dec digits in BCD, together with an i/p carry from a previous stage.

If we apply two BCD digits to a 4-bit binary adder. It will form sum in binary and produce a result that ranges from 0 to 19.

	Binary Sum				BCD Sum				Decimal	
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	1	6
0	0	1	1	1	0	1	0	0	0	7



	$Z_8$	$Z_4$	$Z_2$	$Z_1$	$C$	$S_8$	$S_4$	$S_2$	$S_1$	Decimal
0	1	0	0	0	0	0	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	0	1	0	1	0	10
0	1	0	1	1	0	1	0	1	1	11
0	1	1	0	0	0	1	1	0	0	12
0	1	1	0	1	0	1	1	0	1	13
0	1	1	1	0	0	1	1	1	0	14
0	1	1	1	1	0	1	1	1	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

The columns under the binary sum list the binary value that appears in the o/p's of the 4-bit binary adder. The o/p of two decimal digits must be represents in BCD and should appear in the form listed in the columns under BCD sum.

From the table, it is apparent that when the binary sum is equal to or less than 1001, the corresponding BCD number is identical, and therefore no conversion is needed.

When the binary sum is  $>1001$ , we obtain a non-valid BCD. The addition of 6 (0110) to the binary sum converts it to the correct BCD representation and produces an o/p carry. The correction is needed when binary sum has an o/p carry

$$K=1$$

The other six combinations from 1010 through 1111 that need to have a 1 in position  $Z_8$ . To distinguish them from binary 1010 which also have a 1 in  $Z_8$ , we specify further either  $Z_4$  or  $Z_2$  must have a 1. The condition for a correction & an o/p carry is expressed by the Boolean fn.

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

When  $c=1$ , it is necessary to add 0110 to the binary sum & provide an o/p carry for the next stage.

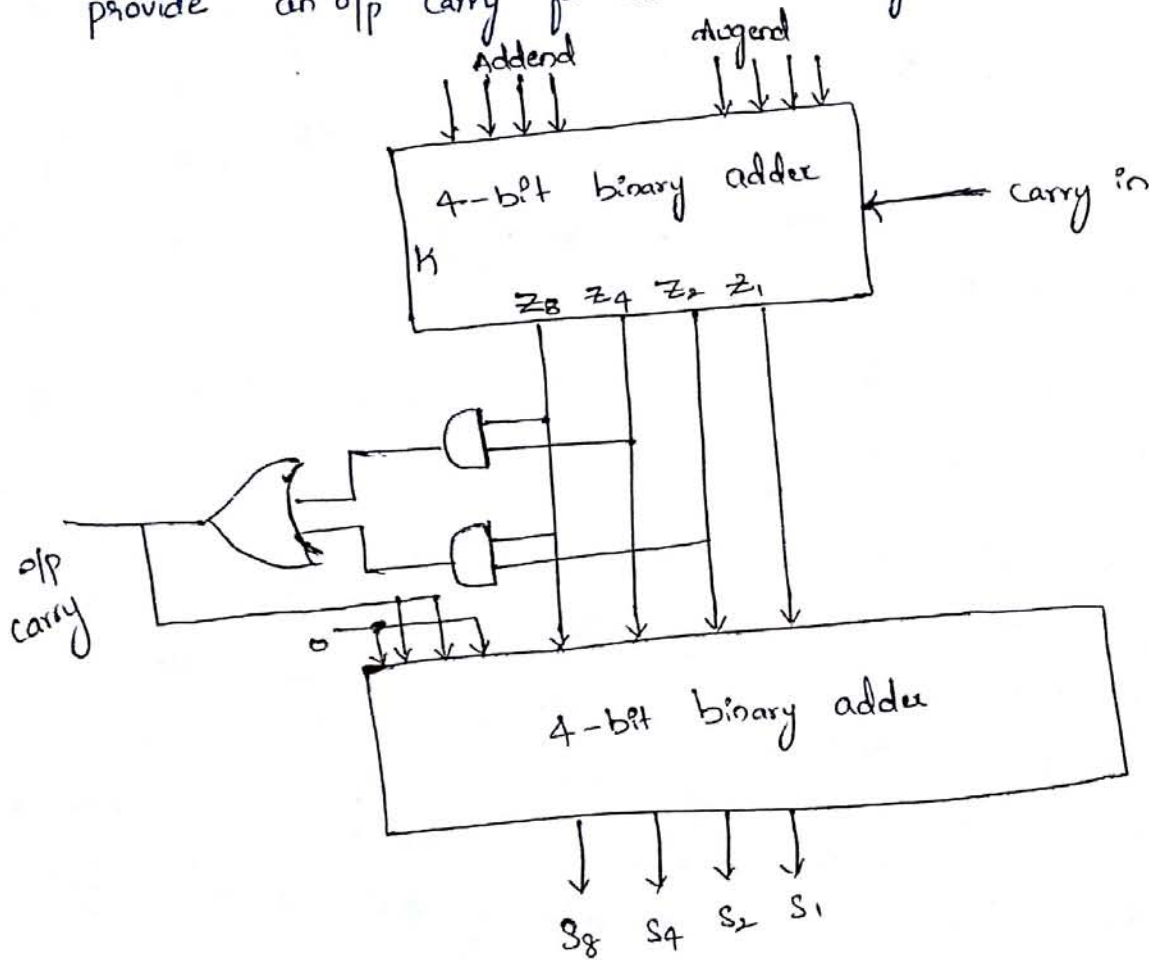


Fig: BCD adder.

# Extra Binary Multiplier

The multiplicand is multiplied by each bit of the multiplier starting from LSB. Each such multiplication forms a partial product.

Successive partial products are shifted one position to the left.

The final product is obtained from the sum of the partial products.

Consider the multiplication of two 2-bit numbers. The multiplier bits are  $A_1$  and  $A_0$ , multiplier bits are  $B_1$  and  $B_0$  and the product is

$C_3 C_2 C_1 C_0$

$B_1 B_0$

$A_1 A_0$

$A_0 B_1 A_0 B_0$

$A_1 B_1 A_1 B_0$

$C_3 C_2 C_1 C_0$

 


Fig: 2-bit Binary multiplier.



Multiplexers:  
It is  
to be  
- 24

### Magnitude Comparator :

A magnitude Comparator is a Comb ckt that compares two A and B and determines their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$  or  $A < B$ .

Let the two numbers, A and B, with four digits each.

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

The two numbers are equal if all pairs of significant digits are equal.  $A_3 = B_3$  and  $A_2 = B_2$  and  $A_1 = B_1$  and  $A_0 = B_0$ . When the numbers are binary, the digits are either 1 or 0, and the equality relation of each pair of bits can be expressed logically with an Ex-NOR function as

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3.$$

$x_i = 1$  only if the pair of bits in position  $i$  are equal.

The Equality of two numbers, A and B is displayed in a Comb ckt by an o/p binary variable that we designate by symbol  $(A=B)$ . For the Equality condition to exist, all  $x_i$  variables must be 1. This dictates an AND operation of all variables.

$$(A=B) = x_3 x_2 x_1 x_0$$

- To determine if  $A >$  or  $<$  B, the relative mag of pairs of significant digits starting from MSB. If two digits are equal compare the next lower significant pair of digits. This comparison continues until a pair of unequal digits is reached.

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

P.B. 25

### Multiplexers:


It is a digital switch, which allows digital information from several sources to be routed onto a single output line.

- It consists of several data-input lines and a single o/p line. The selection of a particular input line is controlled by a set of selection lines.

- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bits combinations determine which input is selected.
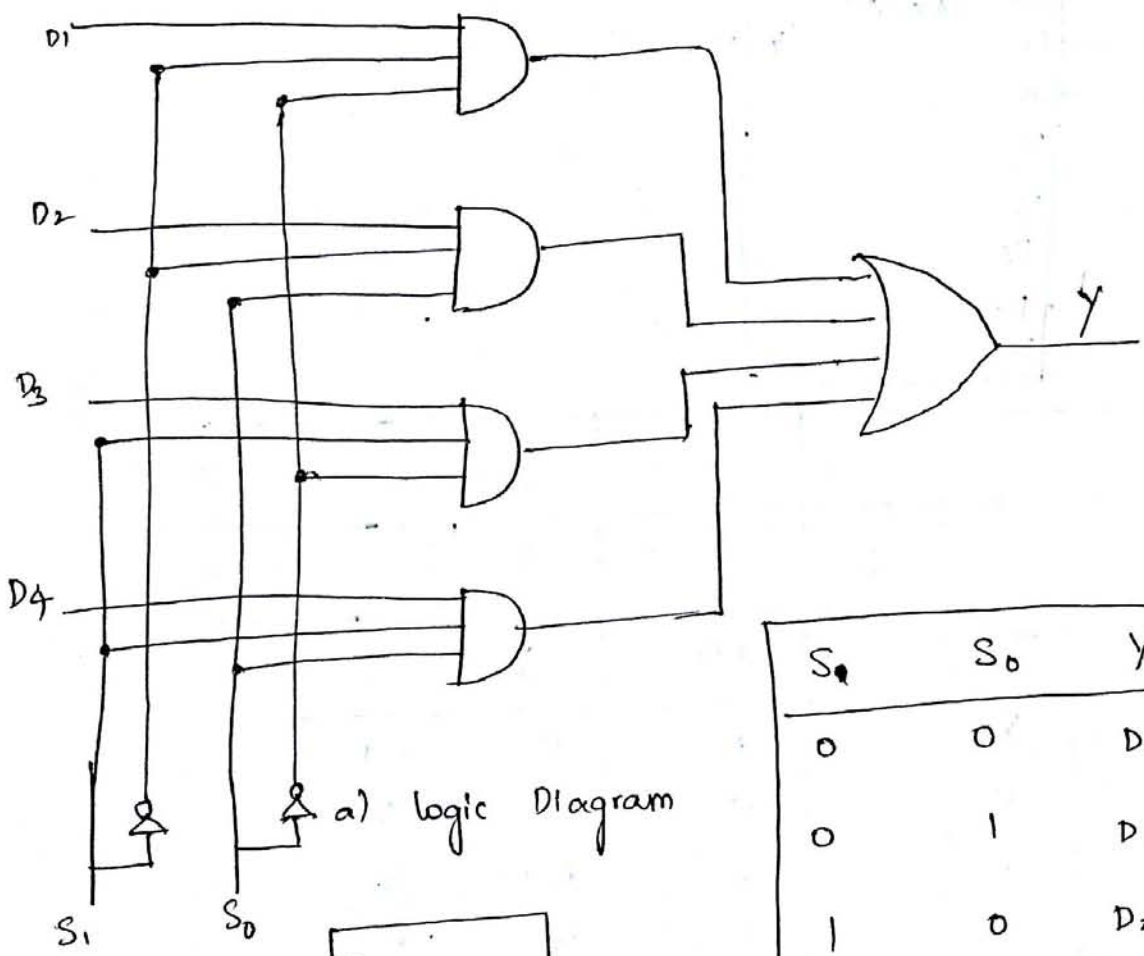
### 4 to 1 line multiplexer:


- It consists of four lines,  $D_0$  to  $D_3$ , is applied to one input of an AND gate. Selection lines are decoded to select a particular AND gate.



a) logic Diagram

$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

b) functional table

 


c) logic Symbol


 
# 74x151 8 to 1 multiplexers

— It is a 8 to 1 multiplexer. It has eight inputs. It provides two outputs, one is active high, the other is active low. These are select lines C, B, A which select one of the eight inputs.

In this op it is not specified in 1s and 0s. Because, multiplexer is a data switch, it does not generate only data of its own, but it simply passes external data, input to the o/p.




Inputs			Outputs		
Select			Enable	Y	Y-bar
C	B	A	EN	Y	Y-bar
X	X	X	1	0	1
0	0	0	0	D <sub>0</sub>	D <sub>0</sub> -bar
0	0	1	0	D <sub>1</sub>	D <sub>1</sub> -bar
0	1	0	0	D <sub>2</sub>	D <sub>2</sub> -bar
0	1	1	0	D <sub>3</sub>	D <sub>3</sub> -bar
1	0	0	0	D <sub>4</sub>	D <sub>4</sub> -bar
1	0	1	0	D <sub>5</sub>	D <sub>5</sub> -bar
1	1	0	0	D <sub>6</sub>	D <sub>6</sub> -bar
1	1	1	0	D <sub>7</sub>	D <sub>7</sub> -bar



74x157 Quad 2-input multiplexer:-

It Selects four bits of data from two Sources under the control a Common Select input (S)

 
The Enable input ( $\bar{E}$ ) is active low. when  $\bar{E}$  is high, all of the o/p's (Y) are forced low regardless of all other input conditions.



Inputs		Outputs			
$\bar{E}$	S	1Y	2Y	3Y	4Y
1	X	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B


74x153 Dual 4 to 1 multiplexer:-

 It contains two identical and identical independent 4 to 1 multiplexers. Each multiplexer has separate Enable input.



Inputs				Outputs	
1EN	2EN	B	A	1Y	2Y
0	0	0	0	1D0	2D0
0	0	0	1	1D1	2D1
0	0	0	0	1D2	2D2
0	0	1	0	1D3	2D3
0	0	1	1	1D0	0
0	1	0	0	1D1	0
0	1	0	1	1D2	0
0	1	0	0	1D3	0
0	1	1	0	0	2D0
0	1	1	1	0	2D1
0	1	1	0	0	2D2
1	0	0	0	0	2D3
1	0	0	1	0	0
1	0	1	0	0	0


2 to 1 multiplexer using two 74LS150

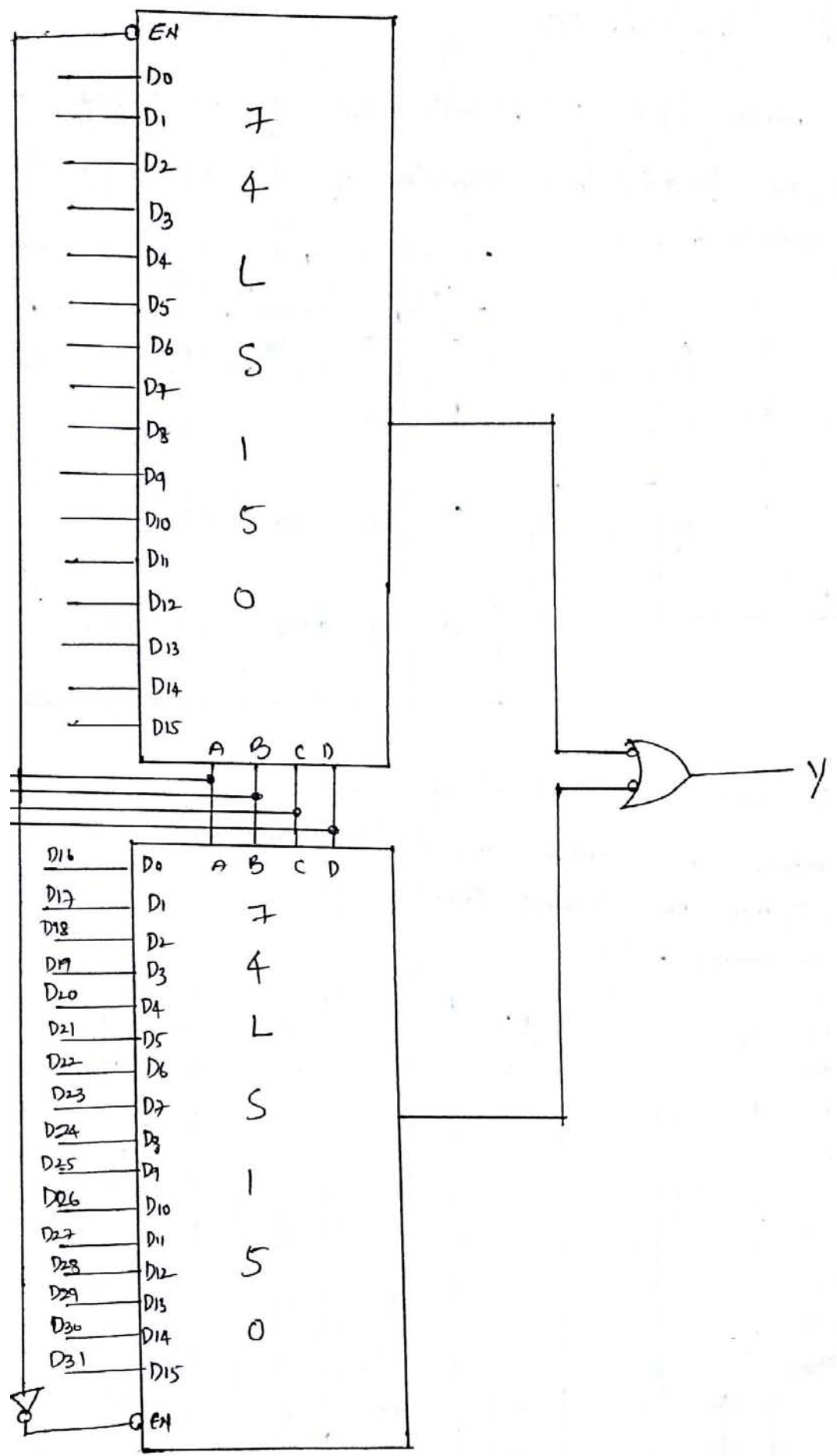

$F(A, B, C, D) = \sum m (0, 1, 2, 4, 6, 9, 12, 14)$

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15


$\bar{A}$  1  $\bar{A}$  0 1 0 1 0

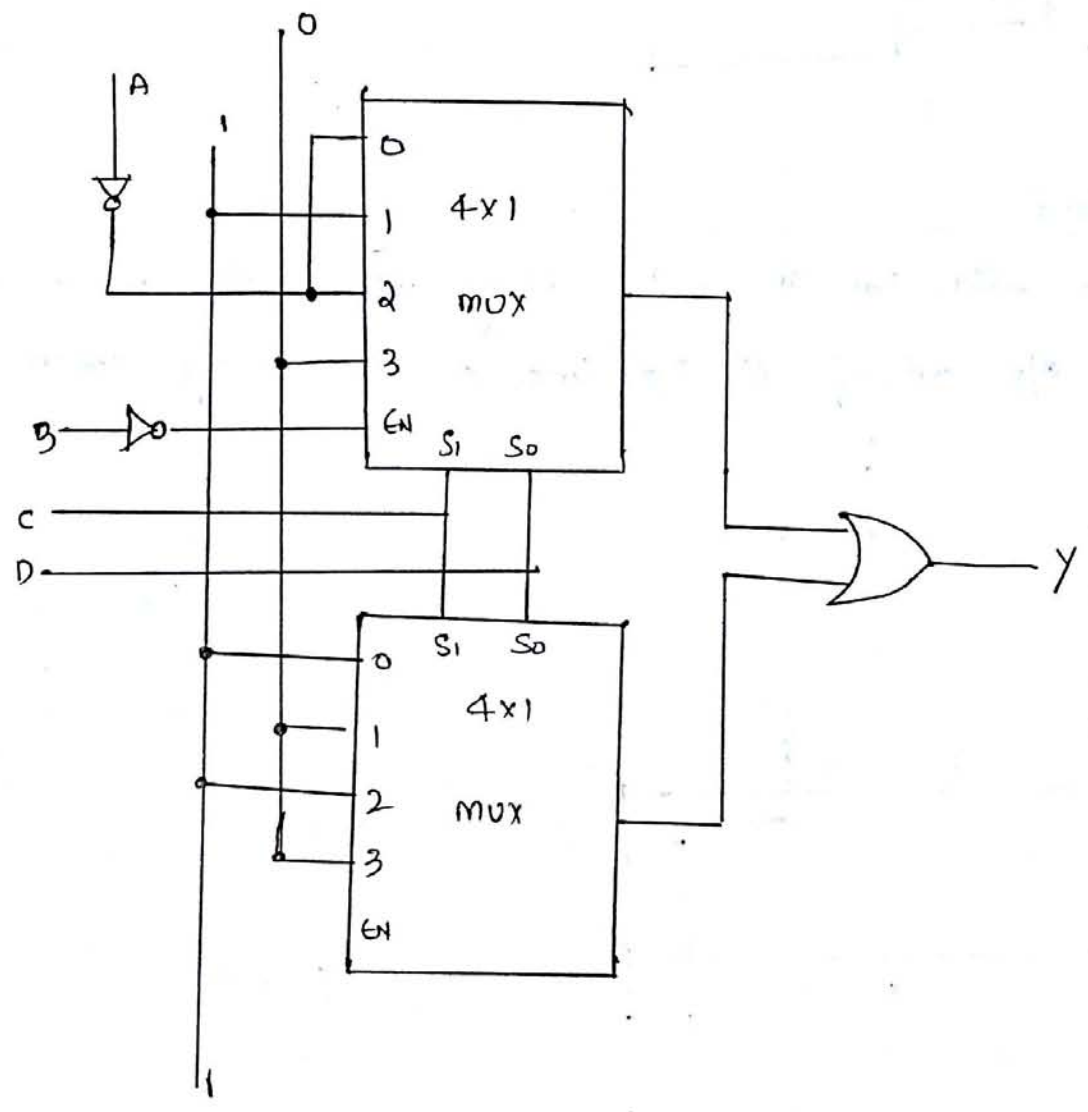

Decoder:-

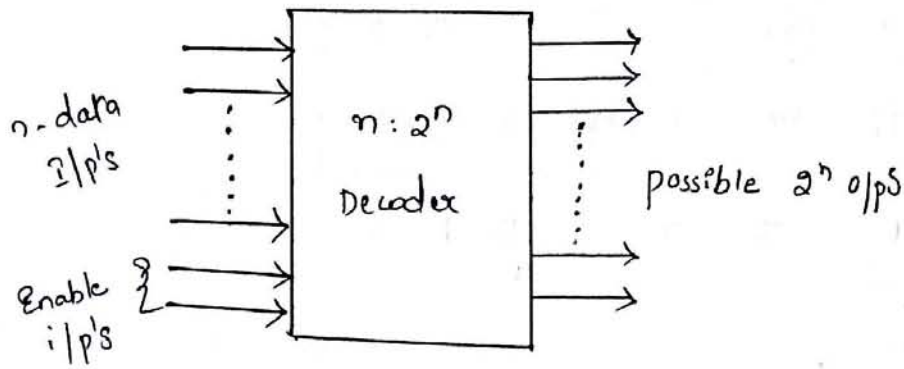
- Decoder is a multiple-input, multiple output logic circuit which converts coded inputs into coded outputs, where the input and output codes are different.
- Input code generally has fewer bits than the output code.
- The encoded information is presented as an input producing 2<sup>n</sup> possible outputs. The 2<sup>n</sup> output values are from 0 through 2<sup>n</sup>-1.




 
### Binary Decoder:

— A decoder which has an  $n$ -bit binary input code and a one activated o/p out of  $2^n$  o/p code is called binary decoder.




2-4, Decoder.

Two inputs are decoded into four o/p's, each o/p representing one of the minterms of the 2 input variables.

Inputs			Outputs			
EN	A	B	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


74x138 3 to 8 Decoder:-

 - 74x138 is a commercially available 3 to 8 decoder.
- It accepts 3 binary inputs (C, B, A) and when Enabled provides eight individual active low o/p's ( $Y_0 - Y_7$ )
- The device has three Enable inputs.
  - two active low ( $\overline{G_{2A}}, \overline{G_{2B}}$ )
  - and one active high ( $G_1$ )



Inputs						Outputs							
$G_{2B}$	$G_{2A}$	$G_1$	C	B	A	$\bar{Y}_7$	$\bar{Y}_6$	$\bar{Y}_5$	$\bar{Y}_4$	$\bar{Y}_3$	$\bar{Y}_2$	$\bar{Y}_1$	$\bar{Y}_0$
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	1	1	1	1	1	1	1	0
0	0	1	0	0	1	1	1	1	1	1	0	1	1
0	0	1	0	1	0	1	1	1	1	1	0	1	1
0	0	1	0	1	1	1	1	1	1	0	1	1	1
0	0	1	1	0	0	1	1	1	0	1	1	1	1
0	0	1	1	0	1	1	1	0	1	1	1	1	1
0	0	1	1	1	0	1	0	1	1	1	1	1	1
0	0	1	1	1	1	0	1	1	1	1	1	1	1


74x139 Dual 2 to 4 Decoder :-

 

Inputs			Outputs			
$\bar{1G}$	1B	1A	$\bar{1Y}_3$	$\bar{1Y}_2$	$\bar{1Y}_1$	$\bar{1Y}_0$
1	X	X	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1



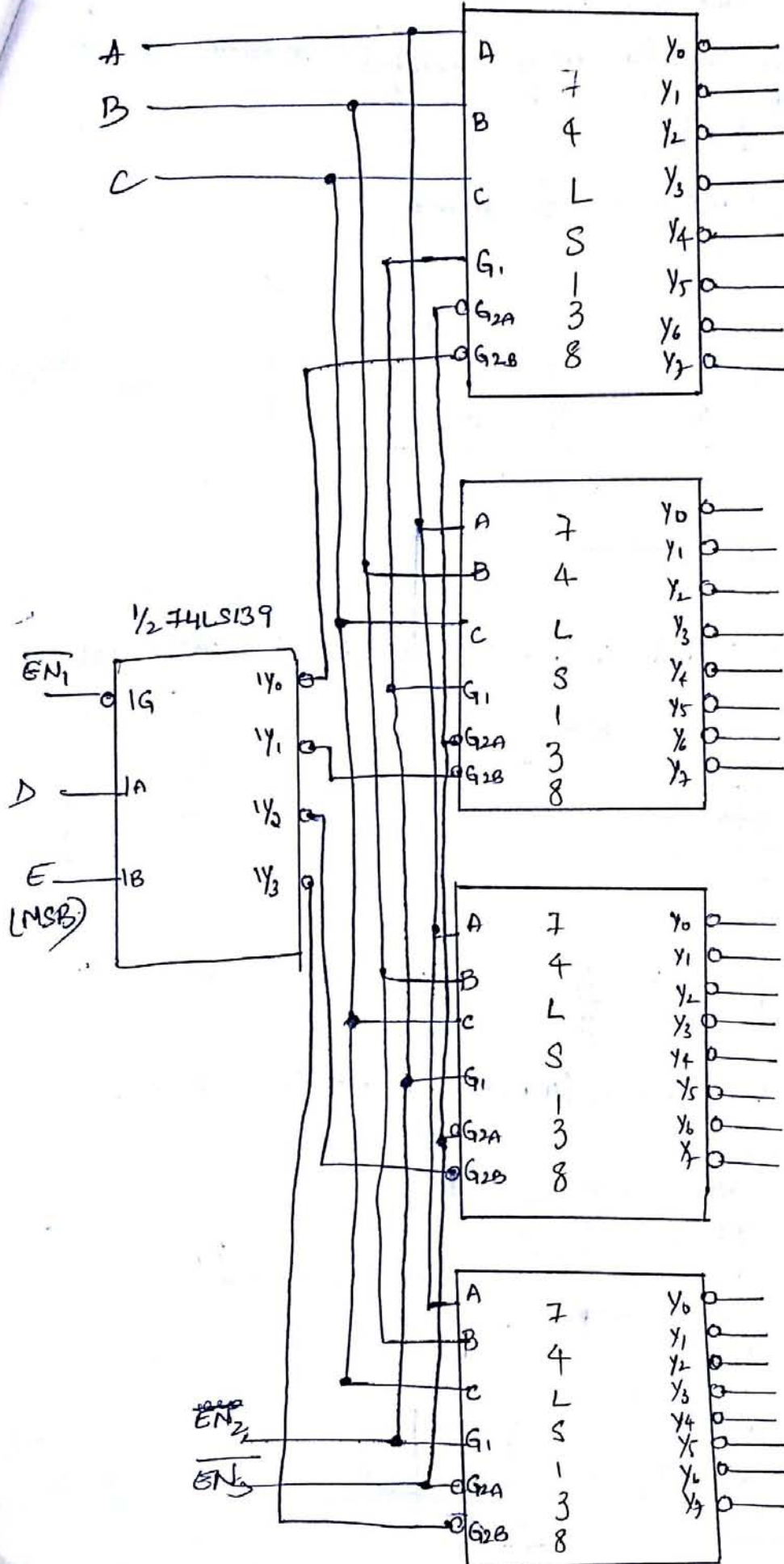5 to 32 decoder using one 2 to 4 and four 3-8 decoder IC's.



- 4th order to 10

$$\overline{EN}_1 = 0$$

$$EN_2 = 1$$

$$\overline{EN}_3 = 0$$

EDCBA.

$$4 \quad ED = 00 \rightarrow 1Y_0 \Rightarrow Y_0 - Y_7$$

$$01 \rightarrow 7Y_1 \Rightarrow Y_8 - Y_{15}$$


$$10 \rightarrow 1Y_2 \Rightarrow Y_{16} - Y_{23}$$

$$11 \rightarrow 1Y_3 \Rightarrow Y_{24} - Y_{31}$$


# Realization of multiple o/p functions using Binary Decoder.

The combination of decoder and external logic gates can be used to implement single or multiple o/p functions. The decoder generates minterms for input variables. Thus by logically ORing specified minterms we can implement the given function.

 
1)  $f = \Sigma(1, 2, 3, 7)$  using 3 to 8 decoder.



 2)  $F(A, B, C) = \Sigma m(0, 3, 5, 7)$  and  $f_2(A, B, C) = \Sigma m(2, 3, 6, 7)$  using 74LS138



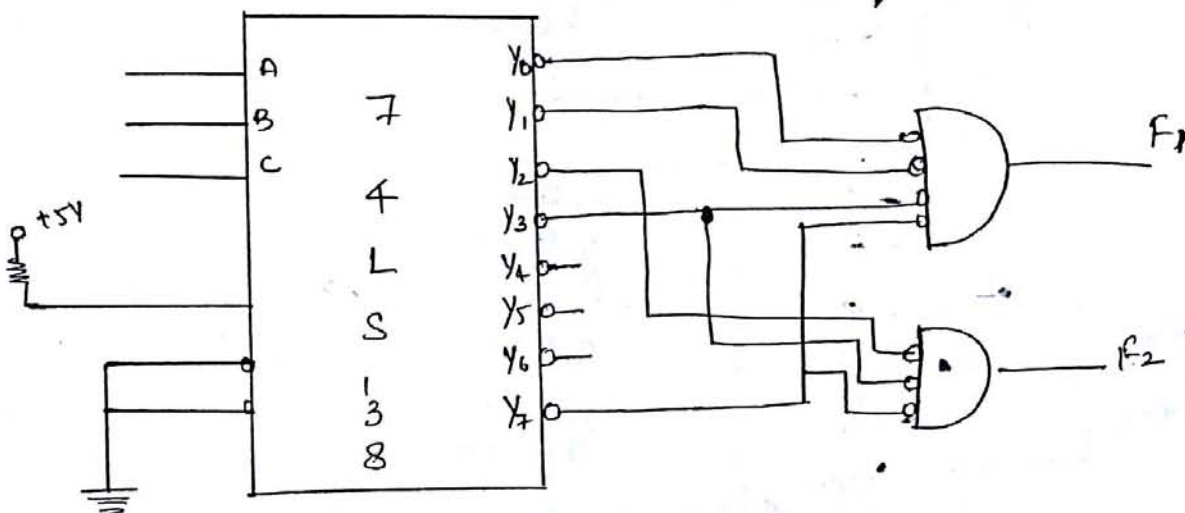
3)  $F(A, B, C) = \Pi(0, 1, 3, 7)$  and  $f_2(A, B, C) = \Pi(2, 3, 7)$



★ Explain for


Encoder :

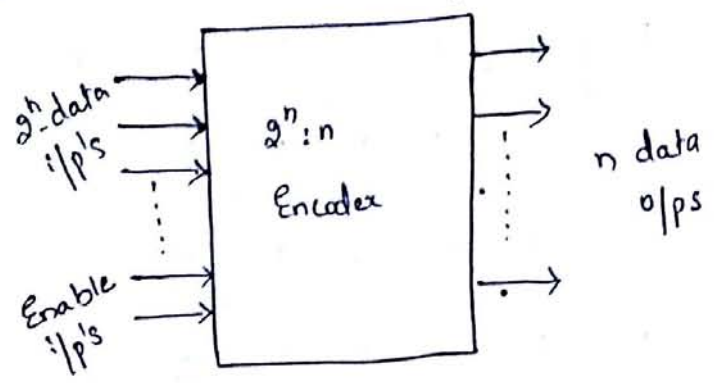An Encoder is a digital ckt that performs the inverse operation of decoder. An Encoder has  $2^n$  input lines and  $n$  o/p lines. In Encoder the output lines generate the binary code corresponding to the input value.



Decimal to Bcd Encoder :- (priority Encoder)

 — Decimal to Bcd Encoder, usually has ten input lines and four o/p lines. The decoded decimal data acts as an input for decoder and encoded Bcd o/p is available on the four o/p lines.




— It has nine input lines and four o/p lines. Both i/p and o/p lines are asserted low. It is important to note that there is no i/p line for decimal zero. When this condition occurs all o/p lines are 1.



	Decimal Value	Inputs									Outputs			
		f	2	3	4	5	6	7	8	9	D	E	B	A
0	0	1	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1	0
2	2	X	0	1	1	1	1	1	1	1	1	1	0	1
3	3	X	X	0	1	1	1	1	1	1	1	1	0	0
4	4	X	X	X	0	1	1	1	1	1	1	0	1	1
5	5	X	X	X	X	0	1	1	1	1	1	0	1	0
6	6	X	X	X	X	X	0	1	1	1	1	0	0	1
7	7	X	X	X	X	X	X	0	1	1	1	0	0	0
8	8	X	X	X	X	X	X	X	0	1	1	0	0	0
9	9	X	X	X	X	X	X	X	X	0	1	0	1	1
		X	X	X	X	X	X	X	X	0	0	1	1	0

Octal to Binary Encoder

Do	Inputs							Outputs		
	D1	D2	D3	D4	D5	D6	D7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

★  
List of Code converters.

- ① Binary  $\rightarrow$  Gray      ② Gray  $\rightarrow$  Binary      ③ BCD  $\rightarrow$  Gray  
④ BCD  $\rightarrow$  Ex-3s      ⑤ Ex-3  $\rightarrow$  BCD      ⑥ Binary - BCD :





# of a 4-bit Binary-to-Gray code converter.

Binary				Gray			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

G<sub>3</sub>

B <sub>3</sub> B <sub>2</sub>	B <sub>1</sub> B <sub>0</sub>	G <sub>3</sub>	
00	00	0	0
00	01	0	0
00	10	1	1
00	11	1	1

$$G_3 = B_3$$

G<sub>2</sub>

B <sub>3</sub> B <sub>2</sub>	B <sub>1</sub> B <sub>0</sub>	G <sub>2</sub>	
00	00	0	0
00	01	0	0
00	10	1	1
00	11	1	1

$$G_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2$$

$$B_2 \oplus B_3$$

G<sub>1</sub>


B <sub>3</sub> B <sub>2</sub>	B <sub>1</sub> B <sub>0</sub>	G <sub>1</sub>	
00	00	0	0
00	01	0	0
00	10	1	1
00	11	1	1

$$G_1 = B_2 \bar{B}_1 + \bar{B}_2 B_1$$

$$B_1 \oplus B_2$$




G<sub>0</sub>

B <sub>3</sub> B <sub>2</sub>	B <sub>1</sub> B <sub>0</sub>	G <sub>0</sub>	
00	00	0	0
00	01	1	1
00	10	1	1
00	11	0	0

 


→ Design a 4-bit Gray to Binary code converter.

$G_3$	$G_2$	$G_1$	$G_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

  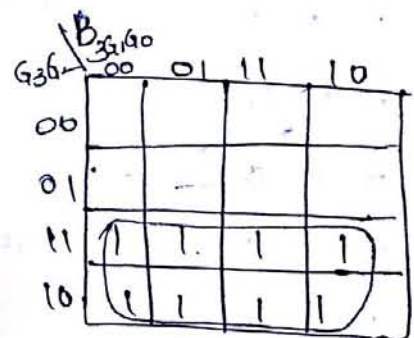

 $B_0 = (G_3 \oplus G_2) \oplus (G_1 \oplus G_0)$








# Qn of a 4-bit Binary-to-BCD code converter.


Decimal	4-bit Binary				BCD output				
	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	A	B	C	D	E
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0
3	0	0	1	1	0	0	0	1	1
4	0	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	1	0	1
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	0	0	0
9	1	0	0	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0
11	1	0	1	1	1	0	0	0	1
12	1	1	0	0	1	0	0	1	0
13	1	1	0	1	1	0	0	1	1
14	1	1	1	0	1	0	0	0	0
15	1	1	1	1	1	0	1	0	1




Block diagram

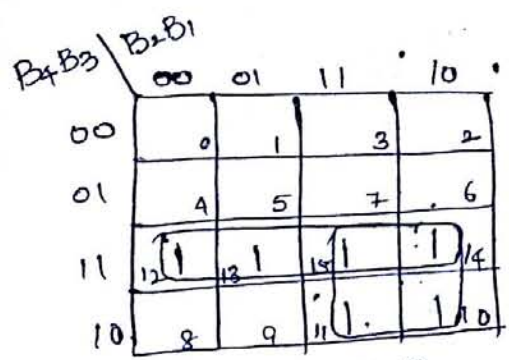


$$A = B_4 B_3 + B_4 B_2$$

 


$$B = B_4 B_3 B_2$$

 

$$C = \bar{B}_4 B_3 + B_3 B_2$$

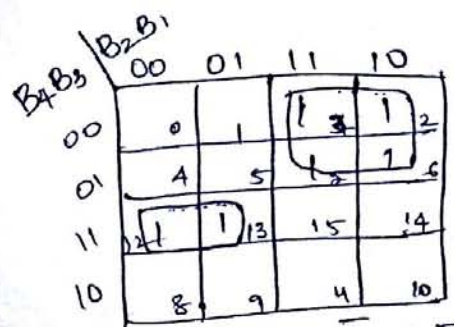

$$D = B_4 B_3 + B_4 B_2$$

 

$$E = B_1$$



# Design of a BCD-to-Gray code converters

## K-map Simplification

$B_3$	$B_2$	$B_1$	$B_0$	D	C	B	A
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	0	0
1	1	1	0	1	1	0	1
1	1	1	1	1	1	0	0

K-map for  $G_0$

$B_3B_2$	$B_1B_0$	00	01	11	10
00	0	1	0	1	
01	0	1	0	1	
11	X	X	X	X	
10		1	X	X	

$G_0 = \overline{B_1}B_0 + B_1\overline{B_0}$   
 $B_1 \oplus B_0$

K-map for  $G_1$

$B_3B_2$	$B_1B_0$	00	01	11	10
00				1	1
01	1	1			
11	X	X			
10				X	X

$G_1 = B_2\overline{B_1} + \overline{B_2}B_1$

don't cases.

K-map for  $G_2$

$B_3B_2$	$B_1B_0$	00	01	11	10
00					
01	1	1	1	1	
11	X	X	X	X	
10	1	1	X	X	

$G_2 = B_2 + B_3$

K-map for  $G_3$

$B_3B_2$	$B_1B_0$	00	01	11	10
00					
01					
11	X	X	X	X	
10	1	1	X	X	

$G_3 = B_3$

# Design of full-subtractor:-


A full subtractor (f.s) subtracts two bits and considering borrow from preceding column produces difference D, Borrow (Bout)

Q.  $A, B, Bin \rightarrow$  i/p's


$D, Bout \rightarrow$  o/p's

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## Block diagram

 

## 5. Logic diagram

 

4. Simplify o/p function variables.

D

A	B Bin			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\begin{aligned}
 D &= \bar{A}\bar{B}Bin + \bar{A}BBin + A\bar{B}\bar{B}in + ABBin \\
 &= \bar{A}(B \oplus Bin) + A(\overline{B \oplus Bin}) \\
 &= A \oplus B \oplus Bin
 \end{aligned}$$

Bout

A	B Bin			
	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$Bout = \bar{A}Bin + \bar{A}B + BBin$$

Subtractors: Half-subtractor  $\rightarrow$  Subtracts one bit from other bit  
 full-subtractor  $\rightarrow$  Subtrahend is subtracted from minuend considering borrow from preceding column

Design of Half-Subtractor: (LSB Subtraction)


1. H.S is combinational ckt that subtracts one bit from other produces the difference D, borrow B.

2.  $A, B \rightarrow$  i/p's ;  $D, B \rightarrow$  o/p's .


3. T.T

I/p's		o/p's	
A	B <sub>in</sub>	D	B <sub>out</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Block diagram

 


4. Simplify o/p function variables.

 

$D = \bar{A}B + A\bar{B} = A \oplus B$        $B = \bar{A}B$

5. Logic diagram

 




★ Hazards and Hazard-free Realizations:-

- Hazards are unwanted switching transients that may appear at o/p of ckt because different paths exhibit different delays. Such a transient is also called a glitch or Spurious Spike; which is caused by hazards behaviour of logic ckt.
- A hazard in a combinational ckt is a condition where a single variable change produces a momentary o/p change when no o/p change should occur.
- Hazards are of two types
  - (i) Static Hazard
  - (ii) Dynamic Hazard
- ↳ a) static 1-hazard  
b) static 0-hazard.

Static - 1 hazard:

Suppose all the i/p's are assigned some level and only i/p say x changes from 0 to 1 or 1 to 0. If o/p is expected to be at 1 regardless of changing variable, the spurious 0 level for a short interval is called static 1 hazard.

 Static 0-hazard: If o/p is expected to be at 0' regardless of changing variable, the spurious 1 level for a short interval is called a static 0 hazard.




Static - 1 - hazard



static 0-hazard.

\* → Static hazards can be eliminated by using redundant gates.

 
→ When o/p changes three or more times when it should show the change from 1 to 0 or 0 to 1 only once, it is called dynamic hazard.




\* → When a ckt is implemented in SOP with AND-OR gates or with NAND gates, removal of static 1(0) hazard generates that no static 0(1) hazards or dynamic hazards will occur.

Static hazards: —

 
Consider the  $f(A, B, C) = \sum m(3, 4, 5, 7)$



$$f = A\bar{B} + BC$$

 

b) Logic diagram

 

c) Contact network.

\* let  $A=1, B=1, C=1$ , and only  $B$  is changing from 1 to 0.

The o/p  $F$  has to remain at logic 1

- (i) When  $B=1$ , o/p of gate 2 is 1, o/p of gate 1 is 0 and o/p  $F=1$ .
- (ii) When  $B$  changes to 0, o/p of gate 2 is 0, o/p of gate 1 is 1 and o/p  $F$  remains at 1.
- (iii) for the change in  $B$  from 1 to 0, if gate 1 responds faster than  $G_2$ ,  $F$  will be 1 as expected.

$$\left. \begin{array}{l} \text{let } G_1 = 10\text{ns} \\ G_2 = 20\text{ns} \end{array} \right\} \begin{array}{l} B=0, \bar{B}=1 \\ A=1 \end{array} \Rightarrow G_1=1 \rightarrow F=1$$






If gate B is faster than A, the output becomes a before the output of A changes to 1, and after a very short time the output of A and B will be 0 resulting in an output of 0.

Let  $G_1 = \text{AND}$ ,  $G_2 = \text{AND}$ ,  $A=0$ ,  $B=0$ ,  $C=0$  till  $t=1 \mu\text{s}$   
 after time  $G_1=1$ ,  $G_2=0$  for

 A little later of course the output goes to 1. This erratic behaviour is known as static 1-hazard.



with contact when it is called the set hazard.

Fig 10 If we consider the pos realization of some f, then

$$f = \text{min}(a, 1, b)$$



Let  $A=0$ ,  $B=0$ ,  $C=0$  and only B is changing from 0 to 1. The output F here also remains at 0.

(ii) when  $A=0$ ,  $G_1=0$ ,  $G_2=1$  and so  $f=0$  when B changes to 1, output of  $G_1=1$ ,  $G_2=0$  and  $f$  remains at 0.

the change in B from 0 to 1. If  $G_2$  responds faster than  $G_1$ ,  $f$  will be 0 as required.  
 If  $G_1$  is faster than  $G_2$ , the output becomes 1 before the output of  $G_2$  changes to 0 and for very short time output of both





$G_1$  and  $G_2$  will be 1 resulting in an opp of 1.


This erratic behaviour is known as static-0 hazard. with contact networks it is called cut set hazard.

Hazard free - Realization :-



→ static -1 hazards arises because two adjacent 1's are covered by different subcubes.

If we want to ensure that this pair of adjacent 1's is covered by same subcube shown marked on map, we need to add one more AND gate.

 The corresponding contact n/w will have one more path. This realization will now have no static -1 hazards but the fn contains a redundant term BC



$$F = A\bar{B} + BC + AC$$

  

→ The removal of static 1 hazards in a fn by addition of subcubes does not guarantee the removal of static 0 hazards in fn.


with  $\star$  Realize the Switching fn  $F(A,B,C) = \sum m(2,4,5,6)$  by a hazard free logic gate network.

A \ BC	00	01	11	10
0				1
1	1	1		1

$$f = A\bar{C} + A\bar{B} + B\bar{C}$$

If we consider SOP form,  $F = A\bar{C} + A\bar{B} + B\bar{C}$

 This SOP form is hazard free because every pair of adjacent 1 is covered by some subcube, and in order to satisfy this constraint, a redundant subcube  $A\bar{C}$  has to be added.



→ Suppose we wish to realize the same fn in POS

A \ BC	00	01	11	10
0	0	0	0	
1			0	

$$f = (A+B)(\bar{B}+\bar{C})$$

There will be a hazard marked by arrow

if we realize it as  $F = (A+B)(B+\bar{C})$

→ By expanding pos form & ignoring term  $B \cdot \bar{B} = 0$  results in same SOP form which is hazard free.

The hazard in pos form must be attributed to ignoring terms like  $B \cdot \bar{B} = 0$

→ we can conclude that hazard free fn has to be realized in its original form without resorting to simplification or factoring.



## Essential Hazards:

- Essential hazard that occur in asynchronous sequential ckt.
- It is caused due to unequal delays, along two or more paths that originate from same input.
- Excessive delay through an inverter ckt in comparison to delay associated with feedback path may cause such a hazard.
- Essential hazards cannot be corrected by adding redundant gates as in static hazard.

This can be corrected by adjusting the amount of delay in affected path.

\* → To avoid essential hazards, each feedback loop must be handled with individual care to ensure that the delay in feedback loop is long enough compared to delays of other signals that originate from input terminals.

## Binary Subtractor (parallel subtractor)

