

R16

Code No: 133BJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, May/June - 2019

NETWORK ANALYSIS

(Common to ECE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub-questions.

PART - A

(25 Marks)

- 1.a) Define cutset matrix. [2]
- b) Two coupled coils of $L_1=0.8\text{H}$ and $L_2=0.2\text{H}$ have a coupling coefficient $K=0.9$. Find the mutual inductance? [3]
- c) Write the relation between Q factor and Bandwidth of parallel resonance circuit. [2]
- d) Write the condition for over damping of series RLC circuit. [3]
- e) Find Laplace transform of ramp function? [2]
- f) Find the one sided Laplace Transform of $Ku(t)$ where K is an unknown real constant. [3]
- g) Define all four admittance parameters of two port network. [2]
- h) Define a driving point impedance and driving point admittance of two port network. [3]
- i) Draw the circuit diagram of π attenuator. [2]
- j) State Foster's reactance theorem. [3]

PART - B

(50 Marks)

2. Draw the directed graph, tree, cutset matrix and tie set matrix for the network shown in figure 1. [10]

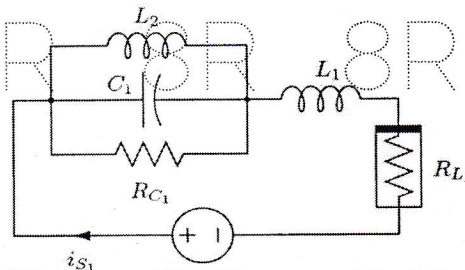


Figure: 1

OR

3. Find the coupling coefficient and energy stored in the inductors for the following circuit shown in figure 2. [10]

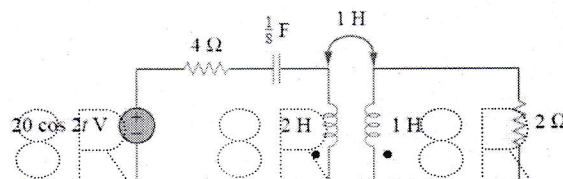


Figure: 2

4. The switch shown in figure 3 is at position 1 for $t < 0$. At $t = 0$ it moves to position 2. Sketch $v(t)$ as a function of time. [10]

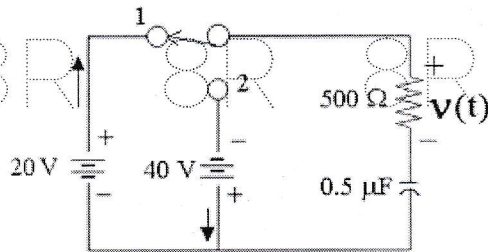


Figure: 3

OR

5. A series RLC circuit with $R = 50\Omega$, $L = 0.1\text{H}$ and $C = 50\mu\text{F}$ has a constant voltage $V = 100\text{V}$ applied at $t = 0$. Find the current transient assuming zero initial charge on the capacitor. [10]

6. Find v for the circuit using Laplace Transform shown in figure 4. [10]

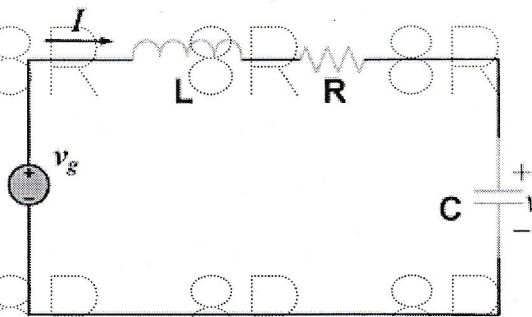


Figure: 4

OR

7. Consider the signal $h(t) = t^4 u(t)$. Use the Laplace Transform multiplication theorem to find the response of this system to a unit step input $u(t)$ in Laplace Transform. [10]

8. Derive the relation between Z-parameters and Y-parameters and also ABCD parameters. [10]

OR

9. Define h-parameters for two port network and find them for the following circuit shown in figure 5. [10]

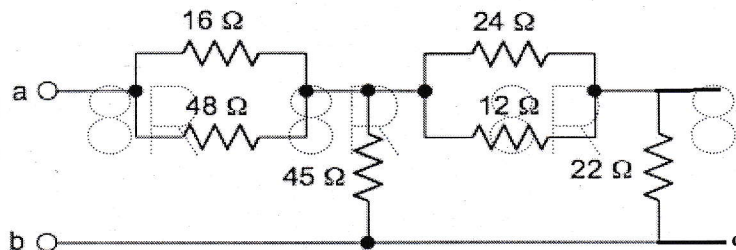


Figure: 5

8R 8R 8R 8R 8R 8R 8R 8

10.a) Explain how to convert T network to π network?

b) A π -pad attenuator is required to reduce the level of an audio signal by 12dB while matching the impedance of the 500Ω network. Calculate the values of the three resistors required. [5+5]

8R 8R 8R 8R 8R 8R 8R 8

OR

11.a) Draw the low pass T filter and draw its frequency response.

b) Design a constant k high pass π filter with cut off frequency of 2 kHz. [5+5]

---oo0oo---

8R 8R 8R 8R 8R 8R 8R 8

8R 8R 8R 8R 8R 8R 8R 8

8R 8R 8R 8R 8R 8R 8R 8

8R 8R 8R 8R 8R 8R 8R 8

8R 8R 8R 8R 8R 8R 8R 8

8R 8R 8R 8R 8R 8R 8R 8