

R18

Code No: 152AC

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech I Year II Semester Examinations, July/August - 2021

BASIC ELECTRICAL ENGINEERING

(Common to ECE, EIE)

Time: 3 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) What are the limitations of superposition theorem?
b) Find the current 'i' in the circuit below shown in figure 1 using Thevenin's theorem.

[5+10]

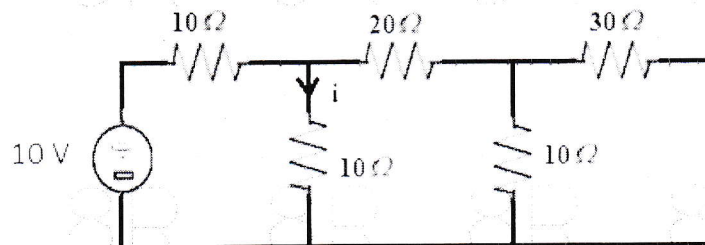


Figure: 1

- 2.a) Define time constant. What is the time constant of RL circuit?
b) Find the current 'i' in the circuit below shown in figure 2 using Norton's theorem.

[5+10]

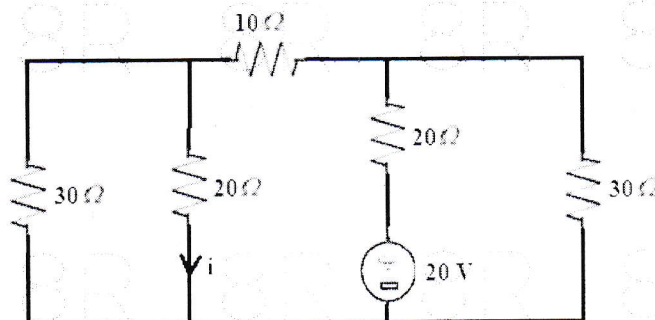


Figure: 2

- 3.a) What are the advantages of phasor representation?
b) A circuit consisting of a coil resistance 10Ω and inductance 0.2 H in series with a capacitor of $10\ \mu\text{F}$ is connected to a variable frequency supply which has a constant voltage of 30 V . Calculate the resonant frequency and current in circuit at resonance.

[5+10]

- 4.a) Define phase sequence. Obtain the relationship between line and phase values of star connected system with 3- ϕ star supply.
b) A series circuit with a resistor of $50\ \Omega$, capacitor of $20\ \mu\text{F}$ and inductance of 0.2 H is connected across 230 V , 50 Hz supply. Calculate current, power and power factor in the circuit.

[8+7]

5.a) What are the main applications of auto transformers? [5+10]
b) How a single phase transformer works? Explain.

6.a) Draw the equivalent circuit of transformer and Explain. [8+7]
b) Explain the working of single phase induction motor.

7.a) Draw the characteristic between torque and slip in three phase induction motor. [7+8]
b) What is a cable? Explain different types of cables.

8.a) What are the applications of MCB? Explain its working principle. [7+8]
b) Discuss about various types of batteries.

---ooOoo---