

Code No.: EE104ES

R20

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

I-B.TECH-I-Semester End Examinations (Supply) - January- 2022

BASIC ELECTRICAL ENGINEERING

(Common to CSC, CSD, CSE, IT)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(20 Marks)

1. a) State KVL. [2M]
- b) Give the V-I relation of (i) Inductance (ii) capacitance. [2M]
- c) Write the expression for resonant frequency of series RLC circuit connected to A.C supply. [2M]
- d) What is the power factor and active power of a circuit carries a current of $15 \angle 45^\circ$ A and applied voltage of $230 \angle 15^\circ$ V? [2M]
- e) What is Ideal Transformer? Write the difference between ideal and practical transformer? [2M]
- f) What is auto transformer? Give its applications. [2M]
- g) Explain the significance of back E.M.F in D.C motor. [2M]
- h) Give the classification of D.C motors. [2M]
- i) Why starter is needed in case of 3-Phase Induction motor? [2M]
- j) Define slip of a 3-phase Induction motor. [2M]

PART-B

(50 Marks)

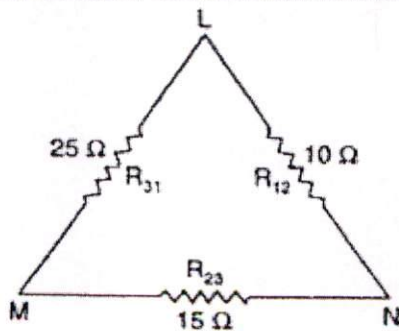
2. a) State and explain Superposition theorem. [5M]
- b) Convert below delta network into an equivalent star network. [5M]



OR

3. a) State and explain Thevenin's theorem. [5M]

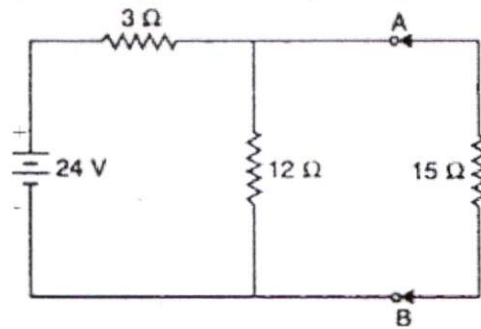b) Find the current flowing through $15\ \Omega$ resistance using Norton's theorem. [5M]



4. a) Derive average and R.M.S value of a sinusoidal quantity. [5M]
 b) A coil takes current of 2 amps when connected across 200V, 50 Hz supply. The power consumed by the coil is found to be 300 Watts. Find the inductance and power factor of the coil. [5M]

OR

5. A balanced 3-phase delta connected load of $(6+j8)\ \Omega$ / phase is connected to a 3-phase 400V, 50 Hz balanced supply. Find the current, p.f, active power, reactive power and apparent power of the load. [10M]
6. a) Explain the construction and working principle of a single phase transformer. [6M]
 b) The maximum flux density in the core of a 220/440V, 50Hz single phase transformer is 1.2Wb/m^2 . If the E.M.F per turn is 20V, determine (i) primary and secondary turns and (ii) area of the core. [4M]

OR

7. a) Develop the equivalent circuit of a single phase transformer. [5M]
 b) Explain various configurations of 3-phase Transformers. [5M]
8. a) Derive the E.M.F equation of D.C. Generator. [5M]
 b) Distinguish between self excited and separately excited D.C. Generators. How are self excited D.C. Generators classified? Give their circuit diagrams. [5M]

OR

9. a) Derive the torque equation of a D.C. Motor. [6M]
 b) A 220 V D.C shunt motor has an armature resistance of $0.5\ \Omega$ and takes a current of 40 A on full loads. By how much main flux must be reduced to raise the speed by 60%, if the developed torque is constant? [4M]
10. a) Sketch and explain torque-slip characteristic of a 3- phase Induction motor. [6M]
 b) Explain how rotating magnetic field is produced in a 3- phase Induction motor. [4M]

OR

11. Explain the working of synchronous Generator with neat sketch. [10M]
