

Code No.: EC404PC

R20

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Regular) - August- 2023
ELECTRONIC CIRCUIT ANALYSIS

(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) Draw the circuit diagram of Darlington pair. [2M]
- b) Prove that $h_{fe} = \beta_m \cdot \beta_b \cdot \beta_e$. [2M]
- c) Draw the voltage shunt feedback amplifier, express its gain. [2M]
- d) Show that bandwidth increases with negative feedback. [2M]
- e) State the condition for Barkhausen criteria for sustainable oscillations. [2M]
- f) Compare RC type Oscillators with LC type. [2M]
- g) Define crossover distortion. [2M]
- h) What is Q-factor and write the expression for Q factor. [2M]
- i) Write the applications of monostable multivibrators. [2M]
- j) State the Miller's Theorem. [2M]

PART-B

(50 Marks)

- 2.a) Define f_β and f_T , and derive the relation between them. [5M]
- b) Derive the expression for gain-bandwidth product for voltage. [5M]

OR

3. Derive the expression for short circuit current gain in common emitter amplifier. [10M]
4. If the gain of an amplifier reduces to 1% of its open loop gain of 120 with negative feedback, compute the feedback factor and loop gain. [10M]

OR

5. Briefly explain the current shunt feedback, also find the gain, input impedance and output impedance. [10M]
6. Briefly explain about RC Phase shift oscillator with neat diagram. [10M]

OR

7. Explain the Wien bridge oscillator circuit with neat diagram. [10M]
8. Compare push pull and complementary symmetry configuration for class-B power amplifiers. [10M]

OR

9. In a tuned amplifier circuit $C=500\text{pF}$, $L=20\mu\text{H}$, $R_L = 1.5\text{k}\Omega$ and the transistor has $h_{fe} = 50$ and input resistance of $200\ \Omega$. The coil used has Q factor=30. Calculate i) resonant frequency of the tuned circuit, ii) impedance of the tuned circuit, iii) voltage gain of the stage. [10M]

10. Draw the circuit diagram of Astable multivibrator and explain its working. [10M]

OR

11. Draw the circuit diagram of Mono multivibrator and explain its working. [10M]
