

Code No.: EC403PC

R20

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
II-B.TECH-II-Semester End Examinations (Supply) - February- 2023
LINEAR IC APPLICATIONS
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) What are the characteristics of Ideal Op-Amp. [2M]
- b) Define CMRR of Op-Amp. [2M]
- c) What is voltage Regulator? List the types of voltage regulators? [2M]
- d) What is the necessity of voltage regulation? [2M]
- e) List the different types of Filters? [2M]
- f) State the Bkhausen Criterion? [2M]
- g) Define Capture range, Lock range? [2M]
- h) List any two applications of IC 555 timer in monostable mode? [2M]
- i) How many resistors are required in a 12 bit weighted resistor DAC. [2M]
- j) What is meant by resolution of DAC? [2M]

PART-B

(50 Marks)

2. Discuss the AC Characteristics of an Op-Amp in detail. [10M]
- OR**
3. Draw the pin Diagram of 741 Op-Amp and explain each pin in detail. [10M]
 4. Draw the circuit Diagram of Instrumentation Amplifier using 741 Op-Amp and explain its operation. [10M]
- OR**
5. Explain the Features of IC 723? [10M]
 6. Design a First Order High Pass filter with a cutoff frequency of 500 KHz with a pass band gain of 2. [10M]
- OR**
7. Draw and explain the Block Diagram of VCO? [10M]
 8. Explain how 555 timer is used as Astable multivibrator & Derive the expression for its frequency of Oscillations. [10M]
- OR**
9. Draw and explain the block diagram of PLL? [10M]
 10. Discuss Successive Approximation ADC with necessary diagrams and suitable examples. [10M]
- OR**
11. List and explain the specifications of DAC. [10M]
