

Code No.: EC401PC

R20

H.T.No.

8 R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**II-B.TECH-II-Semester End Examinations (Supply) - February- 2023**  
**NETWORK ANALYSIS AND TRANSMISSION LINES**  
**(ECE)**

[Time: 3 Hours]

[Max. Marks: 70]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(20 Marks)**

1. a) Define Graph, Tree, Basic Cut set and Basic Tie set. Illustrate with an example. [2M]
- b) Explain Active elements in detail. [2M]
- c) Derive the relation between voltage and current in a series connected RL Circuits. [2M]
- d) Draw a power triangle in series connected RLC networks. [2M]
- e) Derive the relation between RMS and maximum value. [2M]
- f) Define form factor and peak factor [2M]
- g) Differentiate group and phase velocities [2M]
- h) What is condition for distortion less transmission line? [2M]
- i) List the properties of smith chart [2M]
- j) Explain how Quarter wave transformer is used for matching? [2M]

**PART-B**

**(50 Marks)**

- 2.a) What is a basic cutset matrix? Explain with an example. [5 M]
- b) An Iron ring of a mean length of 50 cm has an air gap of 1 mm and a winding of 200 turns. If the relative permeability of the Iron is 400, when a current of 1 Amp flows in the winding, determine the flux density? (Neglect leakage and fringing.) [5 M]

**OR**

- 3.a) Discuss the dot convention used in magnetically coupled coils. [5 M]
- b) Derive an expression for the coefficient of coupling between two mutually coupled coils. [5 M]
- 4.a) Derive and draw the response of a series RLC circuit for a step input. [5 M]
- b) An impedance  $Z_1 = 10 + j10 \Omega$  is connected in parallel with another impedance of resistance  $8.5 \Omega$  and a variable capacitance connected in series. Find C such that the circuit is in resonance at 5 kHz. [5 M]

**OR**

- 5.a) Design a series RLC circuit that will have an impedance of  $10 \Omega$  at the resonant frequency of  $\omega_0 = 100 \text{ rad/s}$  and a quality factor of 80. Find the bandwidth. [5 M]
- b) Obtain the response of the R-L-C series circuit for exponential excitation. Use the Laplace Transform method. [5 M]

- 6.a) Explain different parameters to be considered for the design of attenuators. [5 M]  
b) Draw the symmetrical T and  $\pi$  sections and their decomposition into L sections. [5 M]

**OR**

- 7.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid parameters and ABCD Parameters. [5 M]  
b) Draw the circuit diagram for the T and  $\pi$  sections of the composite filter. [5 M]

- 8.a) Distinguish between the different types of distortions present in conventional transmission lines, and establish the condition for distortion less transmission lines. [5 M]  
b) A  $75 \Omega$  transmission line has a propagation constant of  $0.05+j5$  N/m, at 50 MHz. Find its primary constants, assuming phase velocity as 60% of light velocity and no distortion. [5 M]

**OR**

- 9.a) Explain the significance of infinite line, and hence obtain general expression for the line characteristic impedance using the lossy line equivalent circuit. [5 M]  
b) Establish the expressions for the propagation characteristics  $\alpha$ ,  $\beta$ ,  $\gamma$ ,  $\lambda$ ,  $v_p$ ,  $Z_0$  for lossy distortion less transmission lines. [5 M]

- 10.a) Sketch the variations of input impedances of SC and OC lines with  $5l$ , and explain how a UHF line can be used as an inductance or a capacitance. [5 M]  
b) A  $500 \Omega$  RF line is connected to a load  $75+j40 \Omega$ . Estimate the resultant reflection coefficient, VSWR,  $Z_{min}$ ,  $Z_{max}$ . Also find its Input Impedance, if the line length is  $0.5\lambda$ . [5 M]

**OR**

- 11.a) Explain the principle of impedance matching using a single stub. [5 M]  
b) Define the terms: Reflection coefficient and VSWR. Derive expressions for the same, as applicable to RF lines. [5 M]

\*\*\*\*\*