

Code No.: DS305ES

R20

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
II-B.TECH-I-Semester End Examinations (Supply) - February- 2024
DIGITAL LOGIC DESIGN
(CSD)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) Convert $(145.96)_{10}$ to hexadecimal numbers. [2M]
- b) Define a minterm and a maxterm. [2M]
- c) Identify any two fundamental postulates of Boolean Algebra. [2M]
- d) Realize the NAND gate using NOT gate. [2M]
- e) What is Comparator and deduce the truth table of 1-bit comparator. [2M]
- f) Outline any two applications of encoder and decoder. [2M]
- g) What is latch and flip-flop. [2M]
- h) Differentiate synchronous and asynchronous counters. [2M]
- i) Give the comparison between ROM and PLA. [2M]
- j) Explain RAM briefly. [2M]

PART-B

(50 Marks)

2. Represent decimal number 8620 in i) BCD, ii) Excess-3 code, iii) Binary number and iv). Grey code. [10M]

OR

3. Perform the subtraction with the following unsigned binary numbers by taking the 1's complement of the subtrahend. [5M]
[5M]
 - a) $11110 - 10000$
 - b) $11010 - 1100$

4. Minimize the following expression using K-map and realize using NAND gates. [10M]
$$F(A, B, C, D, E) = \prod(6, 9, 11, 13, 14, 17, 20, 25, 28, 29, 30)$$

OR

5. Simplify the following function and implement with NAND gates [10M]
 $F = \sum m(0, 1, 3, 4, 5, 7, 9, 11, 13, 15)$.

6. Construct a 4-bit binary adder using full-adders to perform binary addition between two 4-bit numbers. [10M]

OR

7. Design 3:8 decoder and explain operation with truth table. [10M]

8. Implement a 3-bit Ring Counter circuit using D-Flip Flops. [10M]

OR

9. Illustrate the operation of clocked SR Flip-Flop with the help of truth table. [10M]

10. Implement the following functions using PROM: $F1 = \sum m(0, 1, 3, 5, 7)$; $F2 = \sum m(0, 4, 3, 6, 7)$. [10M]

OR

11. Classify different PROMS and explain in detail. [10M]
