

Code No.: EC302PC

R20

H.T.No.

8

R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**

**II-B.TECH-I-Semester End Examinations (Supply) - February- 2024**

**DIGITAL SYSTEM DESIGN**

**(ECE)**

**[Time: 3 Hours]**

**[Max. Marks: 70]**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(20 Marks)**

1. a) Given that  $(292)_{10} = (1204)_b$  determine the value of b. [2M]
- b) State De Morgan's theorem and Duality. [2M]
- c) Define Minterm and Maxterm. [2M]
- d) Write the truth table of priority encoder. [2M]
- e) Write the difference between Latch and Flip flop. [2M]
- f) What is shift register? Give the classification of them? [2M]
- g) How many memory locations are addressed using 18 address bits? [2M]
- h) What is the size of the decoder in  $32 \times 10$  ROM? [2M]
- i) Draw the DTL OR gate. [2M]
- j) Draw the symbol of NMOS and PMOS transistor. [2M]

**PART-B**

**(50 Marks)**

2. Convert the following binary numbers to both 1's and 2's complement (i) 101 [10M]  
(ii) 1011.01 (iii) 11.101 (iv) 10111.10 (v) 0.101.
- OR**
3. Realize X-OR gate operation using (i) only NAND gates (ii) only NOR gates. [10M]
  4. Obtain (i) Sum of products form and (ii) Product of sums form for  $F = x'z' + y'z' + yz' + xy$ . [10M]
- OR**
5. With a neat design procedure, explain the implementation of a 2-bit Magnitude Comparator. [10M]
  6. Give the characteristic table, Truth table, characteristic equation and excitation table for T and DFF. [10M]
- OR**
7. Draw and explain 4-bit Universal shift register. [10M]
  8. Describe the design procedure of synchronous finite state machine (FSM) by taking serial binary adder as example. [10M]
- OR**
9. Give the comparison between PROM, PLA and PAL. [10M]
  10. Compare TTL, ECL and CMOS. [10M]
- OR**
11. What is meant by Tristate logic? Draw the circuit of Tristate TTL logic and explain the functions. [10M]

\*\*\*\*\*