

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**I-B.TECH-I-Semester End Examinations (Regular) - January - 2025**  
**BASIC ELECTRICAL ENGINEERING**  
**(Common for ECE, IT, CSD, CSC, CSM)**

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**


**(10 Marks)**

1. a) Draw the V-I characteristic of an Ideal voltage source. [1M]
- b) What is the time constant of the R-L series circuit? [1M]
- c) Define reactive power. [1M]
- d) What is the current relationship between the line and phase values of a 3-phase balanced delta connection? [1M]
- e) What is the efficiency of a transformer? [1M]
- f) What happens if d.c supply is connected to a transformer? [1M]
- g) What is the function of brushes in a d.c generator? [1M]
- h) What are the losses of a d.c motor? [1M]
- i) Define the slip of a 3-phase Induction Motor. [1M]
- j) What is the speed of a synchronous generator? [1M]

**PART-B**


**(50 Marks)**

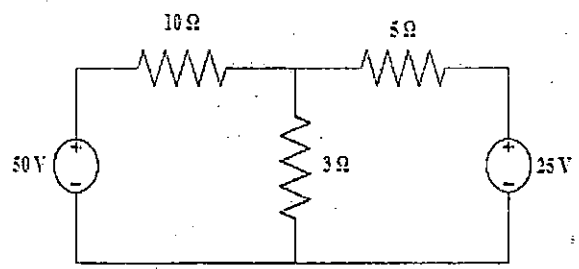- 2.a) State and explain Kirchoff's laws. [5M]
- b) Find the current flowing through each resistance using Kirchoff's laws. [5M]



OR

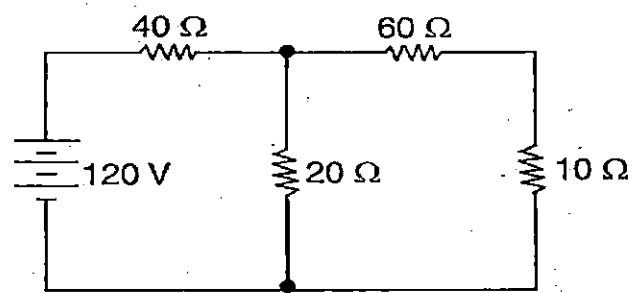- 3.a) State and explain the superposition theorem. [5M]
- b) Using Norton's theorem, find the current in a 10 Ω resistor in the circuit shown in the figure below. [5M]



- 4.a) Define the average value and derive the expression for the same of a sinusoidal alternating quantity. [6M]  
 b) A series R-C circuit having a resistance of  $8\ \Omega$  and  $6\ \Omega$  capacitive reactance is fed by  $230\ \text{V}$ ,  $1\text{-}\phi$  supply. Find the current, power drawn by the circuit and power factor. [4M]
- OR**
- 5.a) Derive resonant frequency, bandwidth of a series R-L-C resonance circuit. [6M]  
 b) Determine the power factor and the input power for a circuit with  $v = 50 \sin(\omega t + 10^\circ)$  and  $I = 2 \sin(\omega t + 40^\circ)\ \text{A}$ . [4M]
- 6.a) Derive an e.m.f equation of a 1-phase transformer. [6M]  
 b) The maximum flux density in the core of a  $220/4400\ \text{V}$ ,  $50\ \text{Hz}$  single-phase transformer is  $1.25\ \text{Wb/m}^2$ . If the emf per turn is  $6\ \text{V}$ , determine (i) primary and secondary turns and (ii) the area of the core [4M]
- OR**
- 7.a) Draw the equivalent circuit of a single-phase transformer. [6M]  
 b) The iron and full-load copper losses in a  $100\ \text{KVA}$  single-phase transformer are  $400$  and  $600\ \text{W}$  respectively. Calculate the efficiency at half-full load,  $0.8\ \text{p.f. lag}$ . [4M]
8. Explain the construction and working of a d.c generator with a neat sketch. [10M]
- OR**
- 9.a) Derive an expression for the torque equation of a d.c motor. [6M]  
 b) Explain the significance of a back e.m.f in a d.c motor. [4M]
- 10.a) Draw the torque-slip characteristics of a 3-phase Induction motor. [5M]  
 b) Explain any one starter used in 3-phase Induction Motor. [5M]
- OR**
11. Explain the constructional details and working principle of 3-phase alternator. [10M]
- \*\*\*\*\*