

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
II-B.TECH-I-Semester End Examinations (Supply) - December- 2024
ELECTRONIC DEVICES AND CIRCUITS
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.
 Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(20 Marks)**

1. a) Define diffusion and transition capacitance. [2M]
- b) List out the different types of clipper circuits. [2M]
- c) Draw the symbols of NPN and PNP transistor. [2M]
- d) Define rise time and fall time for a transistor. [2M]
- e) Write the differences between BJT and FET. [2M]
- f) List out the applications of photo diode. [2M]
- g) Define an amplifier? List out the applications of amplifier. [2M]
- h) What is the need of coupling and bypass capacitors in CE amplifier? [2M]
- i) Draw the circuit diagram of common source JFET amplifier. [2M]
- j) Write the classification of MOSFET along with their symbols. [2M]

PART-B**(50 Marks)**

- 2.a) Explain PN junction diode in forward and reverse bias condition along with V-I characteristics. [7M]
 - b) Explain about load line analysis. [3M]
- OR**
3. Construct and explain the operation of half wave rectifier and derive the equation for ripple factor and efficiency. [10M]
 4. Explain the circuit for a common base configuration with their input and output characteristics. [10M]
- OR**
5. Explain in detail about self bias and derive its stability factor. [10M]
 6. What are the types of breakdown mechanisms in a Zener diode? Explain the reverse bias characteristics of Zener diode. [10M]
- OR**
7. Explain the construction and working principle of operation for N-channel JFET with its characteristics. [10M]
 8. Draw the BJT hybrid models for CE, CB & CC configurations. [10M]
- OR**
9. Draw the circuit diagram of a collector to base bias circuit of a CE amplifier and derive the expression for stability factor. [10M]
 10. Explain the operation of Enhancement mode MOSFET in detail along with its characteristics. [10M]
- OR**
11. Draw the circuit diagram of CS amplifier and explain its working operation. [10M]
