

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Supply) -June- 2025

ANALOG & DIGITAL ELECTRONICS

(Common to CSE, CSC)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) What is meant by “Acceptor” and “Donor”. [2M]
- b) Define Form factor and Peak factor. [2M]
- c) What is the need for biasing a transistor [2M]
- d) Give the differences in performance of an RC coupled amplifier over single stage amplifier. [2M]
- e) Why a field effect transistor is called so? [2M]
- f) Write the features CMOS technology. [2M]
- g) What is a Karnaugh map? [2M]
- h) List out the differences between DEMUX and MUX [2M]
- i) What is a sequential circuit? List the types of sequential circuits. [2M]
- j) Define synchronous counter. [2M]

PART-B

(50 Marks)

- 2.a) What is meant by tunneling? From the energy band diagram explain the V-I characteristics of a tunnel diode. [5M]
- b) Discuss the effect of temperature on PN Junction diodes. [5M]

OR

- 3.a) Draw the circuit diagram of an Full wave rectifier and explain its operation. [5M]
- b) A full wave rectifier has a load of $3.5\text{ k}\Omega$.If the diode resistance and secondary coil resistance together have a resistance of $800\ \Omega$ and the input voltage has a signal voltage of peak value 240 V , Calculate D.C. Power output, A.C. Power Input, Efficiency of the Rectifier [5M]
- 4.a) Draw a self bias circuit and derive the expression for the stability factor. [5M]
- b) What is thermal runaway? How can it be avoided? What are three factors contribute to thermal instability [5M]

OR

5. Derive the equation for the overall voltage gain of a multistage amplifier in terms of the individual voltage gains [10M]
6. Draw the small signal equivalent circuit of FET amplifier in CS connection and derive the equations for voltage gain ,Input impedance and output Impedance [10M]

OR

- 7.a) Convert octal number in binary [5M]
 (i)7013 (ii)1234
- b) Define logic gate and logic circuit? What are called universal logic gates? Why they are called so? [5M]

- 8.a) What is a multiplexer? Explain the operation of 4 to 1 line multiplexer. [5M]
b) Explain how a digital Demultiplexer can be realized using logic gates. [5M]

OR

- 9.a) Design a logic circuit with four input variables that will produce a 1 output when any three input variables are 1s. Use K-Map for simplifying the logic expression. [5M]
b) Draw the truth table of full adder circuit and design using NAND gates. [5M]

- 10.a) Show how a SR flip-flop can be constructed using NOR Gates? Explain the different states of the SR flip-flop. [5M]
b) What is Race-around condition? How can you overcome this effect in J-K flip-flop? Explain. [5M]

OR

11. Explain the operations of S-R Flip-Flop, J-K Flip-Flop with circuit diagrams and excitation tables. [10M]
