

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Supply) -June- 2025

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(MECH)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.


Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(20 Marks)**

1. a) Classify electrical circuit elements. [2M]
- b) Define peak value. [2M]
- c) Outline the function of cable. [2M]
- d) List the components of LT Switchgear. [2M]
- e) What is the function of DC motor? [2M]
- f) Show the transformer schematic diagram. [2M]
- g) Relate diode current and voltage. [2M]
- h) Summarize the operation of half-wave rectifier. [2M]
- i) Label the terminals of a bipolar junction transistor. [2M]
- j) Compare CE and CB characteristics of a transistor. [2M]

PART-B**(50 Marks)**

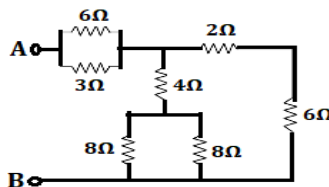- 2.a) Solve for the equivalent resistance between terminals A and B of the network shown below. [5M]



- b) Explain the Kirchhoff's laws? [5M]

OR

- 3.a) The rms current in a single phase AC network is given by 10 A when the applied rms voltage is 220 V and the power factor is 0.8. Solve for the apparent, reactive and the real powers. [6M]
- b) Relate voltage and currents in star and delta connections of three phase AC balanced system. [4M]
- 4.a) Discuss about types of wires and cables. [6M]
- b) Estimate the electricity bill amount for a month of 30 days, if the following appliances are used as specified. (i) 3 LED bulbs of 7 W for 5 hours, (ii) 3 tube lights of 50 W for 4 hours, (iii) A T.V. of 80 W for 6 hours, (iv) 2 fans of 60 W for 10 hours. Take the rate of electricity is Rs. 3.00 per unit. [4M]

OR

- 5.a) Discuss about power factor improvement. [6M]
- b) Explain the operation of ELCB with neat diagram? [4M]
- 6.a) Explain in detail about the losses in a transformer and calculation of efficiency? [6M]
- b) An 8-pole, 1200 rpm, DC generator has 500 armature conductors and a useful flux of 0.05 Wb per pole. Calculate the generated EMF when the armature is (i) Lap wound (ii) Wave wound. [4M]

OR

- 7.a) Explain the construction of 3-phase induction motor? [5M]
- b) Illustrate the working principle of synchronous generator. [5M]

8.a) Explain the operation of PN junction diode? [4M]

b) Compare the characteristics of center tapped transformer type and bridge type full wave rectifiers. [6M]

OR

9.a) Explain how Zener diode acts as a voltage regulator? [6M]

b) Compare ideal and practical diodes. [4M]

10.a) Illustrate the operation of a transistor as an amplifier. [5M]

b) Distinguish PNP and NPN transistors. [5M]

OR

11.a) What is FET and explain the working of FET? [6M]

b) Compare BJT and FET in all aspects. [4M]
