

## CMR ENGINEERING COLLEGE: : HYDERABAD

## UGC AUTONOMOUS

## II-B.TECH-I-Semester End Examinations (Supply) - June- 2025

## DIGITAL LOGIC DESIGN

## (CSD)

[Time: 3 Hours]

[Max. Marks: 60]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A****(10 Marks)**

1. a) What are the basic properties of Boolean algebra? [1M]
- b) Convert  $(AB)_{16} = ( )_2$ . [1M]
- c) State the limitations of Karnaugh map. [1M]
- d) What are called don't care conditions? [1M]
- e) Define Encoder. [1M]
- f) What do you mean by comparator? [1M]
- g) What are the classifications of sequential circuits? [1M]
- h) What is race-around condition? [1M]
- i) What are the types of ROM. [1M]
- j) What are identifiers? [1M]

**PART-B****(50 Marks)**

2. Perform the subtraction on the given unsigned binary numbers using the 2's complement:  
(i) 1001-110101      (ii) 101000-10101 [10M]

**OR**

3. State and prove Associate law and Distributive law using logic gate and truth table. [10M]
4. Simplify the Boolean function using K-map in products of sums form:  
 $F(w, x, y, z) = \sum m(2, 3, 10, 11, 12, 13, 14, 15)$ . [10M]

**OR**

5. Explain NAND-NOR implementations and design the circuit by Using NAND gates  
 $F = (X+Y) \cdot (X'+Y'+Z')$  [10M]

6. Draw the logic diagram of full subtractor and explain its operation. [10M]

**OR**

7. Using 8 to 1 multiplexer, realize the Boolean function  
 $T = f(w, x, y, z) = \sum m(0, 1, 2, 4, 5, 7, 8, 9, 12, 13)$ . [10M]

8. Explain the principle of RS Flip-flop with the help of a logic diagram and truth table. [10M]

**OR**

9. Explain the operation of a 4-bit universal shift register with D flip-flops. [10M]

10. What is ROM? Explain the different types of ROM's in detail. [10M]

**OR**

11. Define HDL and explain various HDL models for combinational circuits. [10M]

\*\*\*\*\*