

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Regular) -June- 2025

ELECTRONIC CIRCUIT ANALYSIS

(ECE)

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(10 Marks)**

1. a) List out different types of coupling used in Multistage amplifiers. [1M]
- b) Define gain bandwidth product of an amplifier. [1M]
- c) Write the expression for Feedback gain of a negative feedback amplifier. [1M]
- d) Compare the Current series and Current shunt feedback amplifiers. [1M]
- e) What is the condition for "Frequency of oscillation"? [1M]
- f) Classify different types of oscillators. [1M]
- g) Define a Q-factor of Tuned amplifier. [1M]
- h) Write the advantages transformer coupled amplifier. [1M]
- i) What are the some applications of Multi vibrators? [1M]
- j) Which amplifier is used in Miller time base generator? [1M]

PART-B**(50 Marks)**

2. Describe different methods used for coupling multistage amplifiers with their frequency response. [10M]

OR

3. Draw the hybrid π equivalent circuit of a transistor in Common Emitter configuration and explain the various parameters in it. [10M]
4. Draw and explain the four topologies of feedback amplifiers. [10M]

OR

5. Derive the input resistance, output resistance and voltage gain with feedback for Voltage shunt negative feedback amplifier using block diagram. [10M]
6. Draw and explain the operation of Hartley oscillator. [10M]

OR

7. Derive the expression for frequency of oscillations for RC phase shift Oscillator. [10M]
8. With a neat diagram, explain the principle of operation of class B push-pull amplifier and find its efficiency? [10M]

OR

9. With circuit diagram, explain the capacitance coupled single tuned amplifier. [10M]
10. Explain the operation of Bistable Multivibrator using transistors with neat sketch. [10M]

OR

- 11.a) Discuss operation of miller sweep generator. [5M]
- b) How to improve the linearity in time base generators? [5M]
