

Code No.: EC404PC

R20

H.T.No.

8

R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**

**II-B.TECH-II-Semester End Examinations (Supply) -June- 2025**

**ELECTRONIC CIRCUIT ANALYSIS**

**(ECE)**

**[Time: 3 Hours]**

**[Max. Marks: 70]**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(20 Marks)**

1. a) Why is a CE amplifier widely used? List out its main limitations. [2M]
- b) List out the features of Darlington pair. [2M]
- c) Draw the circuit of Voltage Shunt feedback amplifier. [2M]
- d) Define feedback factor of a feedback amplifier. [2M]
- e) What are the Classifications of oscillators? [2M]
- f) Draw the circuit of Hartley oscillator. [2M]
- g) List out the applications of tuned amplifier. [2M]
- h) Define conversion efficiency of power amplifier. [2M]
- i) What are the different names of Monostable multivibrator? [2M]
- j) Difference between Miller sweep & Bootstrap sweep circuit. [2M]

**PART-B**

**(50 Marks)**

2. Derive the expression for current gain, voltage gain, input resistance, output resistance of CE amplifier with emitter resistance using simplified h-parameter model. [10M]

**OR**

3. Explain the three types of coupling methods used in multistage amplifiers. [10M]

4. Draw the circuit for Current Series amplifier & derive the expressions for voltage gain, input resistance & output resistance for the circuit. [10M]

**OR**

5. A Voltage Series amplifier with internal amplifier has gain -200, input resistance is 5Kohms, output resistance is 20Kohms & bandwidth 50kohms and having feedback factor is -0.02. Find [10M]

(i) voltage gain with feedback (ii) input resistance with feedback (iii) output resistance with feedback

6. Derive the expression for the frequency of Colpitts oscillator. [10M]

**OR**

7. Explain the principle of Wein bridge oscillators & derive the expression of the frequency of oscillations. [10M]

8. With a neat diagram, Explain the principle of operation of Class-B Push pull amplifier and find its efficiency. [10M]

**OR**

9. Derive the expression for conversion efficiency for a Transformer coupled Class-A power amplifier. [10M]

10. Explain the working principle of Schmitt trigger circuit. [10M]

**OR**

11. Draw and explain the circuit of Astable Multivibrator with necessary waveform. [10M]

\*\*\*\*\*