

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Supply) -June- 2025

LINEAR IC APPLICATIONS

(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(20 Marks)**

1. a) Define an operational amplifier. [2M]
- b) Define input offset voltage. [2M]
- c) What are the different features of IC 723? [2M]
- d) What are the characteristics of a comparator? [2M]
- e) Discuss about all pass filters. [2M]
- f) What are the applications of VCO? [2M]
- g) Draw the functional diagram of 555 timers. [2M]
- h) What are the applications of astable multivibrator using 555 Timer? [2M]
- i) List different ADC and DACs. [2M]
- j) An 8 bit D/A converter as a resolution of 8mV/bit. Find the analog output voltage for the input 10111010. [2M]

PART-B**(50 Marks)**

2. Draw the circuit diagram of a two input non-inverting type summing amplifier and derive the expression for the output voltage. [10M]

OR

3. Explain in detail all the DC and AC characteristics of an ideal Op-Amp with relevant expressions. [10M]

4. Explain the working of instrumentation amplifier with suitable diagram. [10M]

OR

5. Draw the block diagram of Sample & Hold amplifier and explain its operation in detail. [10M]

- 6.a) Design an active high pass filter with cutoff frequency of 4KHz. [5M]
- b) How to generate a sawtooth wave form? Explain the working of such a circuit with neat circuit diagram. [5M]

OR

7. Design a wide band pass filter with $f_L=500$ Hz and $f_H = 2$ KHz, and a pass band gain of 5 for both sections of filter. Also determine the value of Q for the filter. [10M]

8. Draw the block diagram of IC565 PLL and explain about each block. Make circuit connections to track the input signal and explain its operation. [10M]

OR

- 9.a) Draw the circuit diagram of monostable multivibrator by using IC-555 timer and explain its operation. [7M]
- b) Obtain pulse width of output of IC-555 based monostable multivibrator for $C = 0.047\mu F$ and $R = 56K$. [3M]

10. Explain the working of R-2R ladder DAC with neat circuit diagram and write its limitations. [10M]

OR

11. Explain the working of dual slope ADC with neat circuit diagram and compare its performance with other ADC. [10M]
