

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**II-B.TECH-I-Semester End Examinations (Regular) - December- 2025**  
**ANALOG & DIGITAL ELECTRONICS**  
**(Common for IT, CSM)**

**[Time: 3 Hours]****[Max. Marks: 60]****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A****(10 Marks)**

- 1. a) Draw V-I characteristic of a p-n junction diode. [1M]
- b) Why is rectifier so named? [1M]
- c) What is an amplifier? [1M]
- d) Why biasing is necessary in amplifier circuits? [1M]
- e) Define the threshold voltage of a n-channel enhancement MOSFET. [1M]
- f) Draw basic CMOS logic circuit. [1M]
- g) What are the universal gates? Why they are called universal gates? [1M]
- h) List out the applications of multiplexer. [1M]
- i) Compare shift registers and ripple counters. [1M]
- j) What are programmable memories? [1M]

**PART-B****(50 Marks)**

- 2.a) Derive diode current equation. [5M]
- b) A silicon diode has a saturation current of  $7.5\mu\text{A}$  at room temperature 300 K. Calculate the saturation current at 400K. [5M]

**OR**

- 3. Explain the operation of Full wave rectifier and derive the expression for ripple factor of a full-wave center-tap rectifier with capacitor filter. [10M]
- 4. Derive the equation for the overall voltage gain of a multistage CE amplifier. [10M]

**OR**

- 5.a) What is DC load line and AC load line? Explain the criteria for fixing operating point. [5M]
- b) Explain the fixed bias and self-bias circuits in detail. [5M]

- 6. Illustrate in detail about small- signal model of MOSFET. [10M]

**OR**

- 7.a) With the help of truth tables and discuss the functionality of the following logic gates: (i) OR Gate. (ii) NOR Gate. and (iii) XOR Gate. [5M]
- b) Draw the circuit diagram of basic CMOS Gate and explain its operation. [5M]

- 8. Obtain the Standard POS and SOP expressions for the function  $F(A,B,C,D) = A'BD' + ACD + B'CD + A'C'D$ . [10M]

**OR**

- 9. Design a 2-bit comparator using gates. [10M]

- 10. Draw the logic symbol, characteristics table and derive characteristics equation of S-R and J-K flip-flop. [10M]

**OR**

- 11. Design Asynchronous up/down counter using JK flip-flop. [10M]

\*\*\*\*\*