

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

I-B.TECH-II-Semester End Examinations (Supply) - December- 2025

BASIC ELECTRICAL ENGINEERING

(Common for CSM, ECE, AI&DS)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(20 Marks)

1. a) State Kirchhoff's laws. [2M]
- b) Define dependent sources. [2M]
- c) Write the formulae to find out the RMS and Average value of a sinusoidal waveform. [2M]
- d) A sinusoidal voltage is applied to the inductor of 2mH, the frequency is 3KHz. Determine the inductive reactance. [2M]
- e) Why a transformer is not being operated on dc supply? [2M]
- f) List out various losses in a transformer. [2M]
- g) State Fleming's Right hand rule. [2M]
- h) List out the applications of DC Series Motor. [2M]
- i) Define the slip of an induction Motor. [2M]
- j) A 3-phase, 4-pole, 50 Hz induction motor is running at 1455 rpm. Find the synchronous speed and slip. [2M]

PART-B

(50 Marks)

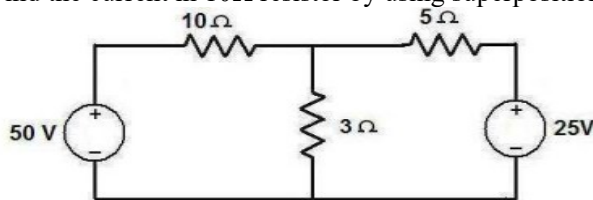2. Find the current in 10Ω resistor by using superposition theorem. [10M]



OR

3. Derive the time domain analysis of RL circuit with DC excitation. [10M]
4. Derive the RMS value and average value for sinusoidal waveform and find form factor. [10M]
5. Explain the response to sinusoidal excitation for a pure resistance circuit and pure inductance circuit. [10M]

OR

6. Explain the operation of a single-phase transformer on lagging load and draw the relevant phasor diagram. [10M]

OR

7. Explain the construction and working of an auto transformer. [10M]
8. Derive the EMF Equation of a DC machine. [10M]

OR

9. Describe the constructional details of DC Machine with neat sketches. [10M]
10. Explain the working of an alternator. [10M]

OR

11. Sketch the Torque - Slip characteristics of 3- phase induction motor and explain. [10M]
