

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Supply) - December- 2025

ELECTRONIC CIRCUIT ANALYSIS

(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) List out the types of distortions occurred in amplifiers. [2M]
- b) Define gain bandwidth of the amplifier. [2M]
- c) Define concept of feedback. [2M]
- d) Draw the block diagram of voltage series feedback amplifier. [2M]
- e) Explain why LC oscillators are not used at low frequencies. [2M]
- f) Differences between Hartley and Colpitts oscillators. [2M]
- g) What is class-A power amplifier? [2M]
- h) Define stagger tuned amplifier. [2M]
- i) Why trigger is needed in multivibrators? [2M]
- j) What are the applications of monostable multivibrator? [2M]

PART-B

(50 Marks)

2. Derive the expression for the CE short-circuit current gain as a function of frequency. [10M]

OR

3. Derive expressions for overall voltage gain and overall current gain of a two stage RC coupled amplifier. [10M]

4. Derive the expression for voltage gain, input resistance, output resistance of the current shunt feedback amplifier. [10M]

OR

5. An amplifier has a voltage gain of 400, $f_1=50\text{Hz}$, $f_2=200\text{kHz}$ and distortion of 10% without feedback. Determine the amplifier voltage gain and D_f when a negative feedback is applied with feedback ratio of 0.01. [10M]

6. Draw the RC-phase shift oscillator and derive the condition for oscillations. [10M]

OR

7. With the help of suitable schematic explain the operation of a Wien Bridge oscillator and derive an expression for its frequency of operation. [10M]

8. Explain the operation of a class B push-pull power amplifier and derive its conversion efficiency and also list out its advantages and disadvantages. [10M]

OR

9. Describe the heat sinks for power amplifiers. [10M]

10. Explain the operation of astable multivibrators with neat diagram, waveforms. [10M]

OR

11. Explain the operation of Bootstrap time base generator circuit with neat diagram. [10M]
