

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**

**II-B.TECH-II-Semester End Examinations (Supply) -December- 2025**

**ELECTRONIC CIRCUIT ANALYSIS**

**(ECE)**

**[Time: 3 Hours]**

**[Max. Marks: 60]**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(10 Marks)**

1. a) Draw the circuit diagram of Darlington Pair. [1M]
- b) Classify different types of amplifiers. [1M]
- c) What are the different types of Feedback Amplifiers? [1M]
- d) What is effect of negative feedback on amplifier gain? [1M]
- e) State Barkhausen criterion of oscillator. [1M]
- f) Classify different types of oscillator [1M]
- g) What is mean by crossover distortion? [1M]
- h) What are the limitations of Single tuned amplifier? [1M]
- i) Define multivibrator. [1M]
- j) What are the applications of Schmitt trigger? [1M]

**PART-B**

**(50 Marks)**

- 2.a) Derive the  $A_I$ ,  $A_v$  for two stages RC coupled amplifier and draw its frequency response. [7M]
- b) Draw the circuit diagram of Direct Coupled Amplifier and explain its operation in detail. [3M]

**OR**

- 3.a) Draw the hybrid-II model of common emitter configuration and describe each component in the  $\Pi$ -model. [7M]
- b) Derive the equation for voltage gain bandwidth product for CE amplifier. [3M]
4. Explain the principle of negative feedback in amplifiers. Show quantitatively the effect of negative feedback on (i) Gain (ii) Stability (iii) Noise (iv) Distortion. [10M]

**OR**

5. Draw the block diagrams of four types of negative feedback amplifier circuits and explain the advantages and disadvantages with necessary derivations. [10M]
6. Starting from the description of a generalized Oscillator, derive the expression for frequency of Oscillation in a Colpitts Oscillator. [10M]

**OR**

- 7.a) Derive the expression for frequency of oscillation of BJT RC phase-shift oscillator with necessary explanation. [7M]
- b) A crystal oscillator has the following parameters:  $L=0.33H$ ,  $C=0.065pF$ ,  $C_m=1.0pF$  and  $R=5.5$  k ohm.
  - i) Find the series resonant frequency. [3M]
  - ii) Find the Q of the crystal. [3M]

8. Explain the operation of a class A push-pull power amplifier and list out its advantages and disadvantages. [10M]

**OR**

- 9.a) Explain stagger tuned amplifier? Draw its frequency response. What applications are of stagger tuned amplifier? [7M]
- b) Discuss in detail about frequency response of tuned amplifiers. [3M]

10. Draw and explain the working principle of astable multivibrator circuit derive the expression for its pulse width. [10M]

**OR**

- 11.a) Draw the circuit diagram of Bootstrap time base generator and explain its operation with necessary waveforms. [7M]
- b) Compare the voltage and current time base generators with some examples. [3M]

\*\*\*\*\*