

**CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS**

**II–B.TECH–I–Semester End Examinations (Supply) - June- 2025
ELECTRONIC DEVICES AND CIRCUITS
(ECE)**

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(20 Marks)**

1. a) Define Diffusion and Transition capacitance. [2M]
- b) List out the different types of clipper circuits. [2M]
- c) Draw the symbols of NPN and PNP transistor? [2M]
- d) Define rise time and fall time for a transistor? [2M]
- e) Write the differences between BJT and FET? [2M]
- f) List out the applications of Photo Diode. [2M]
- g) Define an amplifier? List out the applications of amplifier. [2M]
- h) What is the need of coupling and bypass capacitors in CE amplifier? [2M]
- i) Draw the circuit diagram of common source JFET amplifier? [2M]
- j) Write the classification of MOSFET along with their symbols? [2M]

PART-B**(50 Marks)**

- 2.a) Explain about the PN junction diode in forward and reverse bias conditions and draw its V-I characteristics. [07M]
- b) Explain about load line analysis. [03M]

OR

3. Construct and explain the operation of Half Wave Rectifier and derive the equation for ripple factor and efficiency. [10M]
4. Explain the circuit for a common base configuration with their input and output characteristics. [10M]

OR

5. Explain in detail about self – bias and derive its stability factor. [10M]
6. What are the types of breakdown mechanisms in a Zener diode? Explain the reverse bias characteristics of Zener diode. [10M]

OR

7. Explain the construction and working principle of operation for p-channel JFET with its characteristics. [10M]
8. Draw the BJT hybrid models for CE, CB & CC configurations. [10M]

OR

9. Draw the circuit diagram of a collector to base bias circuit of a CE amplifier and derive the expression for stability factor. [10M]
10. Explain the operation of Enhancement mode MOSFET in detail along with its characteristics. [10M]

OR

11. Draw the circuit diagram of CS amplifier and explain its working operation. [10M]
