

L8B

R09

Code No: 09A60502

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B. Tech III Year II Semester Examinations, May/June, 2013

VLSI Design

(Computer Science and Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Compare the performance of various oxidation process. [15]
- b) Compare MOS and CMOS and Bi-CMOS technologies. [15]
- 2. Explain the working of Bi-CMOS inverter using appropriate transfer characteristics. [15]
- 3.a) Explain the different types of contact cuts used in CMOS design and fabrication. [15]
- b) Draw the stick diagram layout of an 8:1 inverter using appropriate transfer characteristics. [15]
- 4. Explain CMOS domino logic circuit with an example. Compare its performance over that of CMOS logic. [15]
- 5. Design a 4-bit synchronous up/down counters using adders and registers. Implement an adder cell and a register cell using transmission gates and explain. [15]
- 6.a) Discuss the need of stick diagrams and explain with a example. [15]
- b) Explain the need for low power design circuits in VLSI chip fabrication. [15]
- 7. Illustrate the simultaneous minimization of three functions.
 $f_1(A,B,C,D) = \sum_m(0,2,7,10) + d(12,15)$
 $f_2(A,B,C,D) = \sum_m(2,4,5) + d(6,7,8,10)$
 $f_3(A,B,C,D) = \sum_m(2,7,8) + d(0,5,13)$ and implement using suitable PAL. [15]
- 8. What is fault simulation? Explain briefly fault models. Explain the various stick at fault models with suitable examples. [15]

BR BR BR BR BR BR BR BR

BR BR BR BR BR BR BR BR