

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Write the volt-ampere relationship of R, L and C elements.
- b) Explain the independent and dependent sources.
- 2.a) Show that the Line voltage = 1.732 times the phase voltage in a balanced star connected system.
- b) A symmetrical 400 v, 3-phase, supplies a star connected load with $Z_R = 5 \Omega$, $Z_Y = j5 \Omega$ and $Z_B = -j5 \Omega$. Determine the line currents the phase sequence is RYB.
- 3.a) Define the following terms:
 - i) RMS value
 - ii) Average value
 - iii) Form factor
 - iv) Peak factor.
- b) Determine the average and effective values of saw-tooth waveform as shown in below Figure 1.

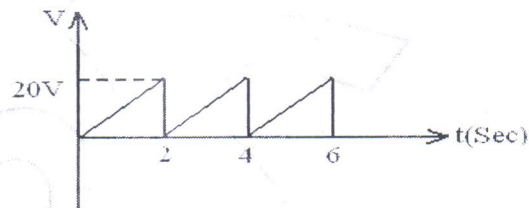


Figure 1

4. A series RLC circuit with $R = 3\Omega$, $L = 1H$ and $C = 0.5F$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped.
- 5.a) Define and explain self-inductance and mutual-inductance.
- b) Two coupled coils of $L_1 = 0.8 H$ and $L_2 = 0.2 H$ have a coupling coefficient $k = 0.9$. Find the mutual inductance M .
- c) State and explain Faraday's laws of electromagnetic induction.
- 6.a) State and explain Tellegens theorem.
- b) When the load impedance R draws the maximum power? Find the maximum power delivered to the load by using maximum power transfer theorem for the given network shown in Figure 2.

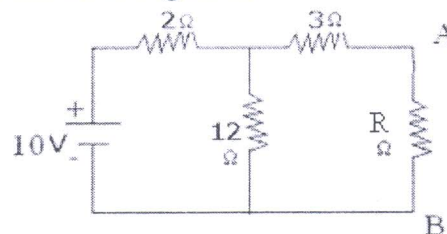


Figure 2

- 7.a) Define and explain the following with an example:
- Oriented Graph
 - Tree of a Graph
 - Tie set and a basic Tie set
 - Cut set and a basic Cut set.
- b) Find the values of V_1 and V_2 in the network shown in Figure 3 using Nodal method of analysis.

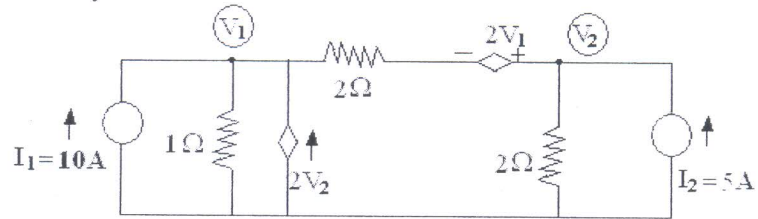


Figure 3

8. Find the current through the capacitor and voltage across 4Ω resistance of the AC network shown in Figure 4 by using superposition theorem.

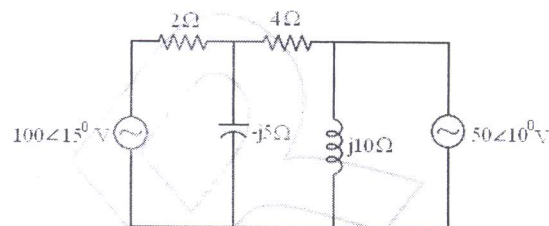


Figure 4

---oo0oo---