

B.Tech II Year I Semester Examinations, May-June, 2012

ELECTRONIC DEVICES AND CIRCUITS

(COMMON TO BME, CSE, EEE, ECE, ECC, EIE, ETM, IT, ICE, MCT)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Explain the concept of diode capacitance. Derive expression for transition capacitance?
- b) Find the value of D.C. resistance and A.C resistance of a Germanium junction diode at 25°C with reverse saturation current, $I_o = 25\mu\text{A}$ and at an applied voltage of 0.2V across the diode. [8+7]
2. Define the following terms and derive the equations with respect to half-wave rectifier:
 - i) Ripple factor
 - ii) Peak inverse voltage
 - iii) Rectification efficiency
 - iv) % Regulation. [15]
- 3.a) With neat sketches and necessary waveforms, explain the input and output characteristics of a BJT in CB configuration. Also derive expression for output current.
- b) Derive the relation among α , β and γ . [10+5]
- 4.a) Explain the basic requirements of transistor biasing. Verify these requirements in collector to base bias circuit.
- b) Design a fixed bias circuit using silicon transistor, with the following specifications: $V_{CC} = 16\text{V}$, $V_{BE} = 0.7\text{V}$, $V_{CEQ} = 8\text{V}$, $I_{CQ} = 4\text{mA}$ & $\beta = 50$. [8+7]
5. Draw the circuit diagram, AC equivalent & small signal equivalent of Common Base amplifier using accurate h-parameter model. Derive expressions for A_{Vs} , A_{Is} , R_I & R_O . [15]
- 6.a) Explain the construction & operation of an N-channel enhancement and depletion MOSFET with the help of static drain characteristics and transfer characteristics.
- b) Define pinch-off voltage and transconductance in field effect transistors. [12+3]
- 7.a) Draw the small-signal model of common drain FET amplifier. Derive expressions for voltage gain and output resistance.
- b) Calculate voltage gain $A_V = V_O/V_i$ and R_O at 1KHz for the circuit shown in Figure.1. FET parameters are $g_m = 2\text{mA/V}$ and $r_d = 10\text{k}$. Neglect capacitances. [8+7]

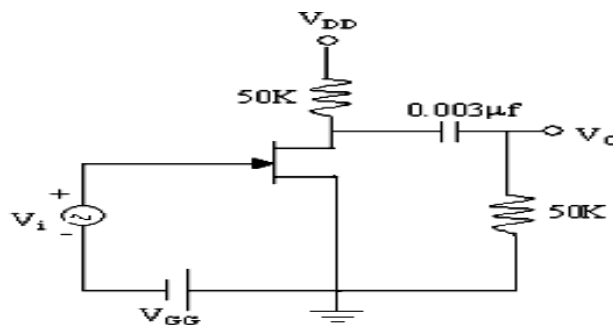


Figure.1

8. With neat energy band diagrams, explain the V-I characteristics of Tunnel diode in detail. Also explain the negative-resistance region in the characteristics and applications of Tunnel diode. [15]

B.Tech II Year - I Semester Examinations, May-June, 2012**ELECTRONIC DEVICES AND CIRCUITS****(COMMON TO BME, CSE, EEE, ECE, ECC, EIE, ETM, IT, ICE, MCT)****Time: 3 hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

- - -

- 1.a) What do you understand by depletion region at p-n junction? What is the effect of forward and reverse biasing of p-n junction on the depletion region? Explain with necessary diagrams.
- b) Explain Zener and avalanche breakdown mechanisms in detail. [8+7]
- 2.a) Draw the circuit diagram of full-wave rectifier with inductor filter. Explain its operation with necessary equations.
- b) A HWR circuit supplies 100mA DC current to a 250Ω load. Find the DC output voltage, PIV rating of a diode and the r.m.s. voltage for the transformer supplying the rectifier. [8+7]
- 3.a) With neat sketches and necessary waveforms, explain the input and output characteristics of a BJT in CE configuration. Also derive expression for output current.
- b) Calculate the collector current and emitter current for a transistor with $\alpha = 0.99$ and $I_{CBO} = 50\mu A$ when the base current is $20\mu A$. [10+5]
- 4.a) What is thermal runaway in transistors? Obtain the condition for thermal stability in transistors.
- b) Design a self bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications: $V_{CC} = 16V$, $V_{BE} = 0.7V$, $V_{CEQ} = 8V$, $I_{CQ} = 4 mA$ & $\beta = 50$. [6+9]
5. Draw the circuit diagram, AC equivalent & small signal equivalent of Emitter Follower amplifier using accurate h-parameter model. Derive expressions for A_{Vs} , A_{Is} , R_I & R_O . [15]
- 6.a) With the help of neat sketches and characteristic curves explain the construction & operation of a JFET and mark the regions of operation on the characteristics.
- b) Derive expression for transconductance in a field effect transistor. [10+5]
- 7.a) Draw the small-signal model of common source FET amplifier. Derive expressions for voltage gain and output resistance.
- b) Give the UJT symbol and simplified equivalent circuit with external resistors included. Describe its negative-resistance nature, with the help of V-I characteristics. [7+8]
- 8.a) With neat sketches, explain the principle of operation of Schottky Barrier Diode.
- b) With neat sketches, explain V-I characteristics of semiconductor Photo Diode. [8+7]

B.Tech II Year - I Semester Examinations, May-June, 2012**ELECTRONIC DEVICES AND CIRCUITS**

(COMMON TO BME, CSE, EEE, ECE, ECC, EIE, ETM, IT, ICE, MCT)

Time: 3 hours**Max. Marks: 75**

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Explain about various current components in a forward biased p-n junction diode.
- b) With neat sketches and necessary waveforms explain about the regulation characteristics of Zener diode. [7+8]

- 2.a) Draw the circuit of full-wave rectifier with capacitor filter. Explain its operation with necessary equations.
- b) A full wave rectifier circuit uses two silicon diodes with a forward resistance of 20Ω each. A DC voltmeter connected across the load of $1K\Omega$ reads 55.4 volts. Calculate
 - i) I_{rms}
 - ii) Average voltage across each diode
 - iii) ripple factor
 - iv) Transformer secondary voltage rating. [7+8]

- 3.a) With neat sketches and necessary waveforms, explain the input and output characteristics of a BJT in CE configuration. Also derive expression for output current.
- b) The reverse leakage current of the transistor when connected in CB configuration is $0.2 \mu A$ while it is $18 \mu A$ when the same transistor is connected in CE configuration. Calculate α and β of the transistor. [10+5]

- 4.a) Explain how I_{CO} variations are compensated with the help of diode and thermistor in transistor biasing circuits?
- b) Design a collector to base bias circuit using silicon transistor to achieve a stability factor of 20, with the following specifications: $V_{CC} = 16V$, $V_{BE} = 0.7V$, $V_{CEQ} = 8V$, $I_{CQ} = 4 mA$ & $\beta = 50$. [7+8]

5. Draw the basic circuit, ac equivalent and h-parameter model of a Common Emitter amplifier. Derive expressions for A_{Vs} , A_{Is} , R_I & R_O . [15]

- 6.a) Explain the construction & operation of an P-channel enhancement and depletion MOSFET with the help of static drain characteristics and transfer characteristics.
- b) Explain why field effect transistor is called as unipolar and voltage controlled device. [12+3]

- 7.a) Draw the small-signal model of common gate FET amplifier. Derive expressions for voltage gain and input resistance.
- b) A Common Source FET amplifier circuit shown in Figure.1 with unbypassed R_S has the following circuit parameters: $R_d = 15K$, $R_S = 0.5K$, $R_g = 1M$, $r_d = 5K$, $g_m = 5mS$ and $V_{DD} = 20 V$. Calculate A_V & R_O . [8+7]

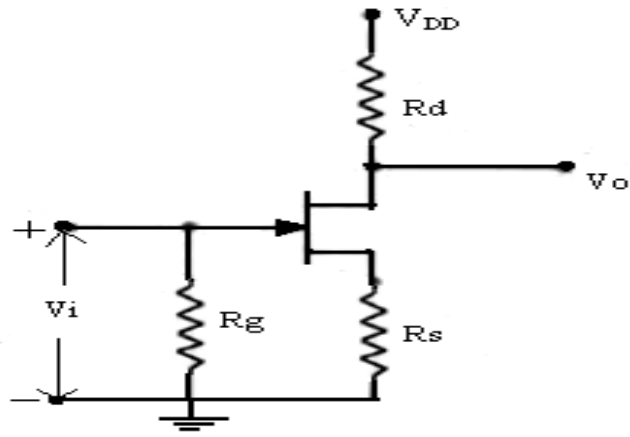


Figure.1

8. With neat energy band diagrams, explain the V-I characteristics of Tunnel diode in detail. Also explain the negative-resistance region in the characteristics. [15]

B.Tech II Year - I Semester Examinations, May-June, 2012**ELECTRONIC DEVICES AND CIRCUITS****(COMMON TO BME, CSE, EEE, ECE, ECC, EIE, ETM, IT, ICE, MCT)****Time: 3 hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

- - -

- 1.a) With neat sketches and necessary waveforms explain the volt ampere characteristics of PN diode.
- b) Explain the temperature dependence of VI characteristics of PN diode.
- c) Compare ideal and practical diodes. [8+4+3]

- 2.a) Draw the circuit of full-wave rectifier with L-section filter and derive expression for its ripple factor.
- b) A 230 V, 60Hz voltage is applied to the primary of a 5:1 step down, center tapped transformer used in a full wave rectifier having a load of 900Ω . If the diode resistance and the secondary coil resistance together has a resistance of 100Ω , determine
 - i) dc voltage across the load.
 - ii) dc current flowing through the load.
 - iii) dc power delivered to the load.
 - iv) PIV across each diode. [7+8]

- 3.a) With the help of a neat diagram explain different current components in an NPN bipolar junction transistor.
- b) With reference to bipolar junction transistors, define the following terms and explain.
 - i) Emitter efficiency.
 - ii) Base Transportation factor.
 - iii) Large signal current gain. [9+6]

- 4.a) Explain the basic requirements of transistor biasing. Verify these requirements in Emitter feedback bias circuit.
- b) An NPN Silicon transistor with $\beta=50$ is used in a common emitter circuit with $V_{CC}=10V$, $R_C=2K$. The bias is obtained by connecting a $100K$ resistance from collector to base. Find
 - i) Q-Point
 - ii) Stability factor, S [8+7]

- 5.a) Compare CB, CE and CC amplifiers in view of A_v , A_i , R_i & R_o .
- b) Estimate A_v , A_i , R_i & R_o in an Emitter Follower circuit with $R_E = 1K$, $h_{ie} = 1100\Omega$, $h_{fe} = 50$, $h_{re} = 2.4 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$. [7+8]

- 6.a) With neat sketches, necessary equations explain the drain & transfer characteristics of MOSFET in enhancement mode.
- b) Why is a Field Effect Transistor called unipolar & voltage controlled device? Explain the drain & transfer characteristics of a JFET in detail. [7+8]

- 7.a)
 - i) Give symbol of UJT and mark required polarities for operation.
 - ii) Explain how the UJT can be used as a negative-resistance device with the aid of static characteristics.
- b) A Common Drain FET amplifier circuit shown in Figure.1 has the following circuit parameters: $R_S = 0.5K$, $R_g = 1M$, $r_d = 5K$, $g_m = 5mS$ and $V_{DD} = 20 V$. Calculate A_v & R_o . [8+7]

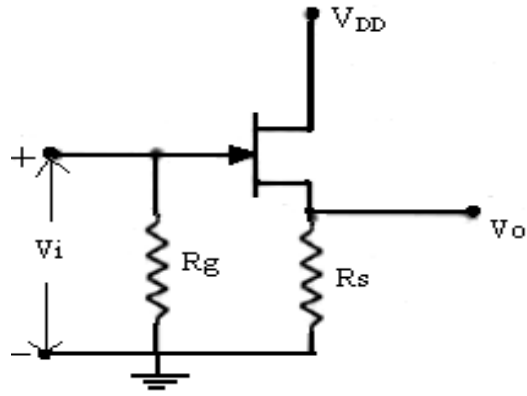


Figure.1

- 8.a) Draw the structure and two-transistor model of SCR, explain its operation with help of V-I characteristics.
- b) Explain the operation of varactor diode with the help of neat diagrams. [10+5]
