

B.Tech II Year - II Semester Examinations, April-May, 2012

STRUCTURED DIGITAL SYSTEM DESIGN

(Common to ECC, EIE, ICE)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- - -

- 1.a) What are the advantages of digital systems?
 b) Convert the number $(0.875)_{10}$ into its:
 i) Binary ii) trinary iii) quinary
 iv) Octal equivalents using the multiplication method.
 c) Design a Carry Look-ahead adder and explain its operation. [4+4+7]
- 2.a) Compare Open collector and Tristate output devices.
 b) Explain the practical aspects of Wired Logic and Bus oriented structures.
 c) Define
 i) Fan-in ii) Fan-out
 iii) Propagation Delay iv) Noise Margin. [4+5+6]
- 3.a) Explain the need for sequential machines.
 b) Design any two oscillator circuits suitable for digital system clock.
 c) What is a race around condition? How is it avoided? Explain. [4+6+5]
- 4.a) The state equations and output equation of a sequential circuit are:
 $J_A = (B'C + B'X)$; $K_A = B$; $J_B = (AB' + B'C)$; $K_B = B$; $J_C = A'C$; $K_C = (B + X')$,
 Output = $ABCX$ (Where X is the external input). Realize the circuit.
 b) With a suitable example, explain the partitioning procedure for state minimization. [7+8]
- 5.a) Design a 3-bit modulo 6 unit distance counter with a Synchronous Clear.
 b) Design a 4-bit parallel-in serial-out shift register and explain its operation. [8+7]
- 6.a) Explain the steps involved in the controller design phase.
 b) Explain the first cut flow diagram for a 2's complement system.
 c) How to specify the system controller states using MDS diagram. [5+5+5]
- 7.a) Explain the process of synchronizing two systems.
 b) Write a short note on Hand Shake.
 c) Explain the sequential machine with an
 i) Output holding register and asynchronous input holding register
 ii) Asynchronous SET/RESET register. [4+4+7]
- 8.a) Discuss in detail about the application of MSI Multiplexers in System controller.
 b) Design a four-bit BCD to Excess-3 code converter and implement it using a (4×4) ROM. [8+7]

B.Tech II Year - II Semester Examinations, April-May, 2012
STRUCTURED DIGITAL SYSTEM DESIGN
(Common to ECC, EIE, ICE)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Define mnemonic and polarized mnemonic.
- b) Implement the following Boolean function using 8-to-1 multiplexer.
 $F(A,B,C,D) = \sum m(0,5,6,13,14)$
- c) Reduce the following Boolean expression using the theorems and identities
 $F = AB + C\bar{D}B + \bar{A}C\bar{D}$ [3+8+4]
- 2.a) Draw schematic diagram for tri-state buffer and explain the its operation.
- b) What are the practical aspects considered in designing the combinational circuits?
- c) Compare the open-collector and tri-state bus system. [6+3+6]
- 3.a) Draw a timing diagram and illustrate SETUP time and HOLDING time. Give a qualitative description of each and how these specifications relate the hardware of the Flip-Flop.
- b) Using timing diagram, analyze the D-Latch Flip-flop. Include propagation Delay in your analysis. [7+8]
- 4.a) Using the state diagram make state assignment for the given state diagram as shown in Fig-1.
- b) Derive the next state maps for the state assignment made from the above obtained state assignment. [8+7]

 


Fig-1

- 5.a) Design a twisted ring counter which will provide the following waveform shown in Fig-2. Make certain the counter is self-correcting.

 


Fig-2

- b) Design an odd length (modulo 7) ring counter which is initialized or reset to state 7 (111). [8+7]

- 6.a) Explain the Multi –Input System Controller design phases.
- b) Illustrate the possible fault caused by an asynchronous input X changing just to the minimum set-up time limits of the D Flip-Flop. [7+8]
7. Design steps for the design of the controller and system for a high speed UART (Universal Asynchronous Receiver and Transmitter) able to send and receive serial data at a 1MHz rate. [15]
8. Implement the following controller using the indirect addressed multiplexer. The controller and system will add two four-bit unsigned numbers ($B_3B_2B_1B_0$ and $A_3A_2A_1A_0$) which are stored in two separate four-bit PIPO's. [15]

B.Tech II Year - II Semester Examinations, April-May, 2012
STRUCTURED DIGITAL SYSTEM DESIGN
(Common to ECC, EIE, ICE)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Define truth-table. What are the uses of truth tables?
- b) Implement the following Boolean function using one 74154 IC (4-to-16) decoder with low asserted outputs

$$F(A,B,C,D) = \sum m(1,4,6,8,11,13,14)$$

- c) Implement the following Boolean function with NOR gates

$$F = C + AB + AD(B + \bar{C})$$

[2+8+5]

- 2.a) Implement F(L) and F(H) with an A-O-I device

	AB			
C	0	1	1	1
	0	0	0	1

where F(L) and F(H) are the functions obtained from minterm and maxterm expressions of the above K-Map respectively.

- b) Define fan-out, fan-in, standard load and propagation delay. [8+7]

- 3.a) Define the following terms:

- i) Release time
- ii) Setup time
- iii) Transition time
- iv) Recovery time.

- b) Using timing diagram, analyze the T Flip-flop. Include propagation delay in your analysis, illustrating the undesirable mode of operation (oscillation or hang) in it. [8+7]

- 4. Design a block diagram and a state diagram for a circuit which samples (with system CLK) an input line [x=1(L)]. This system is to give an indicator (SEQDET(H)) each time the three-bit sequence 110 is detected in a continuous data stream. [15]

- 5.a) Using universal shift register such as 74194 IC (four-bit multi-mode) design a self-correcting modulo ring counter.

- b) A stepper motor drive circuit requires the following waveforms shown in Fig.1 (four signal lines) as inputs. Design a special sequence generator which will provide the necessary signals for this stepper motor drive. [7+8]

 


Fig. 1

6. Design a square wave duty cycle discriminator system controlled by a system controller. This system is to measure the time difference between alternate low and high portions of a low frequency quasi square wave signal (0.1 to 100Hz). [15]
7. Design a four-way traffic light controller, one that will handle traffic flow at high rates in any directions. Associate a left turn with all 4 directions as well as a pedestrian cross walk switch. [15]
- 8.a) Write short notes on Configurable memories.
b) Implement the following expression with PLA

$$F = \overline{A}\overline{B} + BC + \overline{B}\overline{C}$$

[7+8]
