

**B.Tech II Year - II Semester Examinations, April/May-2012**  
**ELECTRICAL AND ELECTRONICS ENGINEERING**  
**(AERONAUTICAL ENGINEERING)**

**Time: 3 hours****Max. Marks: 80**

**Answer any five questions**  
**All questions carry equal marks**

- - -

- 1.a) Explain the principle of generation of sinusoidally alternating voltages.  
b) Derive expression for power in three phase system. [8+8]
  
- 2.a) Currents through three parallel connected impedances are  $i_1(t) = 300 \sin(\omega t + 30^\circ)$ ,  $i_2(t) = 200 \sin(\omega t + 120^\circ)$  and  $i_3(t) = 175 \cos(\omega t + 45^\circ)$ . Determine the total current. Also draw the phasor diagram.  
b) What are the different types of generators? Explain in detail. [8+8]
  
- 3.a) Derive expression for torque equation of D.C. Motor.  
b) A 4 pole DC generator with a shunt field resistance of  $100 \Omega$  and armature resistance of  $1 \Omega$  has 378 wave connected conductors in its armature. The flux per pole is  $0.02 \text{ Wb}$ . If a load resistance of  $10 \Omega$  is connected across the armature terminals and the generator is driven at 100 rpm, calculate the power absorbed by the load. [6+10]
  
- 4.a) Derive E.M.F. equation of single phase transformer.  
b) Explain the principle of operation of three phase induction motor. [8+8]
  
- 5.a) With the help of circuit diagram, explain the procedure of conducting open circuit test on single phase transformer.  
b) Explain the procedure of determining voltage regulation of alternator. [8+8]
  
6. A 200/440 V, 50 Hz, 1-phase transformer on test gave the following results:  
O.C. Test (L.V. Side): 20 V, 0.75 A, 80 W  
S.C. Test (H.V. Side): 20 V, 12 A, 100 W. Find voltage regulation and efficiency at 0.8 p.f. lagging and full load. [16]
  
- 7.a) With the help of circuit diagram explain the procedure of obtaining V-I characteristics of P-N Junction diode.  
b) With an example, explain intrinsic and extrinsic semiconductors. [8+8]
  
8. Write short notes on the following:  
a) Zener diode  
b) BJT  
c) Applications of CRO. [5+5+6]

\*\*\*\*\*

Code No: RR222104

RR

SET-2

**B.Tech II Year - II Semester Examinations, April/May-2012**  
**ELECTRICAL AND ELECTRONICS ENGINEERING**  
**(AERONAUTICAL ENGINEERING)**

**Time: 3 hours**

**Max. Marks: 80**

**Answer any five questions**  
**All questions carry equal marks**

---

- 1.a) Derive expression for torque equation of D.C. Motor.  
b) A 4 pole DC generator with a shunt field resistance of  $100 \Omega$  and armature resistance of  $1 \Omega$  has 378 wave connected conductors in its armature. The flux per pole is  $0.02 \text{ Wb}$ . If a load resistance of  $10 \Omega$  is connected across the armature terminals and the generator is driven at  $100 \text{ rpm}$ , calculate the power absorbed by the load. [6+10]
- 2.a) Derive E.M.F. equation of single phase transformer.  
b) Explain the principle of operation of three phase induction motor. [8+8]
- 3.a) With the help of circuit diagram, explain the procedure of conducting open circuit test on single phase transformer.  
b) Explain the procedure of determining voltage regulation of alternator. [8+8]
4. A  $200/440 \text{ V}$ ,  $50 \text{ Hz}$ , 1-phase transformer on test gave the following results:  
O.C. Test (L.V. Side):  $20 \text{ V}$ ,  $0.75 \text{ A}$ ,  $80 \text{ W}$   
S.C. Test (H.V. Side):  $20 \text{ V}$ ,  $12 \text{ A}$ ,  $100 \text{ W}$ . Find voltage regulation and efficiency at  $0.8 \text{ p.f. lagging}$  and full load. [16]
- 5.a) With the help of circuit diagram explain the procedure of obtaining V-I characteristics of P-N Junction diode.  
b) With an example, explain intrinsic and extrinsic semiconductors. [8+8]
6. Write short notes on the following:  
a) Zener diode  
b) BJT  
c) Applications of CRO. [5+5+6]
- 7.a) Explain the principle of generation of sinusoidally alternating voltages.  
b) Derive expression for power in three phase system. [8+8]
- 8.a) Currents through three parallel connected impedances are  $i_1(t) = 300 \sin(\omega t + 30^\circ)$ ,  $i_2(t) = 200 \sin(\omega t + 120^\circ)$  and  $i_3(t) = 175 \cos(\omega t + 45^\circ)$ . Determine the total current. Also draw the phasor diagram.  
b) What are the different types of generators? Explain in detail. [8+8]

\*\*\*\*\*

Code No: RR222104

RR

SET-3

**B.Tech II Year - II Semester Examinations, April/May-2012**  
**ELECTRICAL AND ELECTRONICS ENGINEERING**  
**(AERONAUTICAL ENGINEERING)**

**Time: 3 hours**

**Max. Marks: 80**

**Answer any five questions**  
**All questions carry equal marks**

---

- 1.a) With the help of circuit diagram, explain the procedure of conducting open circuit test on single phase transformer.
- b) Explain the procedure of determining voltage regulation of alternator. [8+8]
2. A 200/440 V, 50 Hz, 1-phase transformer on test gave the following results:  
O.C. Test (L.V. Side): 20 V, 0.75 A, 80 W  
S.C. Test (H.V. Side): 20 V, 12 A, 100 W. Find voltage regulation and efficiency at 0.8 p.f. lagging and full load. [16]
- 3.a) With the help of circuit diagram explain the procedure of obtaining V-I characteristics of P-N Junction diode.
- b) With an example, explain intrinsic and extrinsic semiconductors. [8+8]
4. Write short notes on the following:
  - a) Zener diode
  - b) BJT
  - c) Applications of CRO. [5+5+6]
- 5.a) Explain the principle of generation of sinusoidally alternating voltages.
- b) Derive expression for power in three phase system. [8+8]
- 6.a) Currents through three parallel connected impedances are  $i_1(t) = 300 \sin(\omega t + 30^\circ)$ ,  $i_2(t) = 200 \sin(\omega t + 120^\circ)$  and  $i_3(t) = 175 \cos(\omega t + 45^\circ)$ . Determine the total current. Also draw the phasor diagram.
- b) What are the different types of generators? Explain in detail. [8+8]
- 7.a) Derive expression for torque equation of D.C. Motor.
- b) A 4 pole DC generator with a shunt field resistance of  $100 \Omega$  and armature resistance of  $1 \Omega$  has 378 wave connected conductors in its armature. The flux per pole is 0.02 Wb. If a load resistance of  $10 \Omega$  is connected across the armature terminals and the generator is driven at 100 rpm, calculate the power absorbed by the load. [6+10]
- 8.a) Derive E.M.F. equation of single phase transformer.
- b) Explain the principle of operation of three phase induction motor. [8+8]

\*\*\*\*\*

Code No: RR222104

RR

SET-4

**B.Tech II Year - II Semester Examinations, April/May-2012**  
**ELECTRICAL AND ELECTRONICS ENGINEERING**  
**(AERONAUTICAL ENGINEERING)**

**Time: 3 hours**

**Max. Marks: 80**

**Answer any five questions**  
**All questions carry equal marks**

---

- 1.a) With the help of circuit diagram explain the procedure of obtaining V-I characteristics of P-N Junction diode.
- b) With an example, explain intrinsic and extrinsic semiconductors. [8+8]
2. Write short notes on the following:
  - a) Zener diode
  - b) BJT
  - c) Applications of CRO. [5+5+6]
- 3.a) Explain the principle of generation of sinusoidally alternating voltages.
- b) Derive expression for power in three phase system. [8+8]
- 4.a) Currents through three parallel connected impedances are  $i_1(t) = 300 \sin(\omega t + 30^\circ)$ ,  $i_2(t) = 200 \sin(\omega t + 120^\circ)$  and  $i_3(t) = 175 \cos(\omega t + 45^\circ)$ . Determine the total current. Also draw the phasor diagram.
- b) What are the different types of generators? Explain in detail. [8+8]
- 5.a) Derive expression for torque equation of D.C. Motor.
- b) A 4 pole DC generator with a shunt field resistance of  $100 \Omega$  and armature resistance of  $1 \Omega$  has 378 wave connected conductors in its armature. The flux per pole is  $0.02 \text{ Wb}$ . If a load resistance of  $10 \Omega$  is connected across the armature terminals and the generator is driven at  $100 \text{ rpm}$ , calculate the power absorbed by the load. [6+10]
- 6.a) Derive E.M.F. equation of single phase transformer.
- b) Explain the principle of operation of three phase induction motor. [8+8]
- 7.a) With the help of circuit diagram, explain the procedure of conducting open circuit test on single phase transformer.
- b) Explain the procedure of determining voltage regulation of alternator. [8+8]
8. A  $200/440 \text{ V}$ ,  $50 \text{ Hz}$ , 1-phase transformer on test gave the following results:  
O.C. Test (L.V. Side):  $20 \text{ V}$ ,  $0.75 \text{ A}$ ,  $80 \text{ W}$   
S.C. Test (H.V. Side):  $20 \text{ V}$ ,  $12 \text{ A}$ ,  $100 \text{ W}$ . Find voltage regulation and efficiency at  $0.8 \text{ p.f. lagging}$  and full load. [16]

\*\*\*\*\*