

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 8 marks and may have a, b, c as sub questions.

PART - A

5 × 4 marks = 20

- 1.a) Explain the Charge Injection Cancellation in Switched capacitor circuits with neat diagram. [4]
- b) Explain the block diagram of PLL. [4]
- c) Write short notes on Hybrid converters. [4]
- d) What is Interpolating? Explain. [4]
- e) What is the importance of oversampling converters? Explain. [4]

PART - B

5 × 8 marks = 40

2. Explain about Unity-Gain Sampler/Buffer with neat circuit diagram. [8]
- OR
3. Discuss the non-ideal effects in switched capacitor circuits. [8]
- 4.a) Explain the dynamics of simple PLL. [4+4]
- b) Discuss about jitter in PLLs. [4+4]
- OR
5. Explain in detail about charge-pump PLLs. [8]
6. List and explain the DC and Dynamic specifications of data converters. [8]
- OR
7. Briefly discuss about binary scaled converters. [8]
8. Explain about Two-step A/D converters. [8]
- OR
9. Explain about Folding A/D converters. [8]
10. Discuss in detail about higher order Modulators with respect to oversampling converters. [8]
- OR
11. Explain in detail about Delta sigma D/A converter. [8]