

**R16**

Code No: 133AB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2017

ANALOG ELECTRONICS

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c-as sub questions.

**PART-A**

(25 Marks)

- 1.a) What is Bias? What is the need for biasing? [2]
- b) How does the input impedance increases due to darlington connection? [3]
- c) Define Gain bandwidth product. [2]
- d) Mention important characteristics of CE amplifier. [3]
- e) Write the expression for basic current equation in MOSFET. [2]
- f) Compare the AC circuit characteristics of the CS, CG and CD. [3]
- g) List the four basic feedback topologies. [2]
- h) State Barkhausen criterion for sustained oscillation. What will happen to the oscillation if the magnitude of the loop gain is greater than unity? [3]
- i) Define Harmonic distortion and intermodulation distortion. [2]
- j) What are the advantages of push pull amplifiers? [3]

**PART-B**

(50 Marks)

- 2.a) In a single stage CB – amplifier circuit,  $R_E = 20K$ ,  $R_C = 10K$ ,  $V_{EE} = -20V$ ,  $V_{CC} = 20V$ ,  $R_L = 10K$ . Find out  $R_i$ ,  $R_o$ ,  $A_i$ ,  $A_v$  and power gain in dB.
- b) Draw the circuit of two stage R-C coupled transistor amplifier and explain the working of it. [6+4]

**OR**

- 3.a) The h-parameters of CE-amplifier are  $h_{ie} = 1100\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 24 \mu A/V$  and  $R_s = 1K\Omega$ ,  $R_L = 10K\Omega$ . Find out current and voltage gains with and without source resistance, input and output impedances.
- b) Discuss briefly Cascode amplifier. [6+4]

4. Derive the expression for the CE short circuit current gain  $A_i$  as a function of frequency using Hybrid -  $\pi$  model. [10]

**OR**

5. Define  $f_\beta$  and  $f_T$  and derive the relation between  $f_\beta$  and  $f_T$ . [10]

- 6.a) What is square law distortion? What is its effect in FET amplifiers?  
b) Draw the small-signal high-frequency circuit of a common source amplifier and derive the expression for voltage gain. [4+6]

OR

- 7.a) Why self-bias is not suitable for depletion type and enhancement type MOSFET?  
b) In a Drain-to-gate bias circuit  $V_{CD} = 12V$ ,  $R_d = 2k$ ,  $R_f = 10m$ . Calculate  $V_{GS}$ ,  $I_D$  and  $V_{DS}$  for  $I_{D(ON)} = 6mA$ ,  $V_{GS(ON)} = 8V$ ,  $V_{GS(TH)} = 3V$ . [4+6]

- 8.a) Explain with the help of mathematical expressions, how the negative feedback in amplifiers increases amplifier bandwidth and reduces distortion in amplifiers.  
b) In a transistorized Hartley oscillator the two inductances are  $2mH$  and  $20\mu H$  while the frequency is to be changed from  $950KHZ$  to  $2050KHZ$ . Calculate the range over which the capacitor is to be varied. [5+5]

OR

- 9.a) An amplifier circuit has a gain of  $60 dB$  and an output impedance  $Z_o = 10K\Omega$ . It is required to modify its output impedance to  $500\Omega$  by applying negative feedback. Calculate the value of the feedback factor. Also find the percentage change in the overall gain, for  $10\%$  change in the gain of the internal amplifiers.  
b) What are the factors that affect the frequency stability of an oscillator? How frequency stability can be improved in oscillators. [5+5]

- 10.a) Derive the equation for maximum efficiency of a class A transformer coupled amplifier.  
b) Explain the principle of stagger tuning technique of transformer – coupled amplifier that is used to obtain band pass filter characteristic with pass band of  $10 KHZ$  with all necessary diagrams for illustration. [5+5]

OR

- 11.a) Design a class B power amplifiers to deliver  $25w$  to a load resistor  $R_L = 8ohms$ , using transformer coupling.  $V_m = V_{cc} = 25V$ . Assume necessary data.  
b) Draw the circuit of double-tuned transformer-coupled amplifier. Discuss the nature of responses of the amplifier for different values of  $KQ = 1$ ;  $KQ > 1$  and  $KQ < 1$ . [5+5]

---ooOoo---