

R15

Code No: 124AF

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, December - 2017

DIGITAL DESIGN USING VERILOG HDL

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub-questions.

PART- A

(25 Marks)

- 1.a) Explain about strobe tasks. [2]
- b) Define logic levels relevant to verilog HDL. [3]
- c) What is drive strength of a device or gate in verilog. [2]
- d) Explain NOR gate primitive with example. [3]
- e) Define fork-join block. [2]
- f) Define force-release construct with an example. [3]
- g) Design verilog module for 4-bit full adder using dataflow operators. [2]
- h) What is recursive function [3]
- i) Write a short note on design verification. [2]
- j) Explain about implicit model. [3]

PART- B

(50 Marks)

- 2.a) Explain the synthesis procedure in verilog HDL.
 - b) Classify the data types and explain. [5+5]
- OR**
- 3.a) Explain different levels of design description in verilog.
 - b) What are the functions of programming language interface (PLI)? Explain. [5+5]
- 4.a) Write notes on tristate gates. Give the relevant syntax, logic diagrams and excitation tables.
 - b) Discuss about strings in detail. [5+5]
- OR**
- 5.a) Explain continuous assignment structures with examples.
 - b) Write about net delay with an example. [5+5]
- 6.a) Design verilog module to identify the highest priority interrupts.
 - b) Write test bench simulation results of above question with explanation. [5+5]
- OR**
- 7.a) Write the differences between begin-end and fork-join blocks.
 - b) Explain about multiple always blocks. [5+5]

- 8.a) What do you mean by user defined primitive? Explain the types with examples.
b) Explain briefly the module paths. [5+5]

OR

- 9.a) Discuss the basic transistor switches.
b) Explain the computer directives. [5+5]

- 10.a) Write and explain the verilog module for positive edge trigger flip-flop.
b) Discuss setup hold, width and period checks used in verilog. [5+5]

OR

- 11.a) Explain cross coupled NOR latch.
b) What are the various sequential memory storage models explain in detail. [5+5]

--ooOoo--