

R16

Code No: 134CC

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
B.Tech II Year II Semester Examinations, December - 2018

PULSE AND DIGITAL CIRCUITS
(Electronics and Communication Engineering)

Max. Marks: 75

Time: 3 Hours

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- 1.a) What is linear wave shaping? Give some examples. [2]
- b) Explain an uncompensated attenuator. [3]
- c) State clamping theorem. [2]
- d) Draw the transfer characteristics of two level clipper. [3]
- e) Draw a transistor as a switch. [2]
- f) Discuss about the transistor saturation. [3]
- g) Write down the application of diode Multivibrators. [2]
- h) How can be hysteresis eliminated in a Schmitt trigger? [3]
- i) Draw unidirectional sampling gate. [2]
- j) Compare MOS and CMOS families. [3]

PART-B

(50 Marks)

- 2.a) Explain the operation of RC high pass circuit with ramp input with circuit diagram.
- b) An ideal $1\mu\text{s}$ is fed to an amplifier. Calculate and plot the output waveform under the following conditions: the 3-dB frequency is [5+5]
i) 10MHz ii) 1MHz iii) 0.1MHz.

OR

- 3.a) Sketch an integrating circuit with a square wave input. Explain how the wave shape obtained.
- b) A $10\mu\text{f}$ capacitor is charged from a 5V source via a $10\text{K}\Omega$ resistance. Calculate the capacitor voltage after 50ms if it is initially charged to -2V. [5+5]

- 4.a) Explain the operation of a double diode clipper with help of circuit diagram and waveforms.

- b) Explain steady state output for a square wave input of a clamping circuit. [5+5]

OR

- 5.a) Discuss about synchronized clamping in detail. [5+5]
- b) Explain clamping operation with help of circuit diagram and waveforms.

- 6.a) Explain the Transistor breakdown in detail. [5+5]
b) Explain the effect of temperature on transistor characteristics. [5+5]

OR

7. List and define all the transistor switching times, with a neat diagrams. [10]

- 8.a) Design Astable Multivibrator and explain its operation with help of circuit diagram and waveforms.
b) Explain the operation of an exponential sweep circuit with help of circuit diagram and waveforms. [5+5]

OR

- 9.a) Discuss different methods improving linearity.
b) Design collector coupled Monostable Multivibrator and explain its operation with help of circuit diagram and waveforms. [4+6]

- 10.a) Compare DTL and TTL families. [4+6]
b) Discuss about RTL logic family in detail, with one example.

OR

- 11.a) Realize AND gate and OR gate using diodes.
b) Explain about Transistor - Transistor logic. Also mention the types of output configuration. [5+5]

---ooOoo---