

# Lecture 12

## Digital Circuits (II)

### MOS INVERTER CIRCUITS

#### Outline

- NMOS inverter with resistor pull-up
  - The inverter
- NMOS inverter with current-source pull-up
- Complementary MOS (CMOS) inverter
- Static analysis of CMOS inverter



#### **Reading Assignment:**

Howe and Sodini; Chapter 5, Section 5.4

# 1. NMOS inverter with resistor pull-up:
  
## Dynamics

- $C_L$  *pull-down* limited by current through transistor
  - [shall study this issue in detail with CMOS]
- $C_L$  *pull-up* limited by resistor ( $t_{PLH} \approx RC_L$ )
- Pull-up slowest



# 1. NMOS inverter with resistor pull-up:

## Inverter design issues

Noise margins  $\uparrow \Rightarrow |A_v| \uparrow \Rightarrow$

- $R \uparrow \Rightarrow |RC_L| \uparrow \Rightarrow$  slow switching
- $g_m \uparrow \Rightarrow |W| \uparrow \Rightarrow$  big transistor
  - (slow switching at input)


Trade-off between speed and noise margin.

During pull-up we need:


- High current for fast switching
- But also high incremental resistance for high noise margin.

## 2. NMOS inverter with current-source pull-up

I—V characteristics of current source:

 


Equivalent circuit models :

 



- High current throughout voltage range  $v_{SUP} > 0$
- $i_{SUP} = 0$  for  $v_{SUP} \leq 0$
- $i_{SUP} = I_{SUP} + v_{SUP}/r_{oc}$  for  $v_{SUP} > 0$
- High small-signal resistance  $r_{oc}$ .

# NMOS inverter with current-source pull-up

## Static Characteristics

 



Inverter characteristics :

  

High  $r_{oc} \Rightarrow$  high noise margins

## PMOS as current-source pull-up

I—V characteristics of PMOS:

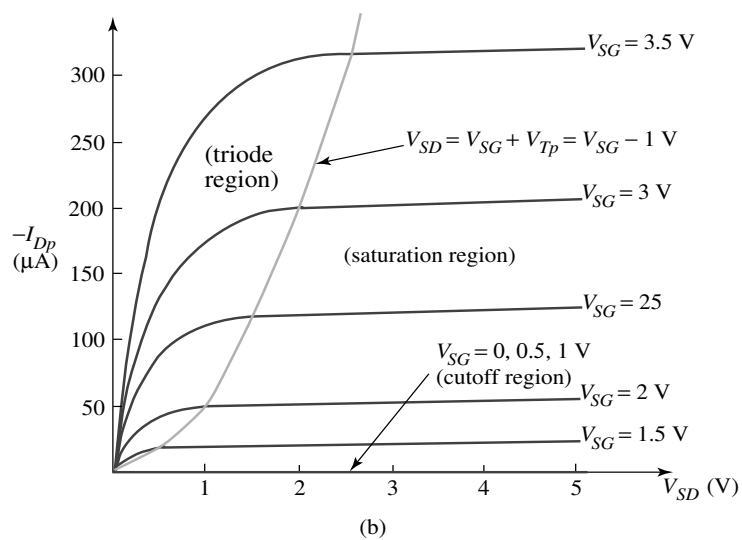 


Note: enhancement-mode PMOS has  $V_{Tp} < 0$ .

In saturation:


$$-I_{Dp} \propto (V_{SG} + V_{Tp})^2$$
 
## PMOS as current-source pull-up:

Circuit and load-line diagram of inverter with PMOS current source pull-up:



## Inverter characteristics:

 

## PMOS as current-source pull-up:


NMOS inverter with current-source pull-up allows high *noise margin* with *fast switching*

- High Incremental resistance
- Constant charging current of load capacitance

But...

When  $V_{IN} = V_{DD}$ , there is a direct current path between supply and ground

 
⇒ power is consumed even if the inverter is idle.





### 3. Complementary MOS (CMOS) Inverter

Circuit schematic:

 


Basic Operation:

- $V_{IN} = 0 \Rightarrow V_{OUT} = V_{DD}$   
 $V_{GSn} = 0 < V_{Tn} \Rightarrow$  **NMOS OFF**  
 $V_{SGp} = V_{DD} > -V_{Tp} \Rightarrow$  **PMOS ON**
- $V_{IN} = V_{DD} \Rightarrow V_{OUT} = 0$   
 $V_{GSn} = V_{DD} > V_{Tn} \Rightarrow$  **NMOS ON**  
 $V_{SGp} = 0 < -V_{Tp} \Rightarrow$  **PMOS OFF**
 
## CMOS Inverter (Contd.):

Output characteristics of both transistors:



Note:


$$V_{IN} = V_{GSn} = V_{DD} - V_{SGp} \Rightarrow V_{SGp} = V_{DD} - V_{IN}$$

$$V_{OUT} = V_{DSn} = V_{DD} - V_{SDp} \Rightarrow V_{SDp} = V_{DD} - V_{OUT}$$

$$I_{Dn} = -I_{Dp}$$


Combine into single diagram of  $I_D$  vs.  $V_{OUT}$  with  $V_{IN}$  as parameter

## CMOS Inverter (Contd.):

 


- *No current while idle in any logic state*

## Inverter Characteristics:

 

- *“rail-to-rail” logic: logic levels are 0 and  $V_{DD}$*
- *High  $|A_v|$  around logic threshold*  
 $\Rightarrow$  *good noise margins*

## 2. CMOS inverter: noise margins

 

- Calculate  $V_M$
- Calculate  $A_v(V_M)$
- Calculate  $NM_L$  and  $NM_H$

### Calculate $V_M$ ( $V_M = V_{IN} = V_{OUT}$ )

At  $V_M$  both transistors are saturated:

$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_M - V_{Tn})^2$$

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2$$

## CMOS inverter: noise margins (contd.)

Define:

$$k_n = \frac{W_n}{L_n} \mu_n C_{ox}; \quad k_p = \frac{W_p}{L_p} \mu_p C_{ox}$$

Since :

$$I_{Dn} = -I_{Dp}$$

Then:

$$\frac{1}{2} k_n (V_M - V_{Tn})^2 = \frac{1}{2} k_p (V_{DD} - V_M + V_{Tp})^2$$

Solve for  $V_M$ :

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_p}{k_n}}}$$

Usually,  $V_{Tn}$  and  $V_{Tp}$  fixed and  $V_{Tn} = -V_{Tp}$   
 $\Rightarrow V_M$  engineered through  $k_p/k_n$  ratio.

## CMOS inverter: noise margins (contd..)

- **Symmetric case:**  $k_n = k_p$

$$V_M = \frac{V_{DD}}{2}$$

This implies:

$$\frac{k_p}{k_n} = 1 = \frac{\frac{W_p}{L_p} \mu_p C_{ox}}{\frac{W_n}{L_n} \mu_n C_{ox}} \approx \frac{\frac{W_p}{L_p} \mu_p}{\frac{W_n}{L_n} 2\mu_p} \Rightarrow \frac{W_p}{L_p} \approx 2 \frac{W_n}{L_n}$$

Since usually  $L_p \approx L_n = L_{min} \Rightarrow W_p \approx 2W_n$

- **Asymmetric case:**  $k_n \gg k_p$ , or  $\frac{W_n}{L_n} \gg \frac{W_p}{L_p}$

$$V_M \approx V_{Tn}$$

NMOS turns on as soon as  $V_{IN}$  goes above  $V_{Tn}$ .

- **Asymmetric case:**  $k_n \ll k_p$ , or  $\frac{W_n}{L_n} \ll \frac{W_p}{L_p}$



$$V_M \approx V_{DD} + V_{Tp}$$

PMOS turns on as soon as  $V_{IN}$  goes below  $V_{DD} + V_{Tp}$ .

## CMOS inverter: noise margins (contd...)

### Calculate $A_v(V_M)$


- Small signal model:

 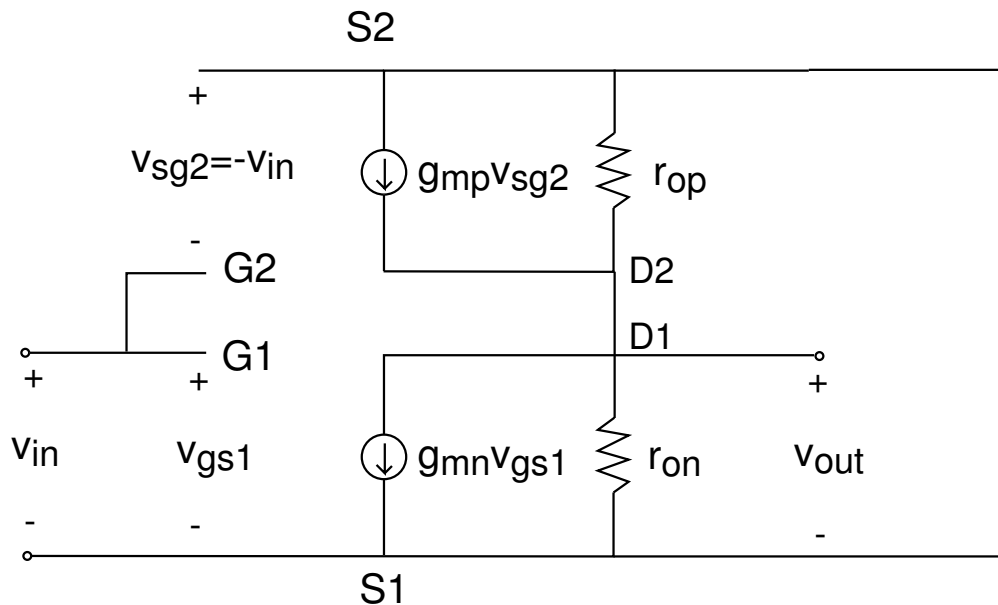

$$A_v = - (g_{mn} + g_{mp}) (r_{on} // r_{op})$$

This can be rather large.
 
## CMOS inverter: calculate noise margins (contd.)



- Noise-margin low,  $NM_L$ :

$$V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

- Noise-margin high,  $NM_H$ :

$$V_{IH} = V_M \left( 1 + \frac{1}{|A_v|} \right)$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_M \left( 1 + \frac{1}{|A_v|} \right)$$



# What did we learn today?

## Summary of Key Concepts

- In NMOS inverter with resistor pull-up, there is a trade-off between noise margin and speed
- Trade-off resolved using current source pull-up
  - Use PMOS as current source.
- In NMOS inverter with current-source pull-up: if  $V_{IN} = \text{High}$ , there is power consumption even if inverter is idling.
- Complementary MOS: **NMOS and PMOS switch-on alternatively.**
  - No current path between power supply and ground
  - No power consumption while idling
- Calculation of CMOS
  - $V_M$
  - Noise Margin

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.