

MIT OpenCourseWare
<http://ocw.mit.edu>

6.334 Power Electronics
Spring 2007

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.


Power Electronics Notes - D. Perreault

Notes: Reading K&V Chapter 24

★★ Switching Losses and snubbers

★ Semiconductor Losses (Back of the Envelope)


Example: Buck converter w/ MOSFET

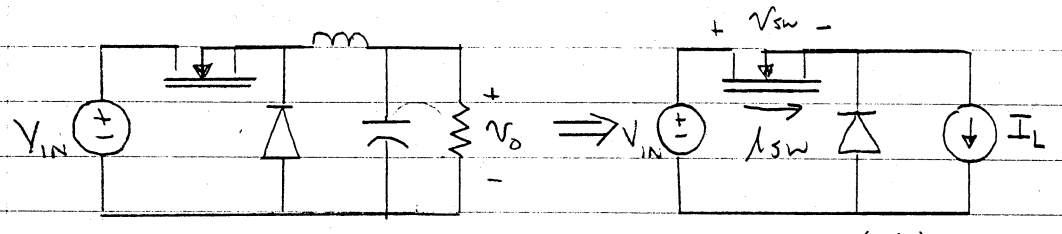

Conduction losses

Fet (resistive) $P_{FET,cond} = I_{rms}^2 R_{ds,on} \approx (I_L D) R_{ds,on}$
 Diode (const drop) $P_{d,cond} = \langle I_{diode} \rangle V_{d,on} \approx (I_L D') V_{d,on}$

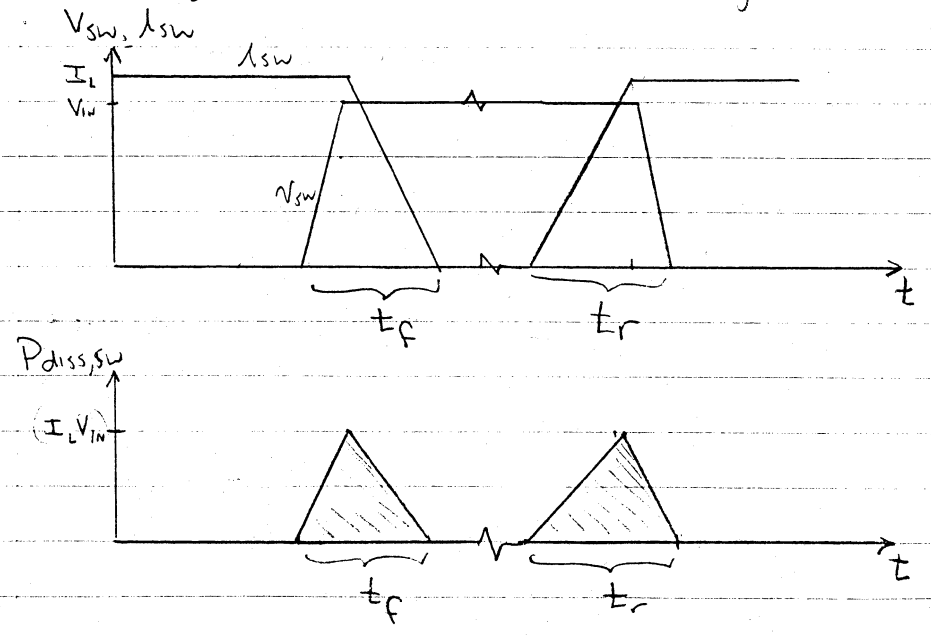Switching Losses (Zoom in on switching) \Rightarrow back of the envelope only!



TURN OFF OF FET
 current falls After voltage rises (diode must turn on before sw. current falls)
 t_f governed by device params + gate drive

Turn on of FET
 current rises before voltage falls (diode must conduct until switch carries whole current)
 t_r governed by device params + gate drive

Linear transitions are a rough approximation!

$$P_{switch,sw} \approx \left(\frac{1}{2} t_f V_{in} I_L + \frac{1}{2} t_r V_{in} I_L \right) f$$

$$= \frac{1}{2} V_{in} I_L (t_f + t_r) f$$

\Rightarrow other losses (e.g. diode rev. recov.) also exist


Power Electronics Notes - D. Perreault

⇒ major switching loss component $\propto f$, we want $f \uparrow$ so L, C size \downarrow but losses limit us.

Other Issues

- we want to switch fast ($\downarrow t_f, t_r$) but other factors exist:

→ Parasitics + Overshoots

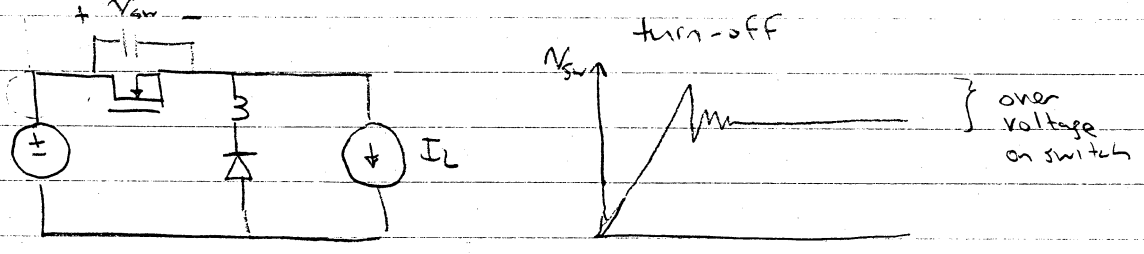


→ EMI

high $\frac{dI}{dt}$, $\frac{dV}{dt}$ lead to EMI, + affects control circuits
($\frac{dV}{dt} \rightarrow$ Capacitive coupling, $\frac{dI}{dt} \rightarrow$ Inductive coupling)

→ Safe Operating Area

Some devices have limitations on simultaneous voltage + current applied instantaneously (BJT's, GTO's, MCT's)

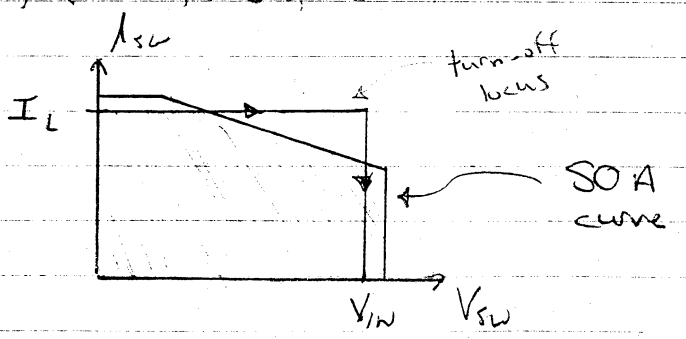Can operate at I_L and can operate at V_{in} , but NOT AT SAME TIME




→ Also, some devices have $\frac{dI}{dt}$ or $\frac{dV}{dt}$ limits (esp. thyristor type devices)

Power Electronics Notes - D. Perreault

- ★ Snubbers : 1.) Control switching Locus
2.) Lower the internal device dissipation

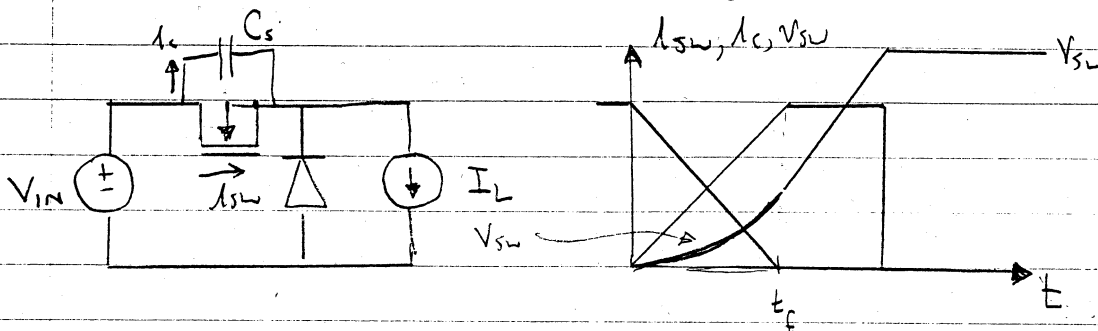If Capacitor across device during turn-off





I_L diverted through C_s while switch turns off.

Reduced V -rise across switch during turn off \rightarrow Lower switch losses

★ BUT there will be a big problem when the switch turns on!!

\therefore Simple RCD turn off snubber

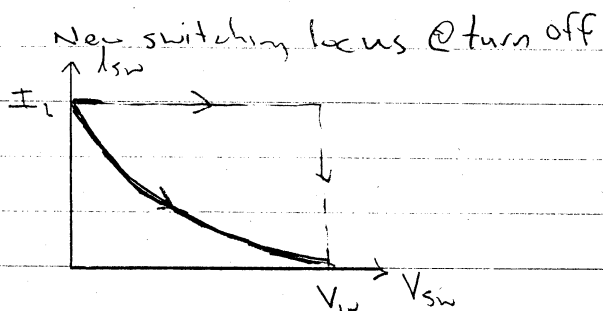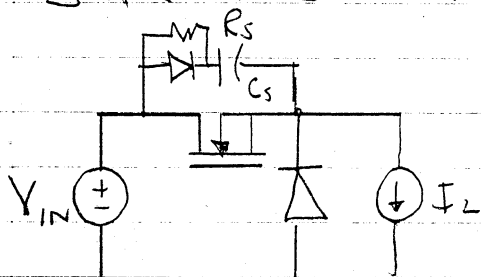

During turn-off, same as above


As calculated on the next page: $W_{\text{turn-off, sw}} \approx \frac{I_L^2 t_f^2}{24C_s}$

During turn on, dissipate C_s energy in R_s $W_{es} = \frac{1}{2} C_s V_{in}^2$
(Note: Need a min duty ratio \neq dutival)

Snubber reduces device switching loss, but increases total dissipation. (typically; this depends on device capacitance)
 \rightarrow definitely more loss if device capacitance exceeds "actual" capacitance

To size snubber, trade, P_{device} , P_{R_s} , $\frac{dv}{dt}$ I_{SWA} , min duty cycle.

Power Electronics Notes - D. Perreault

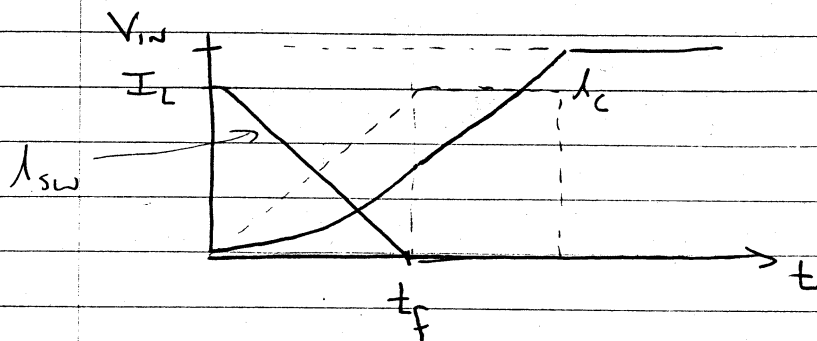

The turn-off loss + Capacitor charging can be calculated as follows:

$$I_{sw}(t) = I_L (1 - t/t_f) \quad 0 < t < t_f$$

$$I_c = I_L (t/t_f) \quad 0 < t < t_f$$

$$V_{sw} = \frac{1}{C} \int_0^t I_c(t) dt = \frac{I_L}{2C t_f} t^2 \quad 0 < t < t_f$$

$$\begin{aligned} \therefore E_{sw,off} &= \int_0^{t_f} V_{sw} I_{sw} dt = \int_0^{t_f} \frac{I_L^2}{2C t_f} \left(t^2 - \frac{t^3}{t_f} \right) dt \\ &= \frac{I_L^2}{6C} t_f^2 - \frac{I_L^2}{8C} t_f^2 \end{aligned}$$

$$E_{sw,off} = \frac{I_L^2 t_f^2}{24C}$$

With no capacitance, we would get

$$E_{loss} = \frac{1}{2} I_L V_{in} t_f$$

$$V_{pk} @ \text{sw. turn off} = \frac{I_L}{2C} t_f \quad (\text{assumed } < V_{in})$$

$$E_{stored} (\text{in capacitor}) = \frac{1}{2} C V_{in}^2$$


$$\text{This is } \geq \frac{1}{2} C \frac{I_L^2 t_f^2}{4C^2} = \frac{I_L^2 t_f^2}{8C}$$

$V_{pk} @$
sw. off point

• The stored energy in C is much larger than the switch transition loss.

Power Electronics Notes - D. Perreault

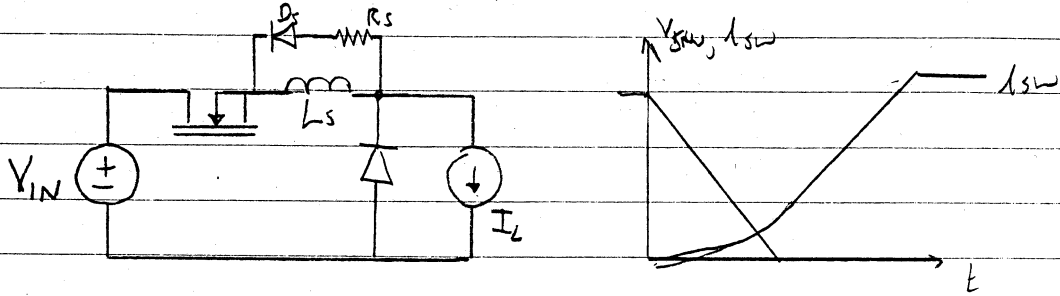Similar snubbing can be implemented for turn on




- reduced switch, diode I_{Ls}
- increased total loss (incl. R_s)
- controlled switching locus (SOA, $\frac{dI}{dt}$)

* Note: Snubber reset implies max duty ratio and imposes an overvoltage on the switch!!!

ZCS/ZVS Techniques, dc-dc converter applications

REVIEW: (put initial stuff on board before class)

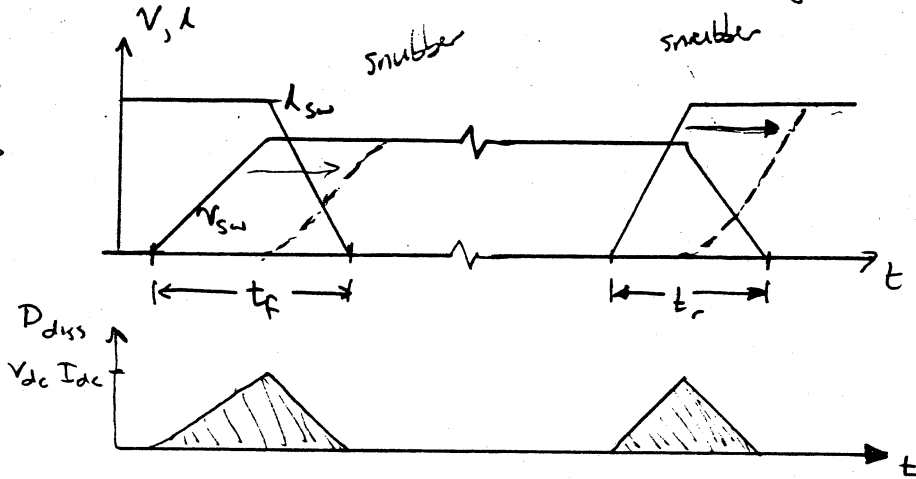The switching transitions in conventional PWM converters generate losses due to the nature of the V, I waveforms during the transitions.




Turn off:
 V rises 1st (dudew)
 I falls 2nd

Turn on:
 I rises 1st (dudew)
 V falls 2nd

This has 3 deleterious effects:

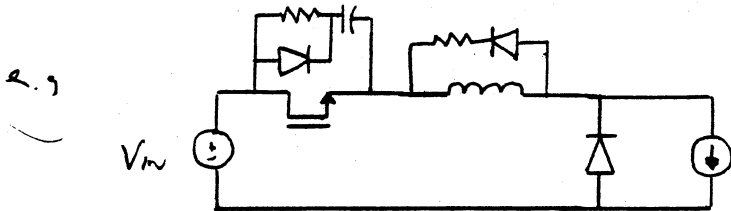1. Achievable f_{sw} & efficiency limited
2. EMI due to fast $di/dt, dv/dt \Rightarrow$ NOISE
3. Switching locus may exceed SOA

LAST TIME: SNUBBERS MITIGATE THESE EFFECTS, BUT ADD LOSSES



Today: Soft-Switching techniques try to mitigate these effects without adding substantial losses.

GENERAL METHODS: Zero-Voltage Switching (ZVS)
 Zero-Current Switching (ZCS)

can be applied to both turn-on and turn-off

These techniques typically require additional circuitry &/or control complexity, &/or additional conduction losses. But, the trade may be worth it...

effects


National Brand

12 782 500 SHEETS FULL SIZE SQUARE
 42 381 50 SHEETS EYE GLASS SQUARE
 42 384 100 SHEETS EYE GLASS SQUARE
 42 389 200 SHEETS EYE GLASS SQUARE
 42 390 200 SHEETS EYE GLASS SQUARE
 42 395 200 SHEETS EYE GLASS SQUARE
 200 RECYCLED WHITE SQUARE
 Made in U.S.A.

3-14-00


Other versions of this technique exist (Half-wave, ZVS version) and for many converter types (boost, buck-boost, Cuk, sepic, etc.)

ex/ ZVS Half-wave QR buck converter

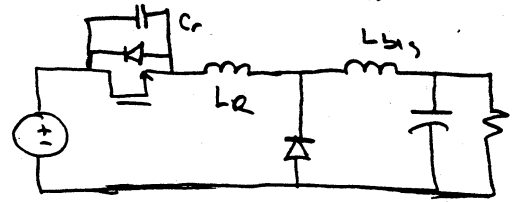

FINAL ASIDE: This converter type is forced to use frequency control to achieve soft switching. (which has its disadvantages) - We are very used to duty ratio (or fixed-frequency PWM) control, but there are actually many methods:

- ex/ Fixed freq PWM
- Frequency control
- Phase-shift control
- Phase control (ac systems)
- and more...

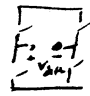show full-bridge example to demo alternative methods


Next example: suppose we want to retain PWM control. We can do this (at a price)

ZVS PWM Buck Converter Example

Extra circuitry & control (+ increased device ratings) to allow soft-switched operation.

Explain operational cycle + duty ratio control approach

- main sw: ZVS turn on, ZVS turn off
- Aux sw: ZVS/ZCS turn on, ZVS turn off
- Diode: ZVS turn on, (poor) ZCS turn off

Advantages: Duty ratio control of main switch (over a range) (PWM) low loss on main & aux switch @ turn off junction cap on main sw is part of Cr. (no turn-on loss)

Disadvantages: Very high voltage rating on main switch (varies w/ load) additional switch & control circuitry → complexity only limited reduction of diode losses at turn off

Other versions of this approach exist (i.e. ZCS, other topologies)


500 SHEETS FULLER'S SQUARE
50 SHEETS FULLER'S SQUARE
25 SHEETS FULLER'S SQUARE
100 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE
42 SHEETS FULLER'S SQUARE




Many other soft-switching approaches exist, some with PWM control (ex / Zero-Voltage Transition Circuits), and some with other methods (ex / phase-shift full bridge, resonant converters, etc.)

Next time: more soft switching techniques. We will focus on popular methods for bidirectional converters and inverters (esp 3ϕ). Esp focus on RPI, AECF, RDCL topologies.

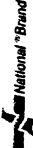
14-002
42-387
42-389
42-390
42-391
42-999
43-000



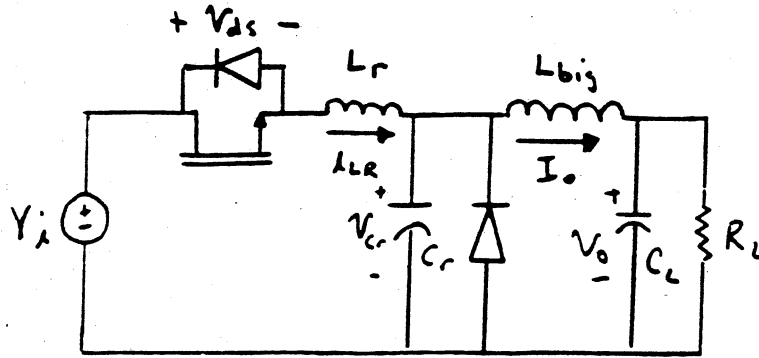
Full-Wave ZCS Quasi-Resonant Buck Converter




Converter

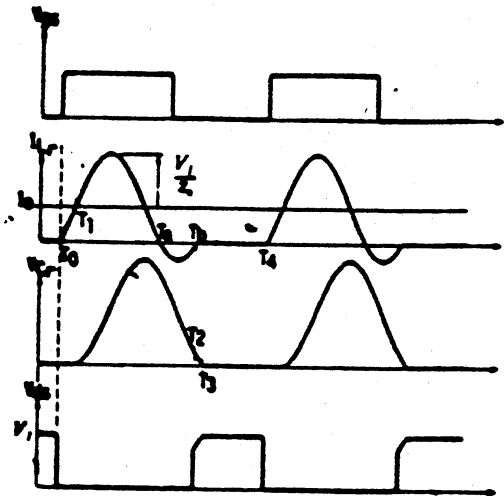


Ideal Waveforms

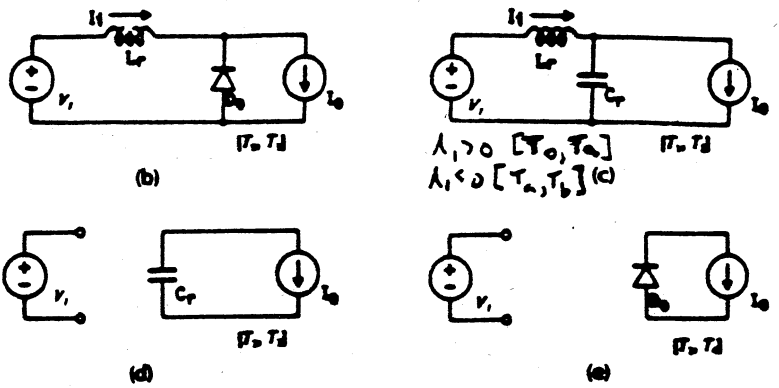

Operating Modes


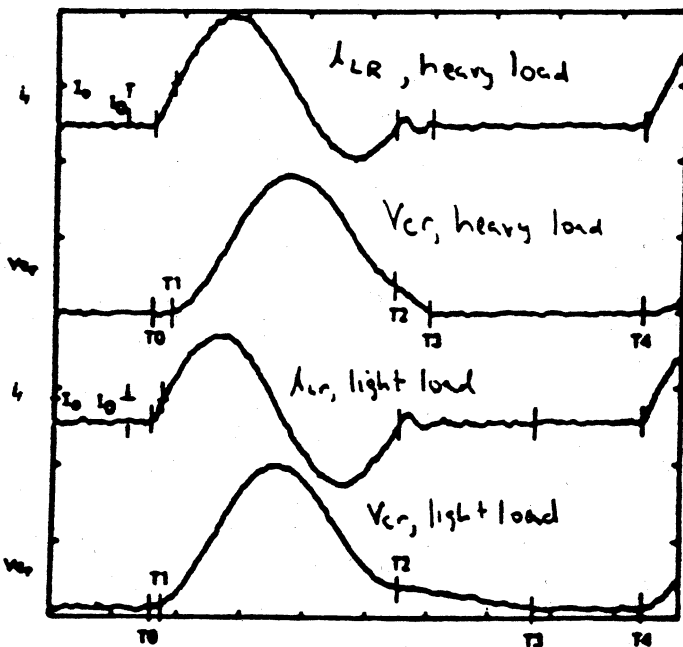


Waveforms at heavy, light loads

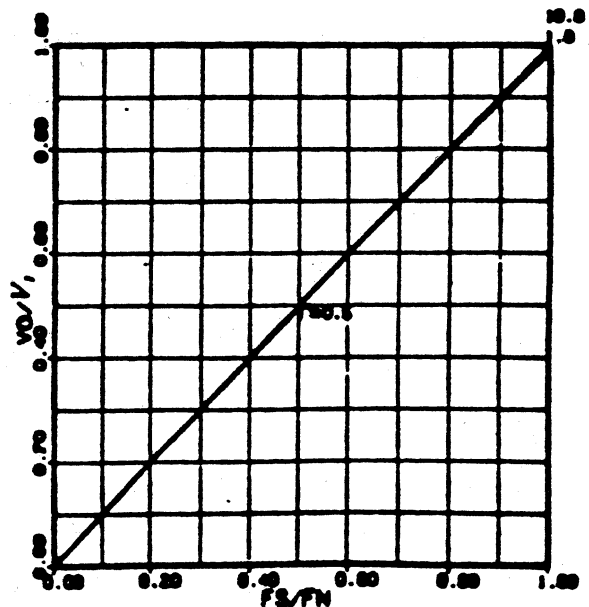

Control Characteristics

ZVS PWM Buck Converter

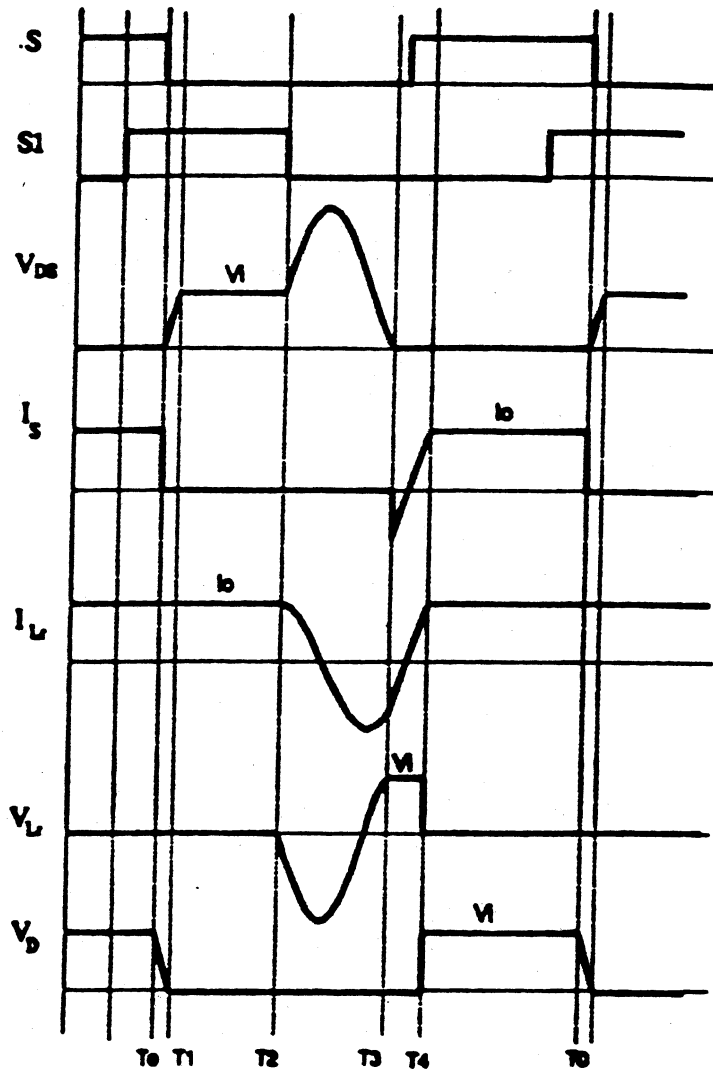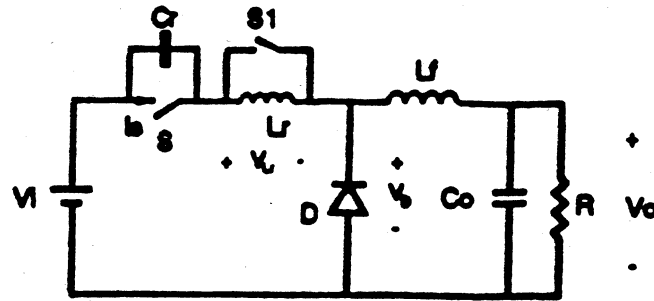

- Main Switch S: ZVS Turn on, ZVS Turn off
- Diode D: ZVS Turn on, poor (high di/dt) ZCS turn off
- Aux. Switch S1: ZVS/ZCS Turn on, ZVS turn off

Figure from "An Overview of Soft-Switching Techniques for PWM Converters," by G. Hua and F.C. Lee, European Power Electronics Journal, Vol. 3, No. 1, March 1993.